



# SVR ENGINEERING COLLEGE

Approved by AICTE & Permanently Affiliated to JNTUA

Ayyalurmetta, Nandyal – 518503. Website: [www.svrec.ac.in](http://www.svrec.ac.in)

Department of Electronics and Communication Engineering



**(15A04404) ELECTRONIC CIRCUIT ANALYSIS LABORATORY R15**

**II B. Tech (ECE) II Semester 2018-19**



STUDENT NAME	
ROLL NUMBER	
SECTION	





# **SVR ENGINEERING COLLEGE**

**Approved by AICTE & Permanently Affiliated to JNTUA**

Ayyalurmetta, Nandyal – 518503. Website: [www.svrec.ac.in](http://www.svrec.ac.in)

## **DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING CERTIFICATE**

**ACADEMIC YEAR: 2018-19**

*This is to certify that the bonafide record work done by*

*Mr./Ms. \_\_\_\_\_ bearing*

*H.T.NO. \_\_\_\_\_ of II B. Tech II Semester in the*

**ELECTRONIC CIRCUIT ANALYSIS LABORATORY.**

**Faculty In-Charge**

**Head of the Department**

**LIST OF EXPERIMENTS      Branch: ECE    Regulation:R15**

**(Minimum 10 experiments to be done using simulation software and hardware)**

1. Determination of  $f_T$  of a given transistor.
2. Voltage-Series Feedback Amplifier.
3. Current-Shunt Feedback Amplifier.
4. RC Phase Shift/Wein Bridge Oscillator.
5. Hartley/Colpitt's Oscillator.
6. Two Stage RC Coupled Amplifier.
7. Darlington Pair Amplifier.
8. Bootstrapped Emitter follower.
9. Class A Series-fed Power Amplifier.
10. Transformer-coupled Class A Power Amplifier.
11. Class B Push-Pull Power Amplifier.
12. Complementary Symmetry Class B Push-Pull Power Amplifier.
13. Single Tuned Voltage Amplifier.
14. Double Tuned Voltage Amplifier.

# **ECE DEPT VISION & MISSION PEOs and PSOs**

## **Vision**

To produce highly skilled, creative and competitive Electronics and Communication Engineers to meet the emerging needs of the society.

## **Mission**

- Impart core knowledge and necessary skills in Electronics and Communication Engineering  
Through innovative teaching and learning.
- Inculcate critical thinking, ethics, lifelong learning and creativity needed for industry and society
- Cultivate the students with all-round competencies, for career, higher education and self-employability

## **I. PROGRAMME EDUCATIONAL OBJECTIVES (PEOs)**

- PEO1: Graduates apply their knowledge of mathematics and science to identify, analyze and solve problems in the field of Electronics and develop sophisticated communication systems.
- PEO2: Graduates embody a commitment to professional ethics, diversity and social awareness in their professional career.
- PEO3: Graduates exhibit a desire for life-long learning through technical training and professional activities.

## **II. PROGRAM SPECIFIC OUTCOMES (PSOs)**

- PSO1: Apply the fundamental concepts of electronics and communication engineering to design a variety of components and systems for applications including signal processing, image processing, communication, networking, embedded systems, VLSI and control system
- PSO2: Select and apply cutting-edge engineering hardware and software tools to solve complex Electronics and Communication Engineering problems.

### **III. PROGRAMME OUTCOMES (PO'S)**

- 1. Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
- 2. Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
- 3. Design/development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
- 4. Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
- 5. Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
- 6. The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
- 7. Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
- 8. Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
- 9. Individual and team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
- 10. Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
- 11. Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
- 12. Life-long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

### **IV. COURSE OBJECTIVES:**

- To review analysis & design of single stage amplifiers using BJT & MOSFETs At low and high frequencies.
- To understand the characteristics of Differential amplifiers, feedback and power amplifiers.
- To examine the response of tuned amplifiers and multi-vibrators
- To categorize different oscillator circuits based on the application
- To design the electronic circuits for the given specifications and for a given application.

## **V. COURSE OUTCOMES:**

After the completion of the course students will be able to

<b>Course Outcomes</b>	<b>Course Outcome statements</b>	<b>BTL</b>
<b>CO1</b>	The ability to analyze and design single and multistage amplifiers at low, mid and high frequencies.	L1
<b>CO2</b>	Designing and analyzing the transistor at high frequencies.	L2
<b>CO3</b>	Determine the efficiencies of power amplifiers	L3
<b>CO4</b>	Determine Frequency response and design of tuned amplifiers.	L4
<b>CO5</b>	Able to Analyze all the circuits using simulation software and Hardware.	L5

## **VI. COURSE MAPPING WITH PO'S AND PEO'S:**

<b>Course Title</b>	<b>PO 1</b>	<b>PO 2</b>	<b>PO 3</b>	<b>PO 4</b>	<b>PO 5</b>	<b>PO 6</b>	<b>PO 7</b>	<b>PO 8</b>	<b>PO 9</b>	<b>PO 10</b>	<b>PO 11</b>	<b>PO 12</b>	<b>PSO 1</b>	<b>PSO 2</b>
<b>Electronic Circuit Analysis Lab</b>	3	3	2	3	3	2	2	1	2	2	1	2	3	2

## **VII. MAPPING OF COURSE OUTCOMES WITH PEO'S AND PO'S:**

<b>Course Title</b>	<b>PO 1</b>	<b>PO 2</b>	<b>PO 3</b>	<b>PO 4</b>	<b>PO 5</b>	<b>PO 6</b>	<b>PO 7</b>	<b>PO 8</b>	<b>PO 9</b>	<b>PO 10</b>	<b>PO 11</b>	<b>PO 12</b>	<b>PSO 1</b>	<b>PSO 2</b>
<b>CO1</b>	3	3	3	3	3	2	1	1	1	2	1	2	3	2
<b>CO2</b>	2	2	2	2	2	1	2	1	2	2	1	2	2	2
<b>CO3</b>	3	3	3	3	3	3	2		2	2	1		3	2
<b>CO4</b>	2	3	2	3	2	2	2	2	2	1	2	2	2	2
<b>CO5</b>	3	3	2	2	3	2	1	1	1	2		1	3	1

## **LABORATORY INSTRUCTIONS**

1. While entering the Laboratory, the students should follow the dress code. (Wear shoes and White apron, Female Students should tie their hair back).
2. The students should bring their observation book, record, calculator, necessary stationery items and graphsheets if any for the lab classes without which the students will not be allowed for doing the experiment.
3. All the Equipment and components should be handled with utmost care. Any breakage or damage will be charged.
4. If any damage or breakage is noticed, it should be reported to the concerned in charge immediately.
5. The theoretical calculations and the updated register values should be noted down in the observation book and should be corrected by the lab in-charge on the same day of the laboratory session.
6. Each experiment should be written in the record note book only after getting signature from the lab in-charge in the observation notebook.
7. Record book must be submitted in the successive lab session after completion of experiment.
8. 100% attendance should be maintained for the laboratory classes.

### **Precautions.**

1. Check the connections before giving the supply.
2. Observations should be done carefully.



I N D E X

**Max. Marks per each experiment : 5**

[illegible]

Sl. No.	Name of the Experiment	Page No.	Date of Performed	Date of Submission	Marks Obtained	Signature of lab incharge
-----	<b>PART – B (Using Hardware) :</b>	-----				
01	Voltage series feedback amplifier	61				
02	Bootstrapped emitter follower	65				
03	Darlington pair amplifier	69				
04	Two stage RC coupled amplifier	73				
05	Current shunt feedback amplifier	79				
06	Single tuned voltage amplifier	83				
07	Class A series-fed power amplifier	89				
08	Complementary symmetry Class B push-pull power amplifier	93				
09	RC phase shift oscillator	97				
10	Colpitt's oscillator	101				
	<b>PART – C - Beyond the Syllabus :</b>					
11	CE-CB Cascode Amplifier :	107				
12	Astable Multivibrator :	111				
	<b>PART – D -Data Sheets , Rules &amp; Syllabus Copy :</b>					
A	<b>Data sheets :</b> PN Diode & Zener Diodes, BJT&UJT JFET-BF W10, BF W11 & BF 245 MOSFET-Z44N	117				
B	<b>Rules :</b> Rules to operate <i>RPS</i> & <i>CRO</i> Rules to write Observation & Record	129				
C	<b>Syllabus Copy</b>	131				

# **PART – A**

**Using simulation software**

**(Off the Syllabus )**



**Experiment No. : 01****Date :**

**Name of the Experiment : VOLTAGE SERIES FEED BACK AMPLIFIER**  
(By using simulation software)

**AIM :**

To obtain the frequency response of *Voltage Series feedback Amplifier*.

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

**THEORY :**

1. Amplifier means which amplifies the sinusoidal and non-sinusoidal wave forms with out change in frequency. In voltage series feedback amplifier, network is in parallel with the the output of the amplifier.
2. A fraction of the output voltage through the feedback network is applied in series with in the input voltage of the amplifier.
3. The series connections at the input, increase the input resistance. In this case the amplifier is a true voltage amplifier.
4. The common collector or emitter follower is an example of voltage series feedback amplifier. Since the voltage developed in the output is in series with the input voltage as for as the base – emitter junction is connected.

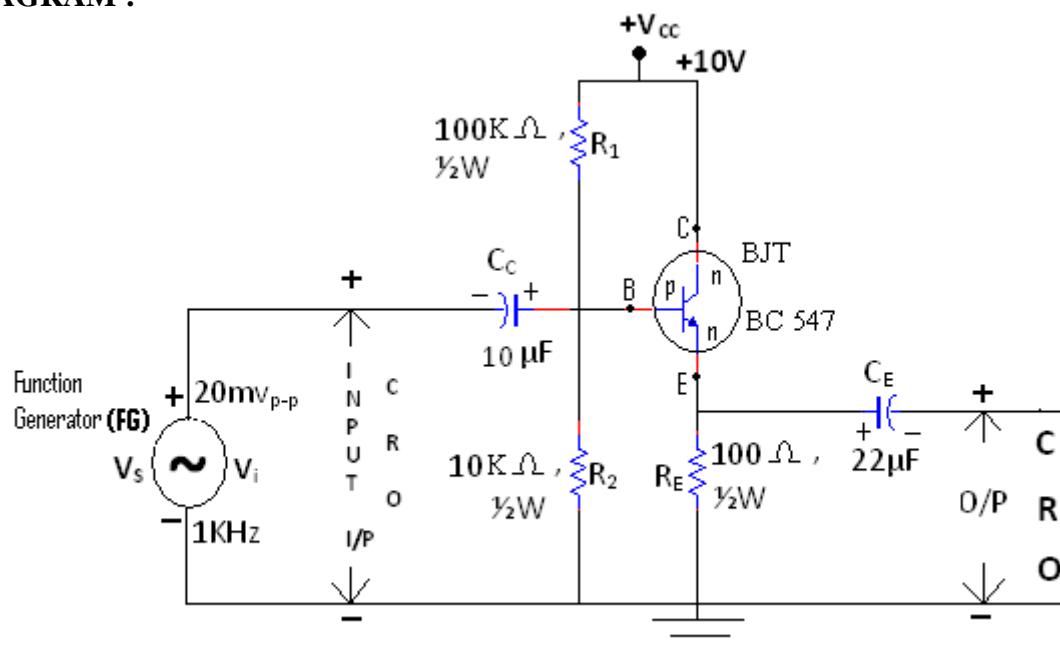
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of voltage series feed back amplifier.

**PROCEDURE :**

1. We have picked up the components from the components bar as per above circuit.
2. Made the connections as per the above circuit diagram by using the components which we have picked up.
3. Connected the CRO across the *Emitter capacitor to ground*.
4. Set the input signal as *sine wave form which is having the value 20mV<sub>P-P</sub>* as constant in the function generator.
5. Initially set the input signal frequency value is 1KHz in the function generator.
6. To simulate the circuit clicked on *run option* through *execute button* in *tool bar*.
7. We have seen the *sine wave* on the **CRO** screen as o/p signal.
8. Calculated the *peak to peak voltage ( $V_{O(p-p)}$ )* and noted down in the tabular form Against the column of 1KHz.
9. Stopped the simulation by clicked on *run option* through *execute button* in the *tool bar*.
10. Repeat the same procedure from points 6 to 9 for the corresponding frequency values by setting in the function generator for the following steps,  
10Hz, 500Hz, 1KHz, 100KHz, 200KHz, 400KHz, 600KHz, 800KHz, 1MHz, 100MHz, 500MHz. in the function generator.
11. Observed the graph for *frequency Vs amplitude* through the *AC Analysis*.
12. Finally shut down the system safely.
13. We have observed that, the graph which is drawn by manually is same to the graph which is obtained from the *AC Analysis*.
14. Now calculated and noted down the values of *voltage gain ( $A_v$ )* and *gain in dB* to the corresponding values of *output voltage ( $V_o$ )* & *input voltage ( $V_i$ )* by using the formulas given below,  
$$\text{Voltage gain } (A_v) = V_o / V_i \quad \text{and} \quad \text{Gain in dB} = 20\log_{10}(A_v).$$
15. Plotted the graphs (frequency response curves) as per below
  - a). frequency on X-axis & gain in dB on Y-axis.
  - b). frequency on X-axis & voltage gain on Y-axis.

**TABULAR FORM :**

Sl.No.	Input Voltage( $V_i$ ) In milli Volts (peak to peak)	Frequency In Hz/KHz.	Output Voltage( $V_o$ ) In mVolts.	Voltage gain $A_v = V_o/V_i$	Gain in dB = $20\log_{10}(A_v)$
01	20mV	10 Hz.			
02	20mV	500 Hz.			
03	20mV	1 KHz.			
04	20mV	100 KHz.			
05	20mV	200 KHz.			
06	20mV	400 KHz.			
07	20mV	600 KHz.			
08	20mV	800 KHz.			
09	20mV	1 MHz.			
10	20mV	100 MHz			
11	20mV	500 MHz.			

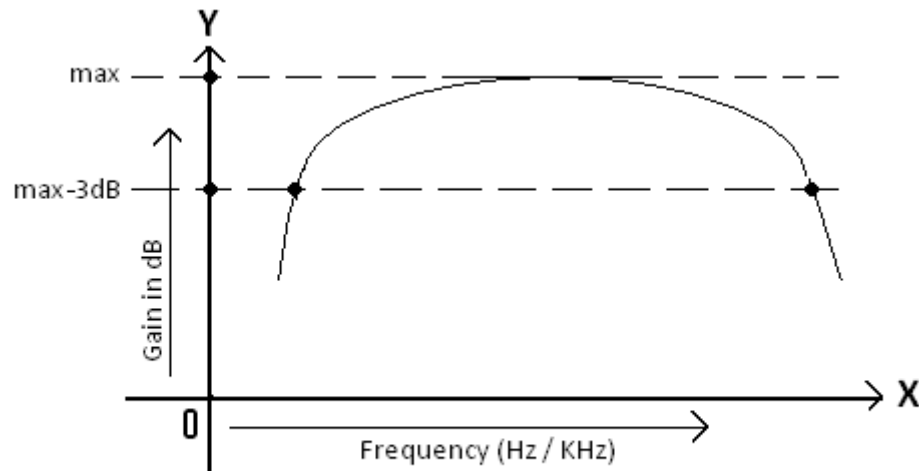
**EXPECTED GRAPH :**

Figure: Frequency response curve of voltage series feed back amplifier.  
For frequency verses gain in dB.

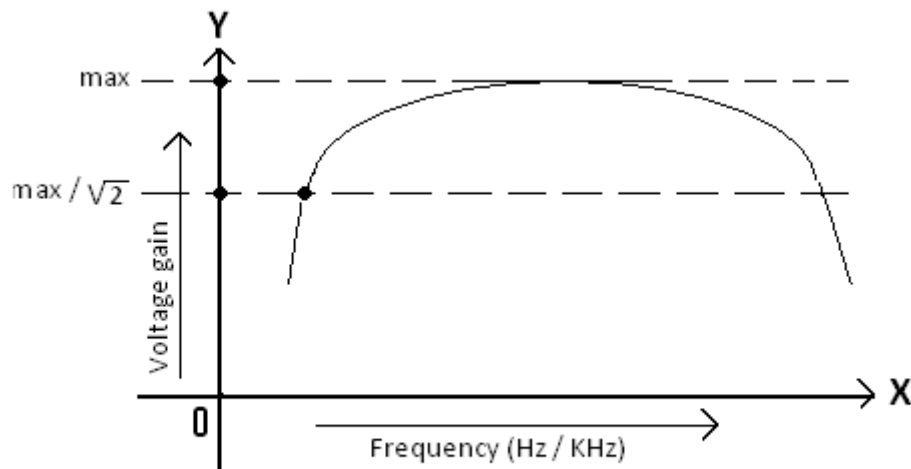


Figure: Frequency response curve of voltage series feed back amplifier.  
For frequency verses voltage gain.

*Note :* It is not possible to find the band width because there is no amplification in this amplifier. It is just working as *buffer*.

**RESULT :**

We have obtained the frequency response curve *frequency verses gain in dB* and *frequency verses voltage gain of a given amplifier*.

**VIVA VOICE QUESTIONS:**

1. What is feedback?
2. What are the advantages of negative feedback?
3. What are the feedback topologies?
4. Example for voltage series feedback amplifier.
5. What are the CC Amplifier characteristics?
6. What are the Applications of Multi stage amplifiers?
7. Example for voltage series feedback amplifier.
8. CC Amplifier characteristics?
9. What is Band Width?
10. Explain the transistor operation with the help of four regions.



**Experiment No. : 02****Date :**

**Name of the Experiment : BOOTSTRAPPED EMITTER FOLLOWER**  
(By using simulation software)

**AIM :**

To obtain the frequency response of *Bootstrapped Emitter Follower*

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

**THEORY :**

Typically Bootstrapping is technique where some part of output is used at the startup. In Bootstrap amplifier, bootstrapping is used to increase the input impedance. Due to which the loading effect on the input source also decreases. The design looks similar to the Darlington pair, having a bootstrap capacitor. Bootstrap capacitor is used to provide AC signal's positive feedback to the base of the transistor. This positive feedback help in improving the effective value of the base resistance. This increment in the base resistance also determined by the voltage gain of the amplifier circuit.

High input impedance improves the amplification of the input signal and thus required in various amplifier applications. If we have low input impedance we will get low amplification. Generally, BJT (Bipolar Junction Transistor) have low input impedance (typically 1 ohm to 50 kilo ohm). So for this, bootstrapping technique is used to increase the input impedance.

The voltage across the input impedance is calculated by using the below formula:

$$V = \{(V_{in} \cdot Z_{in}) / (V_{in} + Z \cdot V_{in})\}$$

Hence, according to the formula, the input impedance is proportional to the voltage across it. If the input impedance is increased the voltage across it will also increase and vice versa.

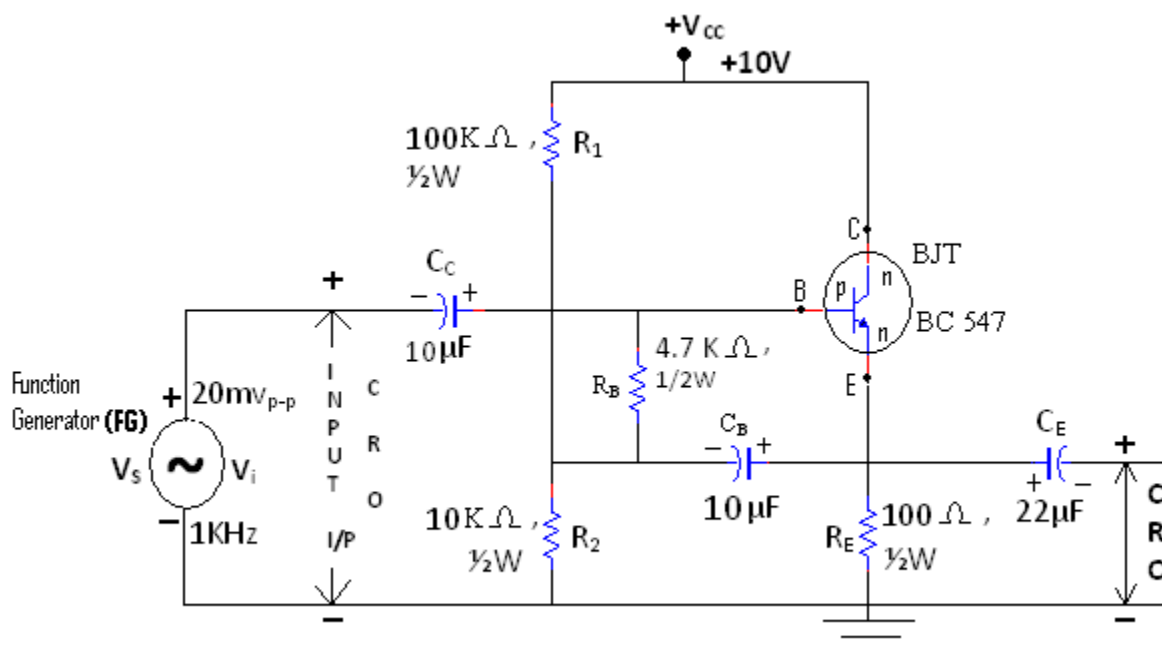
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Bootstrapped Emitter Follower

**PROCEDURE :**

1. We have picked up the components from the components bar as per above circuit.
2. Made the connections as per the above circuit diagram by using the components which we have picked up.
3. Connected the CRO across the Emitter capacitor to ground.
4. Set the input signal as *sine wave form which is having the value 20mV<sub>P-P</sub>* as constant in the function generator.
5. Initially set the input signal frequency value is 1KHz in the function generator.
6. To simulate the circuit clicked on *run option* through *execute button* in *tool bar*.
7. We have seen the *sine wave* on the **CRO** screen as o/p signal.
8. Calculated the *peak to peak voltage ( $V_{O(p-p)}$ )* and noted down in the tabular form Against the column of 1KHz.
9. Stopped the simulation by clicked on *run option* through *execute button* in the *tool bar*.
10. Repeat the same procedure from points 6 to 9 for the corresponding frequency values by setting in the function generator for the steps of 10Hz, 500Hz, 1KHz, 100KHz, 200KHz, 400KHz, 600KHz, 800KHz, 1MHz, 100MHz, 500MHz. in the function generator.
11. Observed the graph for *frequency Vs amplitude* through the *AC Analysis*.
12. Finally shut down the system safely.
13. We have observed that, the graph which is drawn by manually is same to the graph which is obtained from the *AC Analysis*.
14. Now calculated and noted down the values of *voltage gain ( $A_v$ )* and *gain in dB* to the corresponding values of *output voltage ( $V_o$ )* & *input voltage ( $V_i$ )* by using the formulas given below,  

$$\text{Voltage gain } (A_v) = V_o / V_i \text{ and } \text{Gain in dB} = 20\log_{10}(A_v).$$
15. Plotted the graphs (frequency response curves) as per below
  - a). frequency on X-axis & gain in dB on Y-axis.
  - b). frequency on X-axis & voltage gain on Y-axis.

*Note:* Bootstrap Emitter Follower uses to increase the input impedance and to work as correct *Buffer*. For example, The voltage gain of *voltage series feedback amplifier* is 1 it means the output voltage is equal to input voltage, then we can say that it is the correct *Buffer*. Now If you observed the output of *voltage series feedback amplifier* the output voltage is less as compared to input voltage, it means buffer is incorrect. To increase the output voltage which is equal to the input voltage here we have used the *Bootstrapped Emitter Follower*.

**TABULAR FORM :**

Sl.No.	Input Voltage( $V_i$ ) In milli Volts (peak to peak)	Frequency In Hz/KHz.	Output Voltage( $V_o$ ) In mVolts.	Voltage gain $A_v = V_o/V_i$	Gain in dB = $20\log_{10}(A_v)$
01	20mV	10 Hz.			
02	20mV	500 Hz.			
03	20mV	1 KHz.			
04	20mV	100 KHz.			
05	20mV	200 KHz.			
06	20mV	400 KHz.			
07	20mV	600 KHz.			
08	20mV	800 KHz.			
09	20mV	1 MHz.			
10	20mV	100 MHz			
11	20mV	500 MHz.			

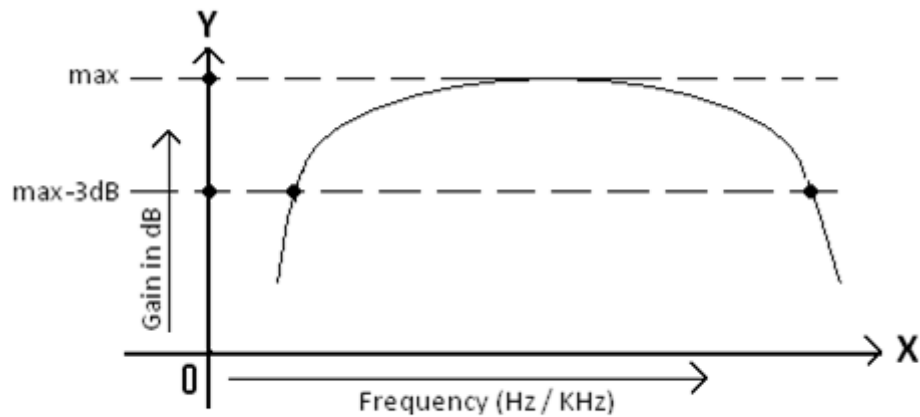
**EXPECTED GRAPH :**

Figure: Frequency response curve of Bootstrapped Emitter Follower.  
For Frequency verses gain in dB.

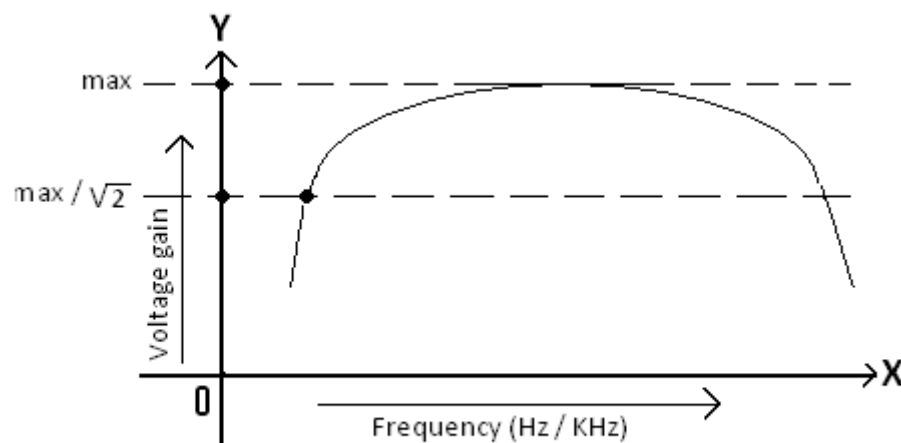


Figure: Frequency response curve of Bootstrapped Emitter Follower.  
For frequency verses voltage gain

*Note :* It is not possible to find the band width because there is no amplification in this amplifier. It is just working as *buffer*.

**RESULT :**

We have obtained the gain of *Bootstrapped Emitter Follower* for different frequencies .

**VIVA VOICE QUESTIONS:**

1. What is Bootstrap Emitter Follower?
  
  
  
  
  
  
  
  
  
  
2. Mention the applications of Bootstrap Emitter follower?
  
  
  
  
  
  
  
  
  
  
3. Which one is Emitter follower? ( CE / CB / CC )
  
  
  
  
  
  
  
  
  
  
4. What are the CC Amplifier characteristics
  
  
  
  
  
  
  
  
  
  
5. What are the Applications of Multi stage amplifiers?

Experiment No. : 03

Date :

Name of the Experiment : **DARLINGTON PAIR AMPLIFIER**  
(Using Simulation software)

**AIM :**

To obtain the frequency response curve of *Darlington pair amplifier* using simulation software

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

**THEORY :**

Darlington Pair amplifier circuit is a connection of two transistors which acts as a single unit with overall current gain equal to the multiplication of the individual current gains of the transistors. Darlington pair **transistor amplifier circuit** is very popular in electronics. Clearly, it is an **Amplifier circuit**. In this article, we are going to discuss the theory and the applications of Darlington pair amplifier.

The current gain of Darlington pair amplifier is almost equal to the product between the current gains of individual transistors. If  $\beta_1$  and  $\beta_2$  be the current gains of individual transistors then overall current gain of Darlington pair amplifier =  $\beta_1\beta_2$ .

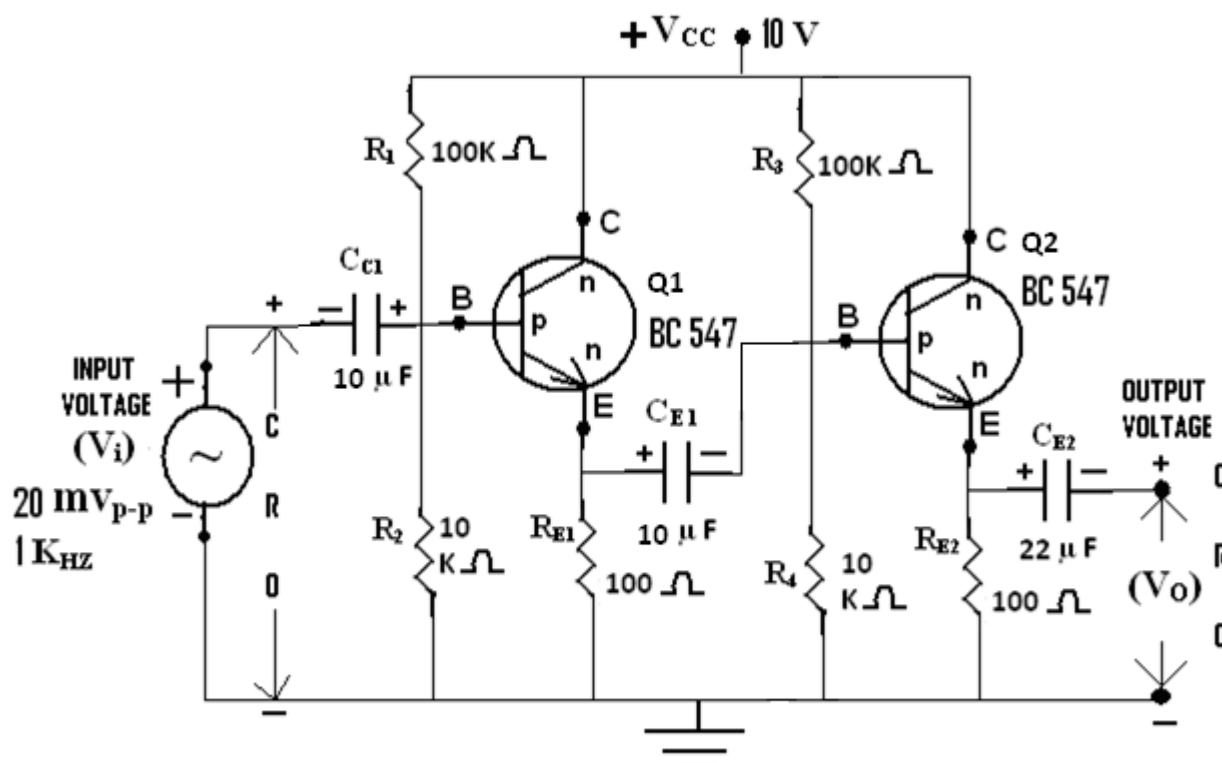
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Darlington pair amplifier.

**PROCEDURE :**


1. We have picked up the components from the components bar as per above circuit.
2. Made the connections as per the above circuit diagram by using the components which we have picked up.
3. Connected the CRO across the capacitor  $C_{E2}$  of second stage.
4. Set the input signal as *sine wave form which is having the value*  $20\text{mV}_{\text{P-P}}$  as constant in the function generator.
5. Initially set the input signal frequency value is 1KHz in the function generator.
6. To simulate the circuit clicked on *run option* through *execute button* in *tool bar*.
7. We have seen the *sine wave* on the **CRO** screen as o/p signal.
8. Calculated the *peak to peak voltage* ( $V_{O(p-p)}$ ) and noted down in the tabular form Against the column of 1KHz.
9. Stopped the simulation by clicked on *run option* through *execute button* in the *tool bar*.
10. Repeat the same procedure from points 6 to 9 for the corresponding frequency values by setting in the function generator for the following steps,  
10Hz, 500Hz, 1KHz, 100KHz, 200KHz, 400KHz, 600KHz, 800KHz, 1MHz, 100MHz, 500MHz. in the function generator.
11. Observed the graph for *frequency Vs amplitude* through the *AC Analysis*.
12. Finally shut down the system safely.
13. We have observed that, the graph which is drawn by manually is same to the graph which is obtained from the *AC Analysis*.
14. Now calculated and noted down the values of *voltage gain* ( $A_V$ ) and *gain in dB* to the corresponding values of *output voltage* ( $V_O$ ) & *input voltage* ( $V_i$ ) by using the formulas given below,  
$$\text{Voltage gain } (A_V) = V_o / V_i \text{ and } \text{Gain in dB} = 20\log_{10}(A_V).$$
15. Plotted the graph between *frequency on X- axis* and *gain in dB on Y- axis*.

**TABULAR FORM:**

Sl.No.	Input Voltage( $V_i$ ) In milli Volts (peak to peak)	Frequency In Hz/KHz.	Output Voltage( $V_o$ ) In mVolts.	Voltage gain $A_V = V_o/V_i$	Gain in dB = $20\log_{10}(A_V)$
1	20mV	10 Hz.			
2	20mV	500 Hz.			
3	20mV	1 KHz.			
4	20mV	100 KHz.			
5	20mV	200 KHz.			
6	20mV	400 KHz.			
7	20mV	600 KHz.			
8	20mV	800 KHz.			
9	20mV	1 MHz.			
10	20mV	100 MHz			
11	20mV	500 MHz.			

**EXPECTED GRAPH :**

The following graph shows for frequency response curve of a *Darlington pair Amplifier*.

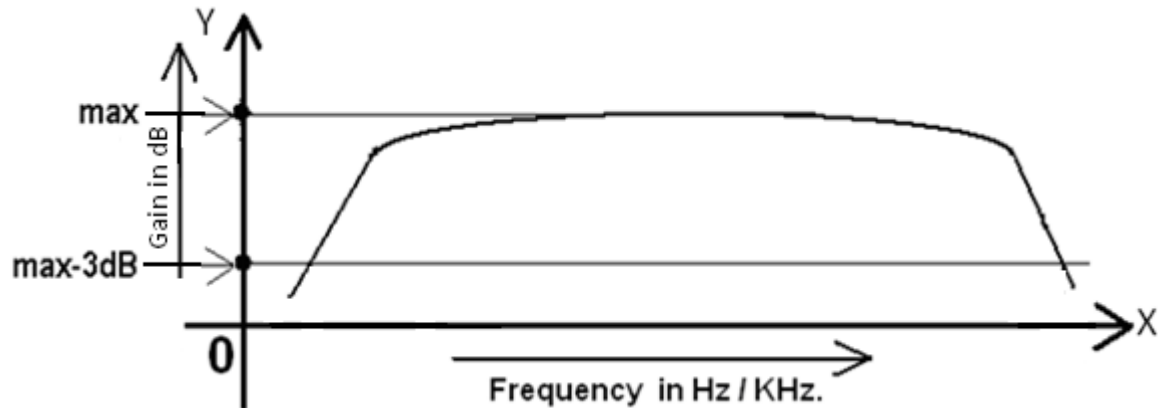**CONCLUSSION :**

We have formed the circuit of Darlington pair amplifier by connected two common collector amplifiers in two stages. The input impedance of two stage common collector amplifier i.e. Darlington pair amplifier is very high as compared to single stage common collector amplifier. Due to this reason only the voltage gain of Darlington pair amplifier is less than as compared to single stage common collector amplifier.

**RESULT :**

I have drawn the frequency response curve of a *Darlington pair amplifier*.

**VIVA VOICE QUESTIONS:**

1. Applications of Darlington pair Amplifier.
2. Applications of Multi stage amplifiers?
3. Mention Advantages of Multistage Amplifiers.
4. What is Band Width?
5. What is Frequency Response?
6. Compare CB,CE, CC configurations of a transistor
7. Explain the transistor operation with the help of four regions
8. What is cascade Amplifier?
9. Explain base width modulation of a transistor
10. Which Amplifier is having CC-CC configuration?



**Experiment No. : 04****Date :****Name of the Experiment : TWO STAGE RC COUPLED AMPLIFIER  
(Using Simulation software)****AIM :**

To verify / plot the frequency response curve *and* to find the band width of a *single stage & two stage RC coupled Amplifier* using Multisim software.

98\*/74

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

**THEORY :**

RC coupling is the most widely used method of coupling in multistage amplifiers. ... In this case the resistance R is the resistor connected at the collector terminal and the capacitor C is connected in between the amplifiers. It is also called a blocking capacitor, since it will block DC voltage.

In RC coupling, a capacitor is used as the coupling device. The capacitor connects the output of one stage to the input of the next stage in order to pass the a.c. signal on while blocking the d.c. bias voltages.

In this way overall voltage gain can be increased, when number of amplifier stage is used in succession, it is called a multistage amplifier. The load of first amplifier is the input resistance of the second amplifier. Thus overall gain is reduced. The output of one stage is connected to the input of next stage through the coupling capacitor. It increases the overall gain of the amplifier and decreases the overall bandwidth of the amplifier.

The applications are : Optical Fiber Communications. Public address systems as pre-amplifiers. Controllers. Radio or TV Receivers as small signal amplifiers.

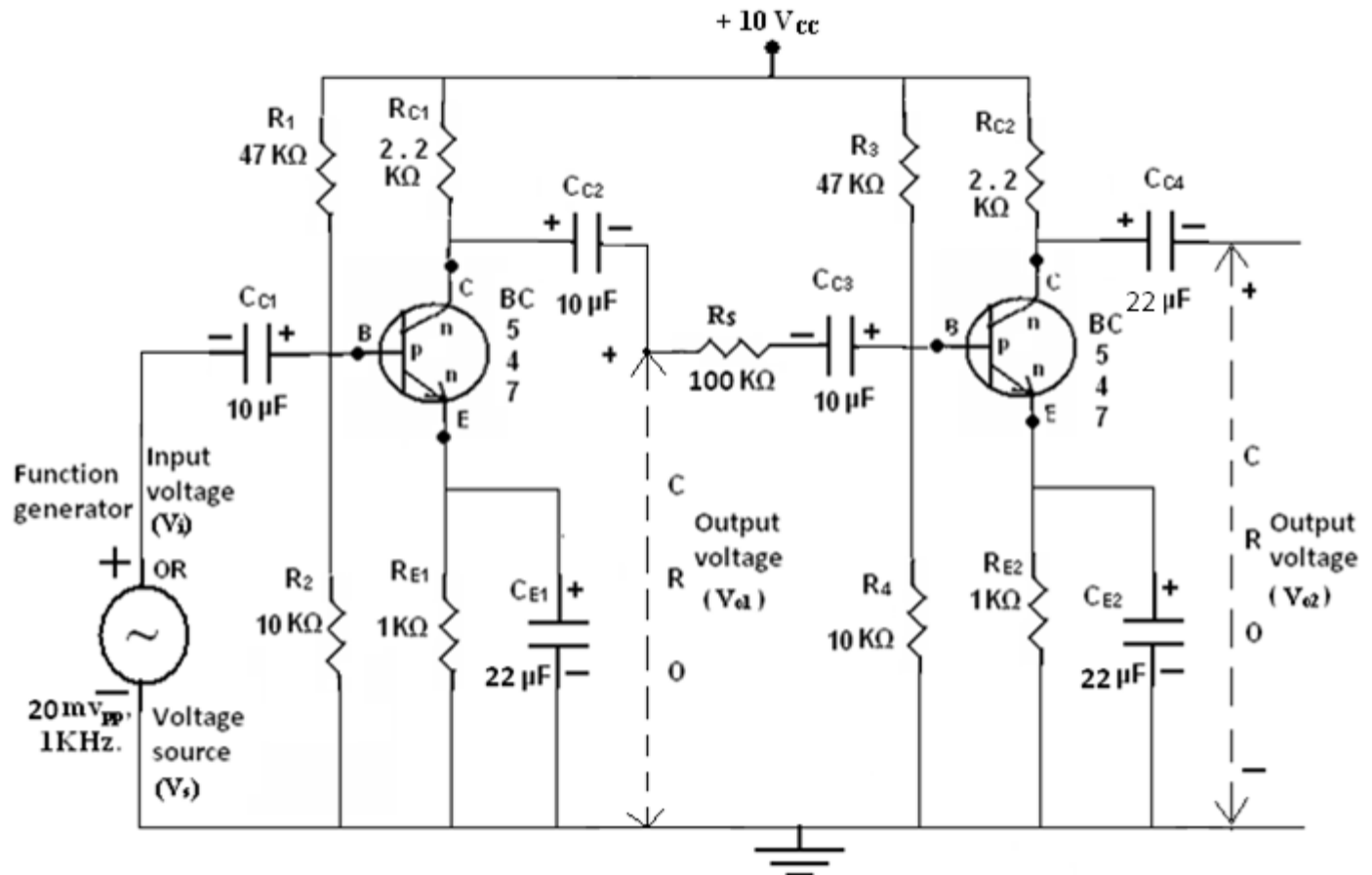
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Two stage RC coupled amplifier.

**PROCEDURE :**

1. We have picked up the components from the tool bar as per above circuit in Multisim software.
2. Made the connections only for single stage up to capacitor  $C_{c2}$  as per the above circuit diagram by using the components which have picked up.
3. Connected the CRO across the capacitor  $C_{c2}$ .
4. Set the input signal value as  $20\text{mV}_{\text{P-P}}$ ,  $1\text{KHz}$  in the function generator as constant and  $V_{\text{CC}}$  as  $10\text{V}$ .
5. To simulate the circuit click on execute / run button in tool bar.
6. We have seen the *Sine wave* on the CRO as O/P signal.
7. Noted/ observed the readings for o/p voltage (Peak to Peak) of output signal in CRO by varying the different frequency steps (i.e.  $10\text{Hz}$ ,  $500\text{Hz}$ ,  $1\text{KHz}$ ,  $100\text{KHz}$ ,  $200\text{KHz}$ ,  $400\text{KHz}$ ,  $600\text{KHz}$ ,  $800\text{KHz}$ ,  $1\text{MHz}$ ,  $100\text{MHz}$ ,  $500\text{MHz}$ .) of the input AC signal in function generator.
8. Noted the above readings to the corresponding frequency steps in the tabular form of *Single stage RC Couple Amplifier*.
9. Stop the simulation by click on *Run button* in tool bar.
10. Observed the graph *frequency Vs amplitude* through the AC Analysis for *Single stage RC Coupled Amplifier*.
11. After this made the circuit for *Two stage RC coupled amplifier*.
12. Remove the CRO which has connected across the capacitor  $C_{c2}$  and connected it across the capacitor  $C_{c4}$  of this circuit.
13. Noted the above readings to the corresponding frequency steps in the tabular form of *Two stage RC Couple Amplifier*.

14. Stop the simulation by click on *Run button* in *tool bar*.
15. Observed the graph *frequency Vs amplitude* through the *AC Analysis* for *Two stage RC Coupled Amplifier*.
16. Shut down the system safely.
17. Calculated and noted the Voltage gain by using the formula of  $V_o / V_i$  and Gain in dB by using the formula of  $20\log_{10}(A_v)$  in the tabular form of both *Single stage* and *Two stage RC Coupled* amplifiers.
18. Drawn the graph for which the *frequency* on X-axis and *Gain* in *dB* on Y-axis for both *RC Coupled Amplifier* circuits..
19. We have calculated the bandwidth of both *RC Coupled amplifiers* from that graph as per given formula,  

$$\text{Band width for Single stage RC Coupled Amplifier (BW)} = f_2 - f_1$$

$$\text{Band width for Two stage RC Coupled Amplifier (BW)} = f_4 - f_3$$
20. We have observed that, the graph which is drawn by manually is same to the graph which is obtained from the *AC Analysis* for both *RC coupled amplifiers*.

### TABULAR COLUMN :

#### A). Single stage RC coupled Amplifier :


Sl. No.	Input voltage (V <sub>i</sub> ) in mV	Frequency in Hz / KHz.	Output Voltage (V <sub>o</sub> ) in V	Voltage gain (A <sub>v</sub> ) = V <sub>o</sub> / V <sub>i</sub>	Gain in dB = 20log <sub>10</sub> (A <sub>v</sub> )
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			
10	20	100 MHz			
11	20	500 MHz.			

#### B). Two stage RC coupled Amplifier :


Sl. No.	Input voltage (V <sub>i</sub> ) in mV	Frequency in Hz / KHz.	Output Voltage (V <sub>o</sub> ) in V	Voltage gain (A <sub>v</sub> ) = V <sub>o</sub> / V <sub>i</sub>	Gain in dB = 20log <sub>10</sub> (A <sub>v</sub> )
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			
10	20	100 MHz			
11	20	500 MHz.			

**EXPECTED WAVEFORM :**

I have got the *Sine wave form* on the CRO as output signal for both *RC Coupled Amplifiers* which is Shown below,

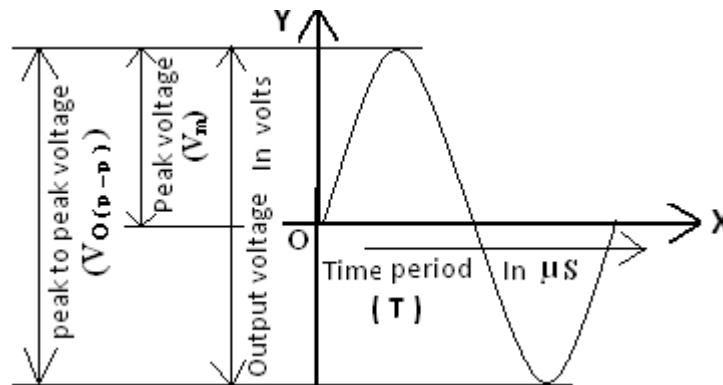**EXPECTED GRAPH :**

The following graph shows the frequency response curves of both *Single stage & Two stage RC coupled Amplifiers*.

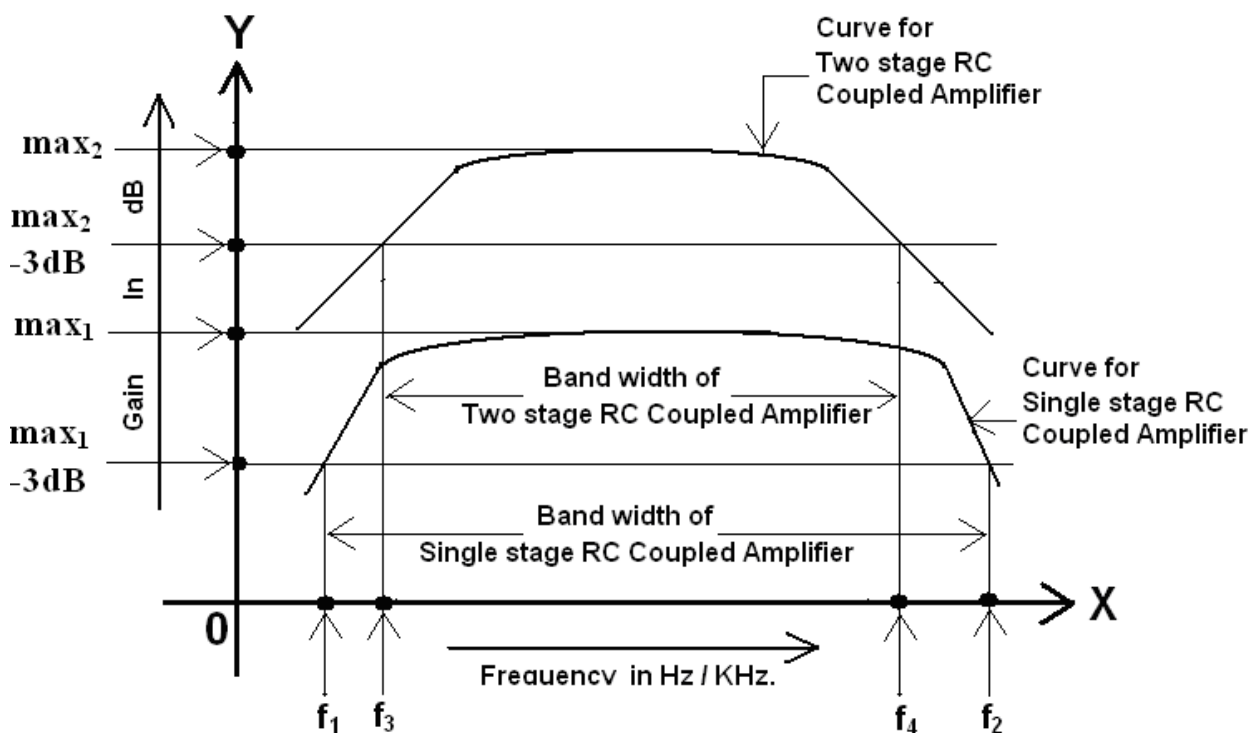**CALCULATIONS :**

- 1). Band width "*single stage RC coupled amplifier*" =  $f_2 - f_1$   
=
- 2). Band width "*two stage RC coupled amplifier*" =  $f_4 - f_3$   
=

**CONCLUSION :**

1. I have observed that
  - a). The bandwidth of *Two stage RC coupled amplifier* is less as compared to *Single stage RC coupled amplifier* and
  - b). The gain of *Two stage RC coupled amplifier* is more as compared to *Single stage RC coupled amplifier*

**RESULT :**

I verified / drawn the frequency response curve and found the bandwidth values of a *single stage & two stage RC coupled amplifiers*. The band width values are,

- 1). Band width of *single stage RC coupled amplifier* =
- 2). Band width of *two stage RC coupled amplifier* =

**VIVA VOICE QUESTIONS:**

1. Need for multi stage amplifier?
2. What are the different coupling schemes?
3. Applications of Multi stage amplifiers?
4. Mention Advantages of Multistage Amplifiers.
5. What is Band Width?
6. What is cascade Amplifier?
7. Compare BJT and FET?
8. What is thermal runaway?
9. What are the advantages of using potential divider bias?
10. What is cascade Amplifier?

Experiment No. : 05

Date :

**Name of the Experiment : CURRENT SHUNT FEEDBACK AMPLIFIER**  
**(Using simulation software)**

**AIM :**

- 1). To plot the graph for frequency response curve of a *Current shunt feedback Amplifier* for both *with feed back* and *without feedback*.
- 2). To find the bandwidth of *Current shunt feedback Amplifier*.


**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

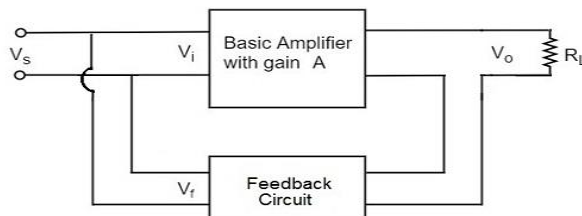**THEORY :**

In the current shunt feedback circuit, a fraction of the output voltage is applied in series with the input voltage through the feedback circuit. This is also known as **series-driven shunt-fed** feedback i.e., a series-parallel circuit.


The below figure shows the block diagram of current shunt feedback, by which it is evident that the feedback circuit is placed in series with the output but in parallel with the input.



As the feedback circuit is connected in series with the output, the output impedance is increased and due to the parallel connection with the input, the input impedance is decreased.

Let us now tabulate the amplifier characteristics that get affected by different types of negative feedbacks.

As the feedback circuit is connected in series with the output, the output impedance is increased and due to the parallel connection with the input, the input impedance is decreased.

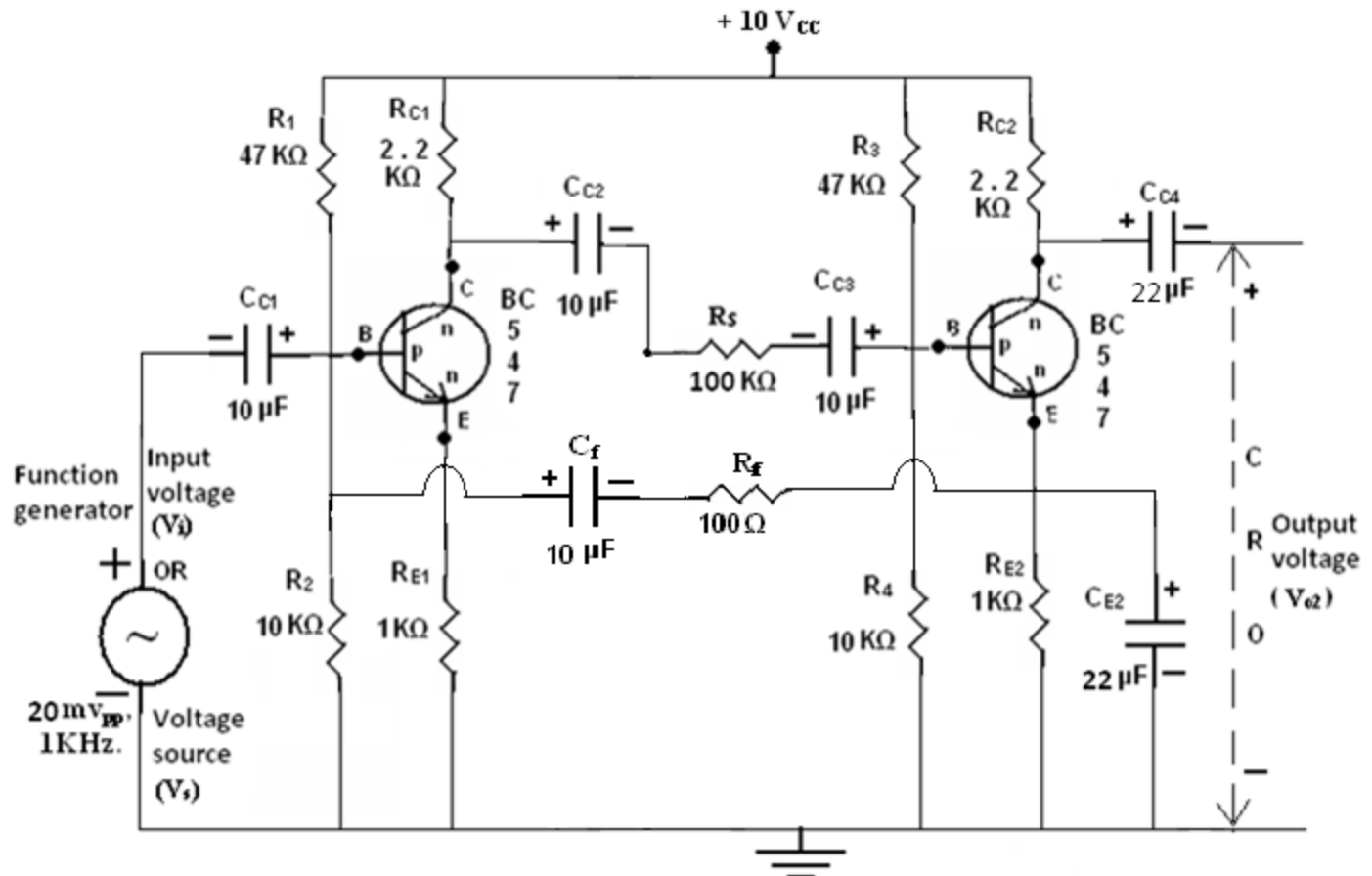**CIRCUIT DIAGRAM :****PROCEDURE :**

1. We have picked up the components from the components bar as per above circuit.
2. Made the connections as per the above circuit diagram by using the components which we have picked up.
3. Connected the CRO across the capacitor  $C_{C4}$ .
4. Set the input signal as *sine wave form* which is having the value  $20\text{mV}_{\text{P-P}}$  as constant in the function generator.
5. Initially set the input signal frequency value is  $1\text{KHz}$  in the function generator.
6. To simulate the circuit clicked on *run option* through *execute button* in *tool bar*.
7. We have seen the *sine wave* on the **CRO** screen as o/p signal.
8. Calculated the *peak to peak voltage* ( $V_{O(p-p)}$ ) and noted down in the column of  $1\text{KHz}$ . For tabular form of *with feedback* amplifier.
9. Stopped the simulation by clicked on *run option* through *execute button* in the *tool bar*.
10. Repeat the same procedure from points 6 to 9 for the corresponding frequency values by setting in the function generator for the following steps,  
 $10\text{Hz}$ ,  $500\text{Hz}$ ,  $1\text{KHz}$ ,  $100\text{KHz}$ ,  $200\text{KHz}$ ,  $400\text{KHz}$ ,  $600\text{KHz}$ ,  $800\text{KHz}$ ,  $1\text{MHz}$ ,  $100\text{MHz}$ ,  $500\text{MHz}$  in the function generator.
11. Observed the graph for *frequency Vs amplitude* through the *AC Analysis*.
12. Disconnected the  $C_f$  and  $R_f$  from the circuit and now the circuit has become as *without feedback amplifier*
13. Now taken the reading in the tabular form of *without feedback amplifier* by repeat the steps from 6 to 11
14. Finally shut down the system safely.



15. We have observed that, the graph which is drawn by manually is same to the graph which is obtained from the *AC Analysis*.
16. We have observed that the readings of *without feed back amplifier's* output voltage is greater than the *with feed back amplifier*
17. Calculated the Voltage gain by using the formula of  $V_o / V_i$  and Gain in dB by using the formula of  $20\log_{10}(A_v)$  in both tabular forms of *with feed back* and *without feed back amplifiers*.
18. Drawn the graphs of both amplifiers in single graph sheet.
19. While drawing the graph taken the *frequency* on X-axis and *Gain in dB* on Y-axis.
20. Finally calculated the *bandwidth* of both amplifiers from this graph sheet as per the following formulas,
  - i). For *Current shunt feed back amplifier (With feed back)*  $(BW) = f_2 - f_1$
  - ii). For *Current shunt feed back amplifier (Without feed back)*  $(BW) = f_4 - f_3$
21. We have noted down that the *band width* of *with feed back amplifier* is high compared to the *without feed back amplifier*.

### TABULAR COLUMN :

#### A). With feed back :


Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in mV	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			
10	20	100 MHz			
11	20	500 MHz.			

#### B). Without feed back :

Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in mV	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			
10	20	100 MHz			
11	20	500 MHz.			

**EXPECTED GRAPH :**

The following graph shows for *Current shunt feed back amplifier* for both *with feed back* and *without Feedback amplifier*.

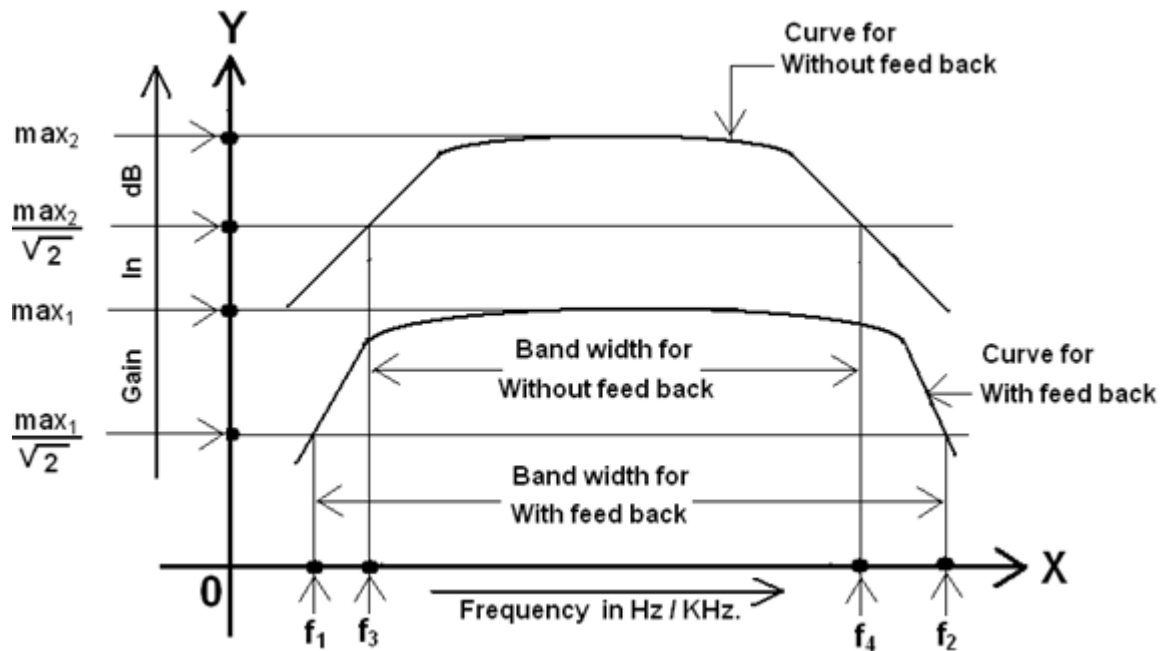**RESULT :**

We drawn the graph for frequency response of a *Current shunt feed back amplifier* for both *with feed back* and *without feed back*.

**VIVA VOICE QUESTIONS:**

1. What is feedback?
2. What are the input and output impedances for current shunt feedback Amplifier.
3. Applications of current shunt feedback Amplifier.
4. What are the feedback topologies?
5. CC Amplifier characteristics?
6. What is Band Width?
7. What is Frequency Response?
8. Explain the transistor operation with the help of four regions



**Experiment No. : 06****Date :****Name of the Experiment : SINGLE TUNED VOLTAGE AMPLIFIER  
(Using simulation software)****AIM :**

To obtain the frequency response curve of *Single tuned voltage amplifier*.

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

**THEORY :**

Tuned amplifiers are mainly preferred to amplify the high-frequency signals in wireless communication. The tuned amplification works based on the tuning circuit implied as load. The range of the frequencies defined for a particular amplification circuit can be fixed or dynamic based on applications. The tuning circuit present at the load consists of an inductor and capacitor. For dynamic frequencies, the values of capacitance should be varied. These amplifiers are very advantageous due to its appealing large bandwidths. The increment in bandwidth is based on the number of tuning circuits present at the load. There are three types of most frequently used tuned amplifiers they are single tuned amplifier, double-tuned amplifier and stagger tuned amplifier.

**Definition:** A tuned amplifier consists of a single tuning circuit at the load can be defined as a single tuned amplifier. It is a multi-stage amplifier, where each stage of this amplifier must be tuned with the same frequencies. For example, tuning a radio station. If the desired carrier wave is passed and matches the defined range of passband frequency, then the radio station is tuned otherwise it is blocked.

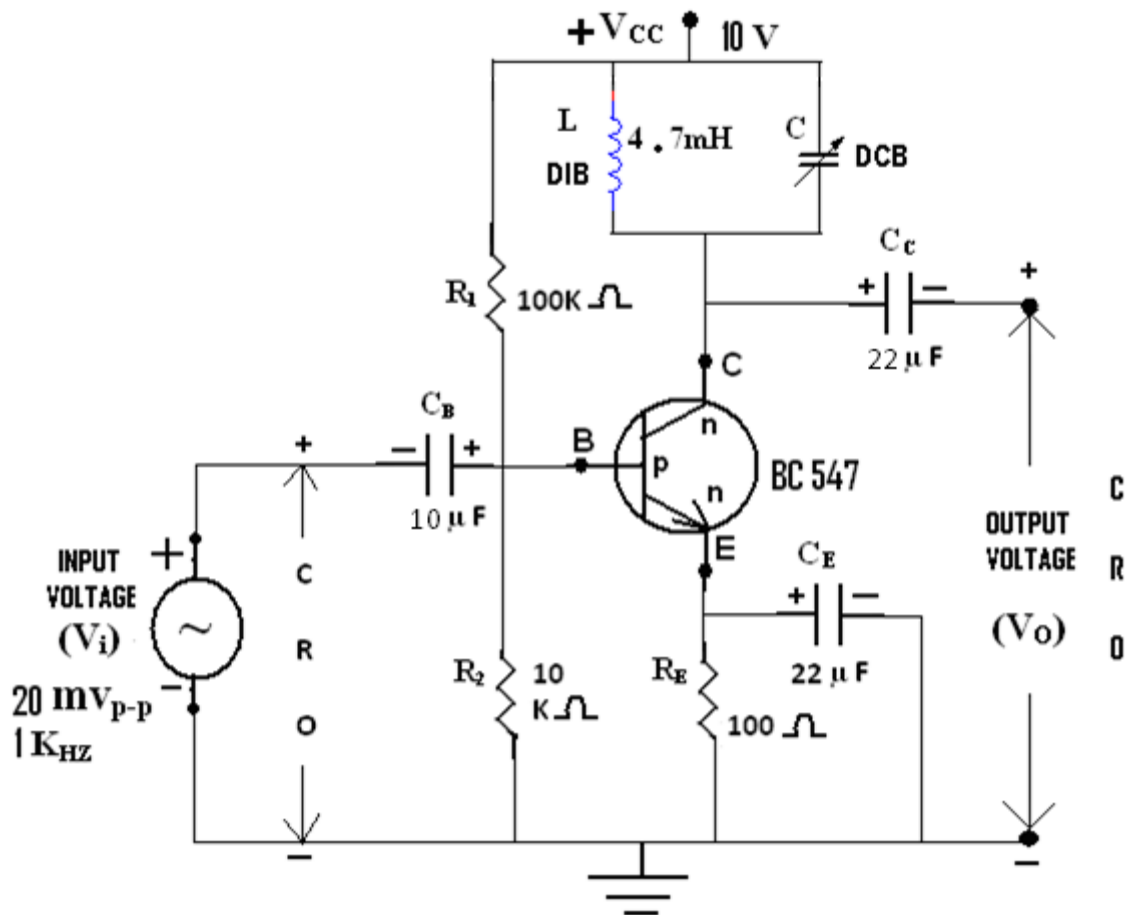
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of single tuned voltage amplifier.

**THEORETICAL CALCULATIONS :**1). When  $L=4.7\text{mH}$ ,  $f_r=10\text{KHz}$ , Then  $C=?$ 

$$\text{We have } f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{OR } C = \frac{1}{[2\pi f_r \sqrt{L}]^2}$$

$$\text{OR } C = \frac{1}{4\pi^2} \times \frac{1}{f_r^2 L} \quad \text{OR } C = \frac{0.0253}{f_r^2 L}$$

$$C = \frac{0.0253}{[10 \times 10^3]^2 \times 4.7 \times 10^{-3}}$$

$$= 54\text{Kpf OR } 54\text{ nF}$$

2). When  $L=4.7\text{mH}$ ,  $f_r=50\text{KHz}$ , Then  $C=?$ 

$$\text{We have } C = \frac{0.0253}{f_r^2 L}$$

$$= \frac{0.0253}{[50 \times 10^3]^2 \times 4.7 \times 10^{-3}}$$

$$= 2.16\text{Kpf OR } 2.16\text{ nF}$$

**PROCEDURE :**

1. We have picked up the components from the components bar as per above circuit.
2. Made the connections as per the above circuit diagram by using the components which we have picked up.
3. Connected the CRO across the *Collector capacitor to ground..*
4. Now set the  $C=54\text{Kpf}$  and  $L=4.7\text{mH}$  to take readings in tabular form-1
5. Set the input signal as *sine wave form which is having the value  $20\text{mV}_{\text{P-P}}$*  as constant in the function Generator until the experiment would completed.
6. To simulate the circuit clicked on *run option* through *execute button* in *tool bar*.
7. We could seen the *sine wave* on the screen of *CRO* as o/p signal.
8. Initially varied the frequency of input signal until the maximum output voltage could obtained, and noted this to the corresponding frequency value in the tabular form -1 .
9. Later calculated and noted the peak to peak output voltage to the corresponding frequency values which are available in the tabular form-1.
10. Stopped the simulation by clicked on *run option* through *execute button* in the *tool bar*.
11. Observed the graph for *frequency Vs amplitude* through the *AC Analysis*.
12. Now set  $C=2.16\text{Kpf}$  and  $L=4.7\text{mH}$  to take readings in tabular form-2.
13. Repeat the same procedure from points 6 to 11 for the corresponding frequency values which are available in the tabular form
14. Finally shut down the system safely.
15. Now calculated and noted down the values of *voltage gain* ( $A_v$ ) and *gain in dB* to the corresponding values of *output voltage* ( $V_o$ ) & *input voltage* ( $V_i$ ) by using the formulas given below,  

$$\text{Voltage gain } (A_v) = V_o / V_i \text{ and } \text{Gain in dB} = 20\log_{10}(A_v).$$
 These values has been noted in the both tabular forms.
16. Plotted the graphs for both tabular forms (frequency response curves) as per given below,
  - a). frequency on X-axis & gain in dB on Y-axis.
  - b). frequency on X-axis & voltage gain on Y-axis.
17. Calculated and noted the *band width* & *resonant frequency* from both frequency response curves by using the following formula,  

$$\text{Band width} = f_2 - f_1.$$
18. We have observed that, the graph which is drawn by manually is same to the graph which is obtained from the *AC Analysis*.

**TABULAR FORM – 1:**

When  $f_r = 10\text{KHz}$ ,  $C = 54\text{Kpf}$ ,  $L = 4.7\text{mH}$

Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in V	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	5 KHz.			
5	20				
6	20	20KHz.			
7	20	50KHz.			
8	20	100 KHz.			
9	20	200 KHz.			
10	20	500 KHz.			
11	20	1 MHz.			
12	20	100 MHz			
13	20	500 MHz.			

**TABULAR FORM – 2 :**

When  $f_r = 50\text{KHz}$  ,  $C = 2.16\text{Kpf}$  ,  $L = 4.7\text{mH}$



Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in V	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	20KHz.			
5	20				
6	20	60KHz.			
7	20	100 KHz.			
8	20	200 KHz.			
9	20	500 KHz.			
11	20	1 MHz.			
12	20	100 MHz.			
13	20	500 MHz.			

**EXPECTED GRAPH :**

The following graphs shows the frequency response curve for *single tuned voltage amplifie*

A). When  $f_r = 10\text{ KHz}$  ,  $C = 54\text{ Kpf}$  ,  $L = 4.7\text{mH}$

B). When  $f_r = 50\text{ KHz}$  ,  $C = 2.16\text{ Kpf}$  ,  $L = 4.7\text{mH}$

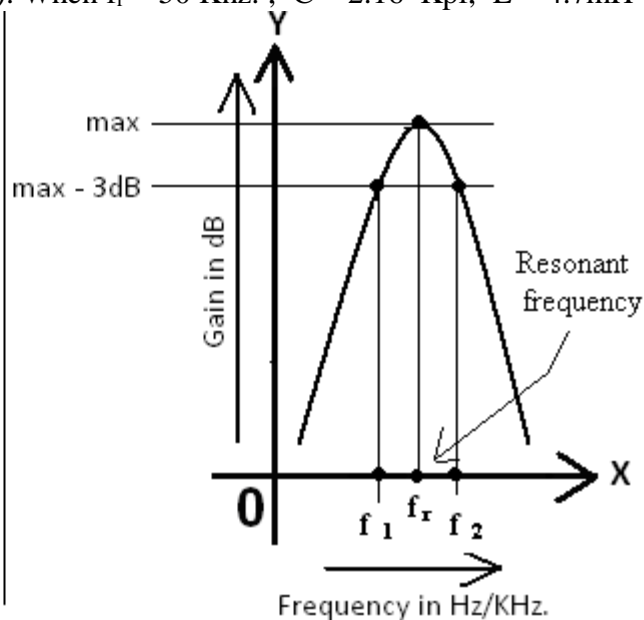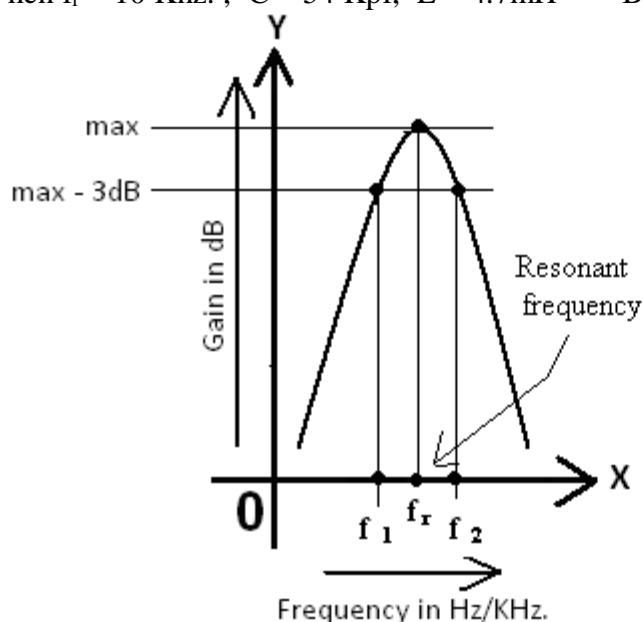**PRACTICAL CALCULATIONS :**

When $f_r = 10\text{ KHz}$ , $C = 54\text{ Kpf}$ , $L = 4.7\text{mH}$	When $f_r = 50\text{ KHz}$ , $C = 2.16\text{ Kpf}$ , $L = 4.7\text{mH}$
1). Band width = $f_2 - f_1$ =	1). Band width = $f_2 - f_1$ =
2). Resonant frequency ( $f_r$ ) =	2). Resonant frequency ( $f_r$ ) =



**TABULAR FORM -3 :**

The following tabular form shows the comparison between the theoretical and practical resonant frequency values.

Sl.No.	Inductor (L) (Note down from the theoretical calculations)	Capacitor (C) (Note down from the theoretical calculations)	Theoretical Resonant frequency ( $f_r$ ) (Note down from the theoretical calculations)	Practical Resonant frequency ( $f_r$ ) (Note down from the graph)	Max. voltage gain in dB at resonant frequency . (Note down from the graph)
1.	4.7mH	54Kpf	10KHz.		
2.	4.7mH	2.16Kpf	50KHz.		

**CONCLUSSION :**

If I observed in the tabular form-3 the voltage gain of the output signal is maximum when the practical resonant frequency value is approximately equal to the theoretical resonant frequency value.

**APPLICATIONS :**

Mainly uses in the radio receivers to tuned the appropriate signal / station which is transmitted in relay station.

**RESULT :** I have drawn the frequency response curve and calculated the values of band width, and resonant frequency of a *single tuned voltage amplifier*.

**VIVA VOICE Questions:**

1. What is single Tuned Amplifier?
2. What is Q factor?
3. What is tank circuit?
4. Mention Applications of single Tuned Amplifier.
5. What is the resonant frequency of single tuned Amplifier?
6. Tuned Amplifier is Narrow or Wide BW Amplifier?
7. Difference between single tuned and double tuned Amplifier?
8. What is stagger tuned Amplifier?
9. Effect of cascading of single tuned Amplifier on BW?
10. What is frequency response?

**Experiment No. : 07****Date :****Name of the Experiment : CLASS A SERIES - FED POWER AMPLIFIER  
(Using Simulation Software)****AIM :**

1. To verify / plot the output signal (sine wave form) of a given *Class-A Series-fed Power Aamplifier* by using *multisim* software.
2. To calculate the conversion efficiency of a given amplifier by using *multisim* software.

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

**THEORY :**

Class A power amplifier is a type of power amplifier where the output transistor is ON full time and the output current flows for the entire cycle of the input wave form. Class A power amplifier is the simplest of all power amplifier configurations. They have high fidelity and are totally immune to crossover distortion. Even though the class A power amplifier have a handful of good feature, they are not the prime choice because of their poor efficiency. Since the active elements (transistors) are forward biased full time, some current will flow through them even though there is no input signal and this is the main reason for the inefficiency

The theoretical maximum efficiency of a Class A power amplifier is 50%. In practical scenario, with capacitive coupling and inductive loads (loud speakers), the efficiency can come down as low as 25%. This means 75% of power drawn by the amplifier from the supply line is wasted. Majority of the power wasted is lost as heat on the active elements (transistor).As a result, even a moderately powered Class A power amplifier require a large power supply and a large heatsink.

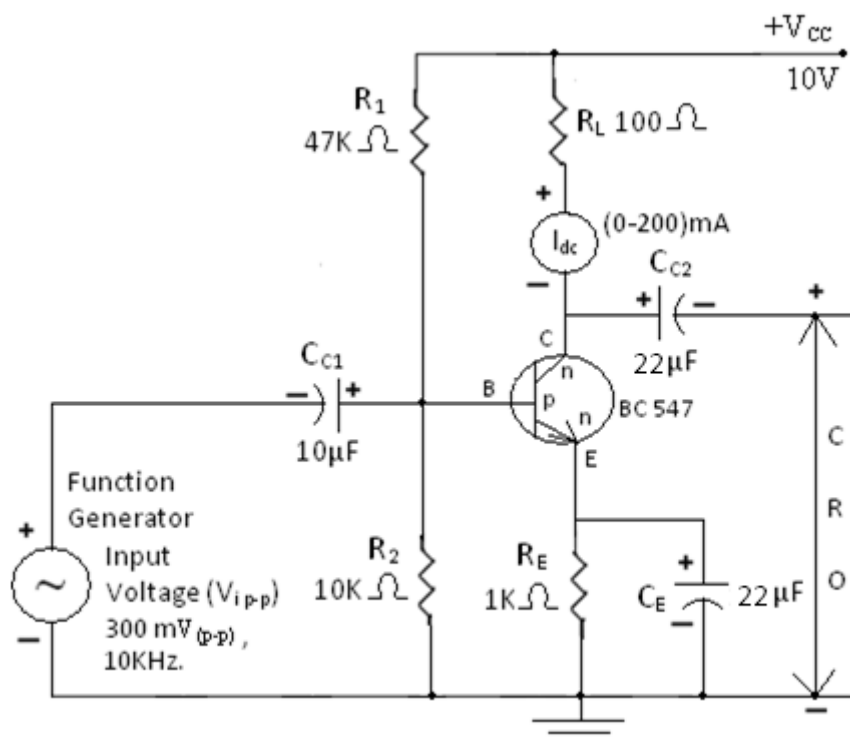
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Class A Series-fed Power Amplifier

**PROCEDURE :**

1. Picked up the components from *components bar* in multisim software as per the circuit diagram.
2. Made the connections as per the circuit diagram.
3. Set the  $300\text{ mV}_{p-p}$  (as input voltage),  $10\text{ KHz}$  (as input frequency) *sine wave* signal to the circuit from the *Function generator*.
4. Noted down the *Input voltage* ( $v_i$ ), *Input frequency* against the corresponding columns of the tabular form of *practical calculations*.
5. Set the *supply voltage*  $20\text{V}$  as  $V_{CC}$  to the circuit as shown in the circuit diagram.
6. To simulate this circuit click on *Run* button in *tool bar*.
7. Observed the *sine wave* signal in *CRO* and drawn this signal on the graph sheet.
8. Calculated the *output voltage* ( $V_{O p-p}$ ), *time period* ( $T$ ), *frequency* ( $f$ ) from the graph, and noted down these values against the corresponding columns in the tabular form of *practical calculations*.
9. Noted down the *supply voltage* ( $V_{CC}$ ) and *collector dc current*  $I_{dc}$  at *Quiescent* condition i.e. when no signal is applied i.e. by disconnected the *function generator* from the circuit against the corresponding columns of the tabular form of *practical calculations*.
10. Stop the simulation by click on *Run* button in *tool bar*.
11. Shut down the system safely.
12. Later calculated and noted the input *dc power*  $P_i(dc)$ , output *ac power*  $P_o(ac)$  and % of *efficiency* ( $\eta$ ) by using the formulas which are mentioned in the corresponding columns of the tabular form of *practical calculations*.
13. Noted that the practical value should be less than the *Typical Max. efficiency value* i.e. **25.4%**.


**PRACTICAL CALCULATIONS :**

The practical calculations for the parameters are shown in the following tabular form.

Sl.No.	Name of the parameter	Value
01.	Input Voltage ( $V_i$ ) <sub>p-p</sub> ( In mV).	300
02	Input frequency (In Khz.).	10
03	Supply DC Voltage ( $V_{CC}$ ) (in Volts.)	10
04	Output voltage $V_{O(p-p)}$ (In volts.).	
05	Time period (T) for output signal (In ms)	
06	Frequency for output signal = $1/T$ (In Khz.)	
07	Collector dc current ( $I_{dc}$ ) (At quiescent condition i.e. When no input signal is applied) (In mA.).	
08	Collector DC current when sine wave (AC) signal is applied as input signal ( $I_{ac}$ )	
09	Input DC power $P_i(dc) = I_{dc} \times V_{CC}$ (In Watts).	
10	Output ac power $P_o(ac) = \frac{V_{O^2(p-p)}}{8R_L}$ (In Watts)	
11	% of efficiency ( $\eta$ ) = $[ P_o(ac) / P_i(dc) ] \times 100 =$	

**EXPECTED WAVEFORM :**

The following waveform shows the output signal of *Class A Series-fed Power Amplifier* .

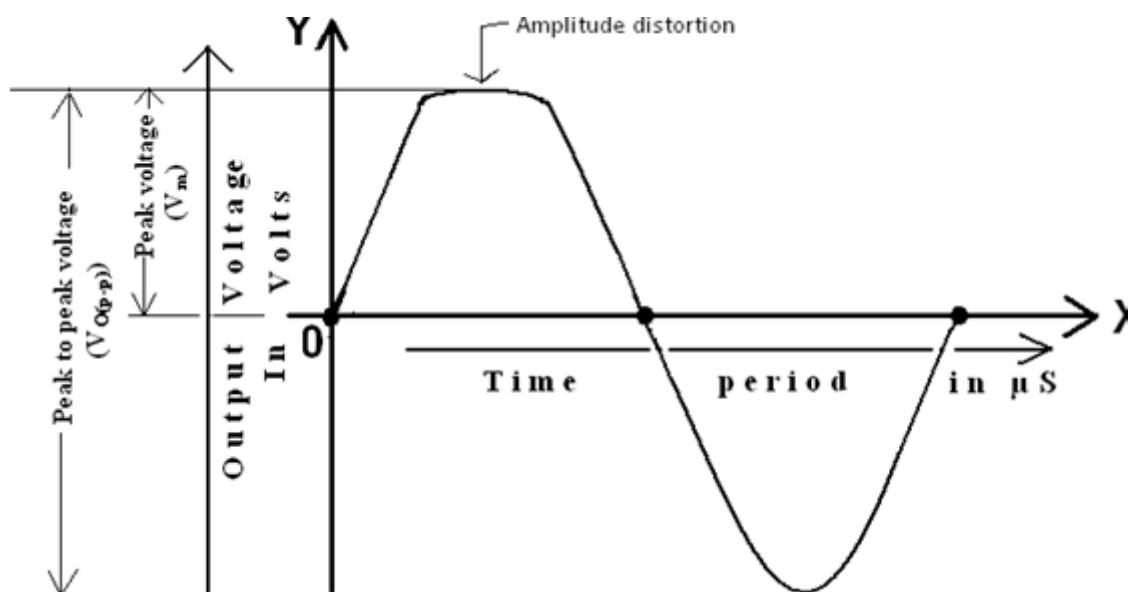**RESULT :**

I have verified / drawn the output signal and calculated the conversion efficiency of given *Class-A Series-fed Power amplifier*.

**VIVA VOICE Questions:**

1. What is Power Amplifier?
2. Classifications of power Amplifiers.
3. Efficiency of class A power Amplifier.
4. Difference between Direct coupled and Transformer coupled class A power Amplifier?
5. What is the amplitude (Harmonic) Distortion?
6. Where is the Q point in class A power Amplifier?
7. Applications of class A power Amplifier.
8. What are the disadvantages of class A power Amplifier.
9. Mention the conduction angle of class A power Amplifier.
10. What are the disadvantages of class A power Amplifier.

**Experiment No. : 08****Date :****Name of the Experiment : COMPLEMENTARY SYMMETRY CLASS B PUSH-PULL  
POWER AMPLIFIER (Using Simulation Software)****AIM :**

1. To verify / plot the output signal (sine wave form) of a given *Complementary symmetry Class-B push-pull Power Amplifier* by using *multisim* software.
2. To calculate the conversion efficiency of given *Complementary symmetry Class-B push-pull Power Amplifier* by using *multisim* software.

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software

**THEORY :**

Class B amplifier is a type of power amplifier where the active device (transistor) conducts only for one half cycle of the input signal. That means the conduction angle is  $190^\circ$  for a Class B amplifier. Since the active device is switched off for half the input cycle, the active device dissipates less power and hence the efficiency is improved. Theoretical maximum efficiency of Class B power amplifier is 78.5%.

Class-B or Push-pull amplifiers use two “complementary” or matching transistors, one being an NPN-type and the other being a PNP-type with both power transistors receiving the same input signal together that is equal in magnitude, but in opposite phase to each other. This results in one transistor only amplifying one half or  $190^\circ$  of the input waveform cycle while the other transistor amplifies the other half or remaining  $190^\circ$  of the input waveform cycle with the resulting “two-halves” being put back together again at the output terminal. Then the conduction angle for this type of amplifier circuit is only  $190^\circ$  or 50% of the input signal. This pushing and pulling effect of the alternating half cycles by the transistors gives this type of circuit its amusing “push-pull” name, but are more generally known as the **Class B Amplifier**


**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Class-B complimentary symmetry power amplifier.

**PRACTICAL CALCULATIONS :**

The practical calculations for the parameters are shown in the following tabular form,

SINo.	Name of the parameter	Value
01.	Input peak to peak voltage ( $V_i$ ) ( In Volts).	4
02	Input frequency (In Khz.).	10
03	Positive supply DC Voltage ( $+V_{CC}$ ) (in Volts.)	10
04	Negative supply DC Voltage ( $-V_{CC}$ ) (in Volts.)	10
04	Peak to peak voltage of output $V_{O(p-p)}$ (In volts.).	
05	Peak voltage of output ( $V_m$ ) = $V_{O(p-p)} / 2$ (In volts.).	
06	Time period (T) for output signal (In ms)	
07	Fequency for output signal = $1/T$ (In Khz.)	
08	Collector dc current ( $I_{dc}$ ) (At quesient condition i.e. When no input signal is applied) (In mA.).	
09	Collector DC current when sine wave (AC) signal is applied as input signal ( $I_{ac}$ )	
10	Input DC power $P_i(dc) = I_{dc} \times V_{CC}$ (In mWatts).	
11	Output ac power $P_o(ac) = \frac{V_m^2}{2R_L}$ (In mWatts) =	
12	% of efficiency ( $\eta$ ) = $\frac{P_o(ac)}{P_i(dc)} \times 100$	
13	Typical Max. efficiency ( $\eta$ ) =	78.50 %

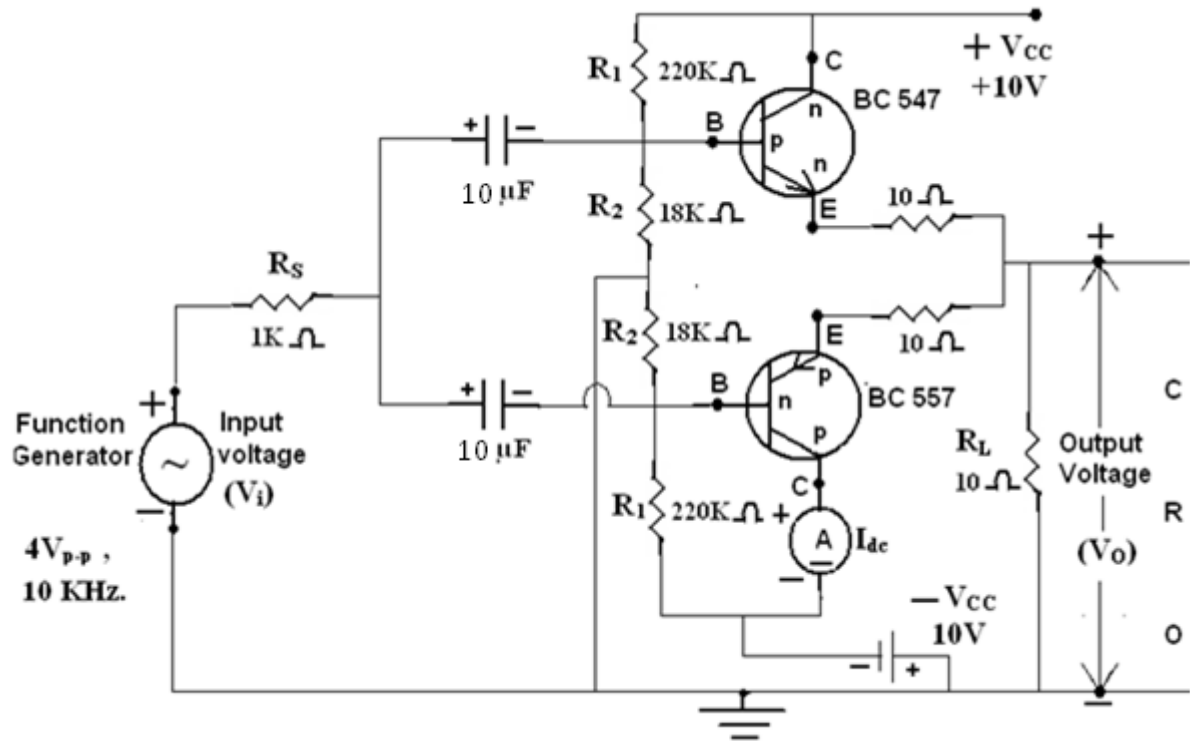


**PROCEDURE :**

1. Picked up the components from *components bar* in multisim software as per the circuit diagram.
2. Made the connections as per the circuit diagram.
3. Set the 4  $V_{p-p}$  (as input voltage) , 10 KHz (as input frequency) *sine wave* signal to the circuit from the *Function generator*.
4. Noted down the *Input voltage*( $V_i$ ) , *Input frequency* against the corresponding columns of the tabular form of *practical calculations*.
5. Set the *supply voltage* 20V as  $V_{CC}$  to the circuit as shown in the circuit..
6. To simulate this circuit click on *Run* button in *tool bar*.
7. Observed the *sine wave* signal in CRO<sub>2</sub> and drawn this signal on the graph sheet.
8. Calculated the *output voltage* ( $V_{o-p-p}$ ) , *time period* ( $T$ ), *frequency* ( $f$ ) from the graph, and noted down these values against the corresponding columns of the tabular form of *practical calculations*.
9. Noted down the *supply voltage* ( $V_{CC}$ ) and *collector dc current*  $I_{dc}$  at *Quiescent* condition i.e. when no signal is applied i.e. by disconnected the *function generator* from the circuit against the corresponding columns of the tabular form of *practical calculations*.
10. Stop the simulation by click on *Run* button in *tool bar*.
11. Shut down the system safely.
12. Later calculated and noted the *Input dc power*  $P_i(dc)$ , *output ac power*  $P_o(ac)$  and % of *efficiency* ( $\eta$ ) by using the formulas which are mentioned in the corresponding columns of the tabular form of *practical calculations*.
13. Noted that The practical value should be less than the *Typical Max. efficiency value i.e. 78.5%*.

**Note:** During the execution I have waited for 15 minutes of time until we get the maximum peak to peak amplitude. The max. peak to peak value is  $\leq 0.84V$

**EXPECTED WAVEFORM :**

The following waveform shows the output signal for *complementary symmetry Class B push-pull power amplifier*.

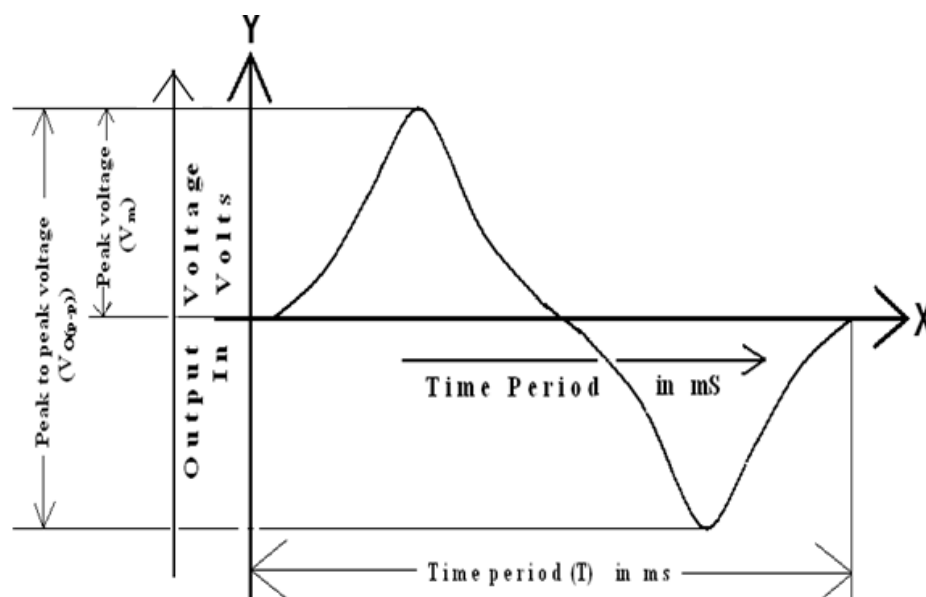**RESULT :**

I have verified / drawn the output waveform and calculated the conversion efficiency of given *Complementary symmetry Class-B push-pull Power Amplifier*.

**VIVA VOICE Questions:**

1. What is Power Amplifier?
2. Classifications of power Amplifiers.
3. Efficiency of class B power Amplifier.
4. Difference between Transformer coupled and Complementary symmetry class B power Amplifier?
5. What is the Crossover Distortion?
6. Where is the Q point in class B power Amplifier?
7. Applications of class B power Amplifier.
8. What are the disadvantages of class B power Amplifier.
9. Mention the conduction angle of class B power Amplifier.
10. What are the disadvantages of class B power Amplifier.

Experiment No. : 09

Date :

### Name of the Experiment : RC PHASE SHIFT OSCILLATOR (Using Simulation Software)

#### AIM :

To verify the *sine wave form* and to calculate its frequency values of a given *RC Phase shift Oscillator* by using multisim software.

#### APPARATUS :

1. System ----- 1 No.
2. Multisim software.

#### THEORY :

A phase shift oscillator can be defined as; it is one kind of linear oscillator which is used to generate a sine wave output. It comprises of an inverting amplifier component like operational amplifier otherwise a transistor. The output of this amplifier can be given as input with the help of the phase shifting network. This network can be built with resistors as well as capacitors in the form of a ladder network. The phase of the amplifier can be shifted to 180° at the oscillation frequency by using a feedback network to provide a positive response. These types of oscillators are frequently used as audio oscillators on audio frequency. This article discusses an overview of RC phase shift oscillator.

RC phase-shift oscillator circuit can be built with a resistor as well as a capacitor. This circuit offers the required phase shift with the feedback signal. They have outstanding frequency strength and can give a clean sine wave for an extensive range of loads. Preferably an easy RC network can be expected to include an o/p which directs the input with 90°.

#### CIRCUIT DIAGRAM :

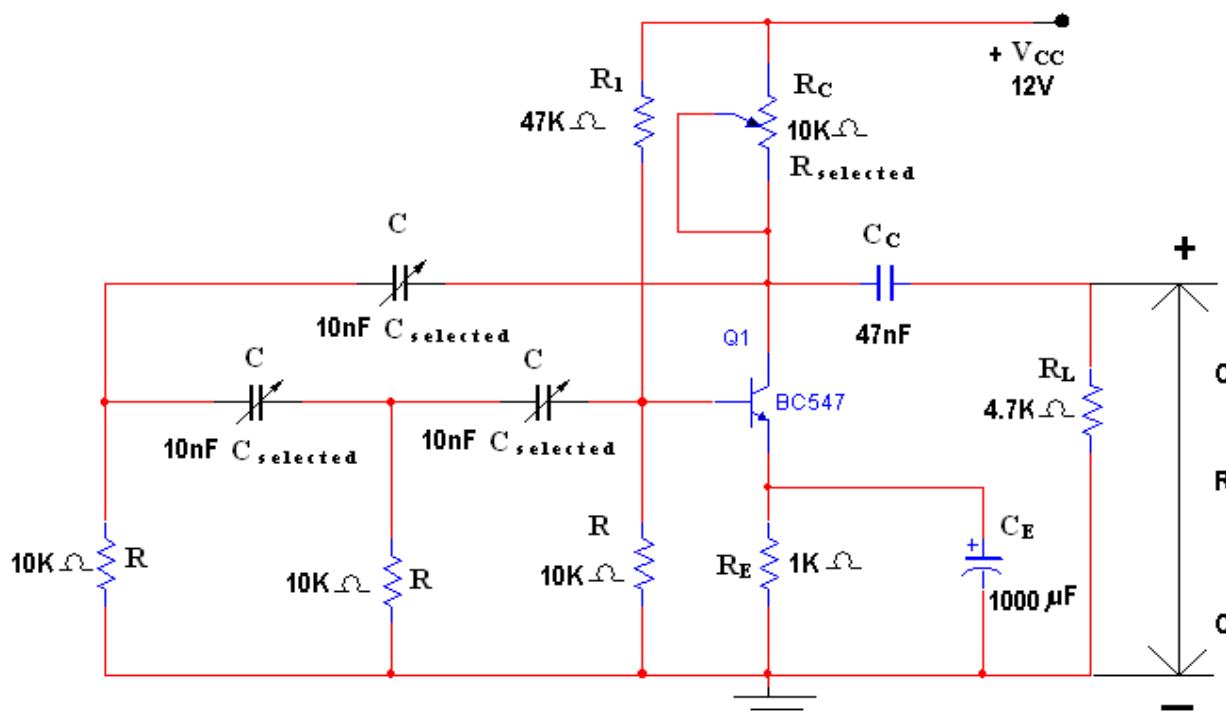


Figure: Circuit diagram of RC Phase shift oscillator.

**PROCEDURE :**

1. Picked up the components from *components bar* in multisim software as per the circuit diagram.
2. Made the connections as per the circuit diagram.
3. Set the  $V_{CC}$  value as 12V.
4. Initially set the *Capacitor C* values as 1nF (0.001 $\mu$ F or 1Kpf) by varied the *capacitor C* Value in % by using the following formula,

$$\text{Setting in \%} = \frac{C_{\text{required}} \times 100}{C_{\text{selected}}}$$

5. To start the simulation clicked on *Run button*.
6. Varied the  $R_C$  value until we get *sine wave form* which consist the  $V_{O(p-p)}$  is approximately 6V because this circuit is designed to get the output voltage as  $6V_{(p-p)}$  in the *CRO*.
- 7.. We observed *Sine wave form* as a output signal in the *CRO*.
8. Drawn the *sine wave form* on the graph by taking the *time period* on X-axis and *Amplitude ( $V_{O(p-p)}$ )* on Y-axis.
9. Calculated and noted the *collector resistor ( $R_C$ )* and *theoretical frequency ( $f_o$ )* value for corresponding *capacitor C* values in the tabular form by using the formulas which are given below,


$$R_C = R_{\text{selected}} - \left[ \frac{\text{Setting in \%} \times R_{\text{selected}}}{100} \right]$$

$$f_o = \frac{1}{2\pi R_C \sqrt{6+4(R_C/R)}}$$

10. Calculated the frequency and output voltage ( $V_{O(p-p)}$ ) values from the graph then noted in the Columns of *practical frequency* and *output voltage* for corresponding *capacitor C* values in the tabular form respectively.
11. Stopped the simulation by click on *Run option* through *Execute button*.
12. Repeat the same procedure from points 4 to 11 for corresponding C values which are given below,
  - a). 2.2 nF ( 0.0022  $\mu$ F or 2.2Kpf ).
  - b). 3.3 nF ( 0.0033  $\mu$ F or 3.3Kpf ).
  - c). 10.0 nF ( 0.01  $\mu$ F or 10Kpf ).
13. Shut down the system safely.
14. We compared that *theoretical frequency value ( $f_o$ )* and *practical frequency value* are same approximately.

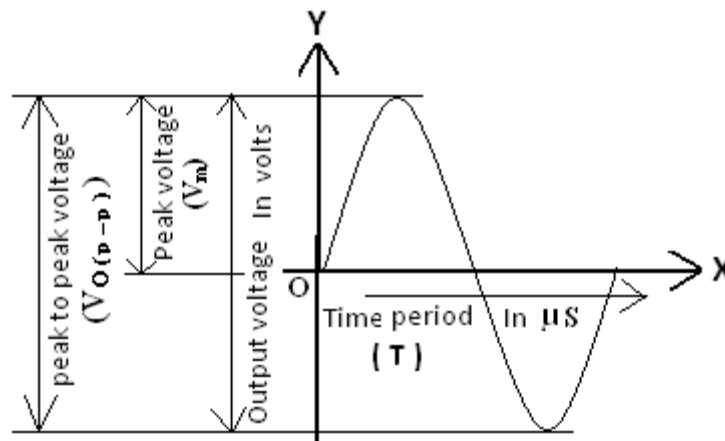**EXPECTED WAVEFORM :**

The following waveform shows the output signal for different capacitor values of *RC phase shift Oscillator*,



**CALCULATIONS :**

Sl. No.	Resistor (R) In KΩ	Capacitor (C) In Kpf	$R_C = R_{\text{selected}} - \left[ \frac{\text{Setting in \%} \times R_{\text{detected}}}{100} \right]$ In KΩ	Theoretical frequency (fo) $\frac{1}{2\pi RC \sqrt{6+4(R_C/R)}}$ In Hz/KHz.	Practical Time Period (In μS)	Practical Frequency In Hz/KHz.	Output Voltage (V <sub>O(p-p)</sub> ) In Volts
1	10	1					
2	10	2.2					
3	10	3.3					
4	10	10					

**Note:** If we observed in the tabular form, for which the C value of 10nF the peak to peak output voltage ( $V_{O(p-p)}$ ) is 4V approximately, but this circuit is designed to get the ( $V_{O(p-p)}$ ) value as 6V approximately. So for this C value we can't considered. If we observed regarding to frequency value, when the C value is increases then the frequency value is decreases.

**RESULT :**

I have verified / drawn the output signal and calculated the frequency values of a given RC phase shift oscillator.

**VIVA VOICE QUESTIONS:**

1. What is positive feedback Amplifier?
2. State Barkhausen condition for oscillation.
3. What are the classifications of oscillators?
4. What are the types of RC oscillators?
5. What is the frequency of RC phase shift oscillator?
6. Applications of RC oscillators?
7. In RC phase shift oscillator, each RC section gives how much phase shift?
8. In AF oscillators which oscillators are used?

**Experiment No. : 10****Date :****Name of the Experiment : COLPITTS OSCILLATOR**

(By using Simulation Software)

**AIM :**

To draw the *sine wave form* and to calculate its frequency values of a given *Colpitts Oscillator*.

**APPARATUS :**

1. System ----- 1 No.
2. Multisim software.

**THEORY :**

The basic configuration of the **Colpitts Oscillator** resembles that of the *Hartley Oscillator* but the difference this time is that the centre tapping of the tank sub-circuit is now made at the junction of a “capacitive voltage divider” network instead of a tapped autotransformer type inductor as in the Hartley oscillator.

the resonant frequency of the LC tank circuit and is given as:

$$f_r = \frac{1}{2\pi\sqrt{L C_T}}$$

where  $C_T$  is the capacitance of  $C_1$  and  $C_2$  connected in series and is given as:

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} \quad \text{or} \quad C_T = \frac{C_1 \times C_2}{C_1 + C_2}$$

The configuration of the transistor amplifier is of a *Common Emitter Amplifier* with the output signal  $180^\circ$  out of phase with regards to the input signal. The additional  $180^\circ$  phase shift require for oscillation is achieved by the fact that the two capacitors are connected together in series but in parallel with the inductive coil resulting in overall phase shift of the circuit being zero or  $360^\circ$ .


**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Colpitt's oscillator.

**PROCEDURE :**

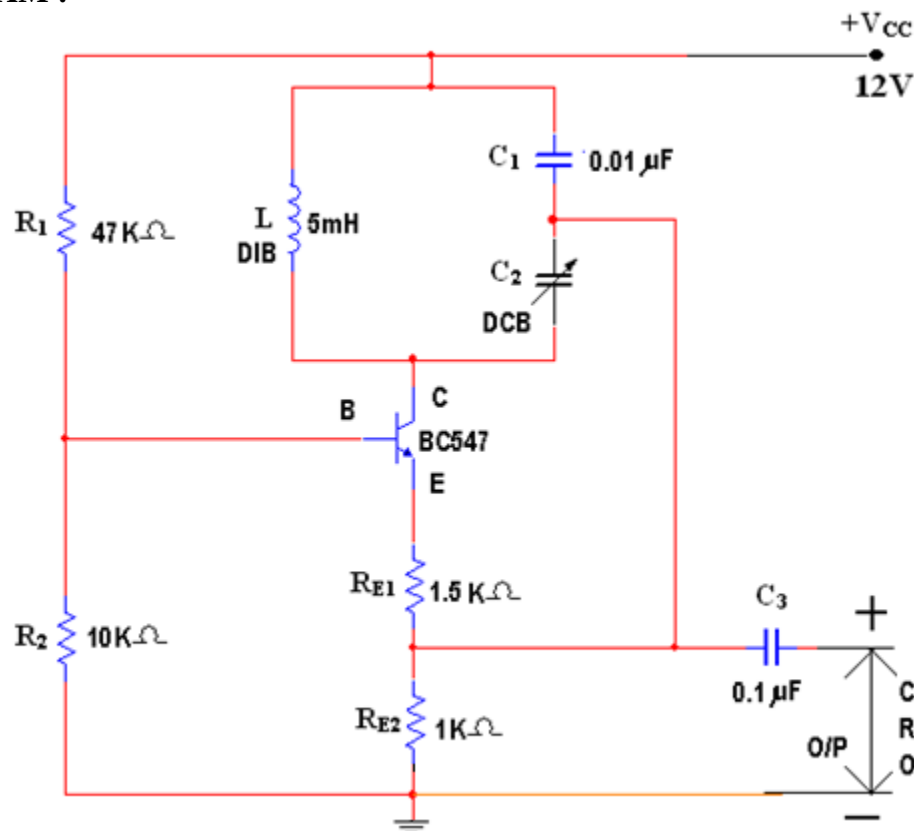1. First calculated the theoretical frequency for all capacitor  $C_2$  values by using the formula which is available in the tabular form.
2. Picked up the components from *components bar* in multisim software as per the circuit diagram.
3. Made the connections as per the circuit diagram.
4. Set the  $V_{CC}$  value as 12V.
5. Set the *inductance*( $L$ ) value as 5mH in DIB and *Capacitor*  $C_2$  value as 1nF (0.001μF or 1Kpf) in DCB.
6. To start the simulation clicked on *Run button*.
7. We observed *Sine wave form* as a output signal in the *CRO*.
8. Drawn the *sine wave form* on the graph by taking the *time period* on X-axis and *Amplitude* ( $V_{O(p-p)}$ ) on Y-axis.
9. Calculated the time period and output voltage ( $V_{O(p-p)}$ ) values from the graph then noted in the Columns of *practical time period* and *output voltage* for corresponding *capacitor*  $C_2$  values in the tabular form respectively.
10. Stopped the simulation by click on *Run option* through *Execute button*.
11. Repeat the same procedure from points 5 to 11 for corresponding  $C_2$  values which are given below,
  - a). 2.2 nF/2.2Kpf.
  - b). 3.3 nF/3.3Kpf.
  - c). 10.0 nF/10Kpf.
12. Shut down the system safely.
13. Now calculated the practical frequency by using formula  $1/T$  and noted it in corresponding columns of  $C_2$
14. We compared that *theoretical frequency* value ( $f_o$ ) and *practical frequency* value are same approximately.




**TABULAR FORM / CALCULATIONS :**

Sl No.	Capa Citor (C <sub>1</sub> )	Capa Citor (C <sub>2</sub> )	Indu-ctor. (L)  In mH	Total Capacitance (C <sub>T</sub> ) $C_1 C_2 / (C_1 + C_2)$ In nF	Theoretical Frequency(f <sub>0</sub> )= $\frac{1}{2\pi \sqrt{L C_T}}$ In KHz	Pract-ical – Time-Period. In μS	Pract-Ical frequency In KHz.	Output voltage (V <sub>O p-p</sub> ) In Volts.
1.	10Kpf	1Kpf	5					
2.	10Kpf	2.2Kpf	5					
3.	10Kpf	3.3Kpf	5					

**EXPECTED WAVEFORM :**

The following waveform shows the output signal for *Colpitts Oscillator*

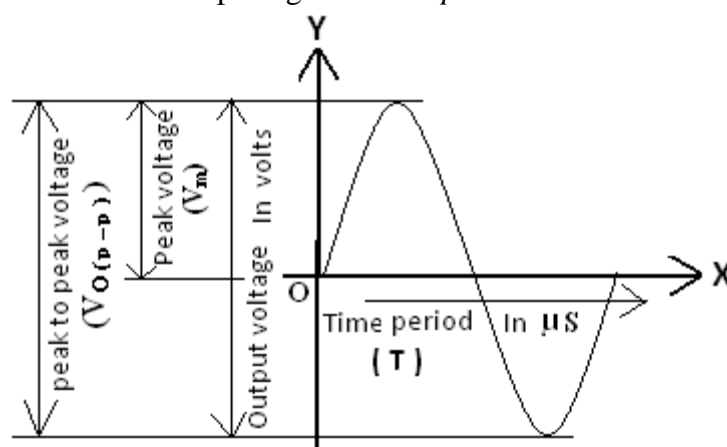**RESULT :**

I have drawn the output signal and calculated the frequency values of a given *Colpitts Oscillator*.

**VIVA VOICE Questions:**

1. What are LC oscillators?
2. What is the frequency of Colpitts oscillator?
3. What is the condition for sustained oscillation in Colpitts oscillator?
4. Applications of LC oscillators?
5. In Colpitts oscillator, feedback circuit consists of how many Inductors and capacitors?
6. Which type of feedback is used for Colpitts oscillator?
7. What is Q in Colpitts oscillator?
8. What is the advantage of Colpitts oscillator?
9. How does Colpitts oscillator calculate frequency?
10. What are the advantages and disadvantages of LC oscillator?

# **PART – B**

**Using Hardware  
(Off the Syllabus)**



**Experiment No. : 1****Date :****Name of the Experiment : VOLTAGE SERIES FEED BACK AMPLIFIER**

(By using Hardware)

**AIM :**

- To obtain the frequency response of *Voltage Series feedback Amplifier* by using hardware.
- To calculate the bandwidth of this amplifier.

**APPARATUS :**

- |                              |       |            |
|------------------------------|-------|------------|
| 1). Function Generator       | ----- | 1 No.      |
| 2). Cathode Ray Oscilloscope | ----- | 1 No.      |
| 3). Regulated Power Supply   | ----- | 1 No.      |
| 4). Bread Board              | ----- | 1 No.      |
| 5). Probes                   | ----- | 2 No.      |
| 6). Connecting wires         | ----- | A Few Nos. |

**COMPONENTS :**

- |                |                             |       |       |
|----------------|-----------------------------|-------|-------|
| 1). Transistor | a). BC547 NPN               | ----- | 1 No. |
| 2). Resistors  | a). $100\ \Omega$           | ----- | 1 No. |
|                | b). $10\ \text{K}\ \Omega$  | ----- | 1 No. |
|                | c). $100\ \text{K}\ \Omega$ | ----- | 1 No. |
| 3). Capacitors | a). $10\ \mu\text{F}$       | ----- | 1 No. |
|                | a). $22\ \mu\text{F}$       | ----- | 1 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

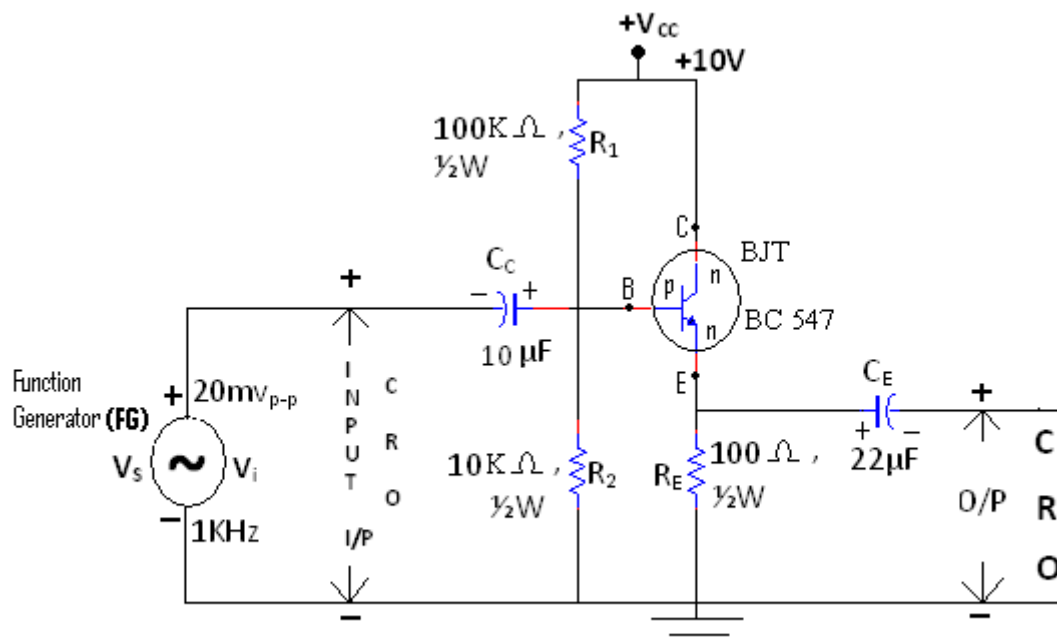
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of voltage series feed back amplifier.

**PROCEDURE :**

- 1). Connected the circuit as per the circuit diagram.
- 2). Removed the probe of *CRO* from output (O/P) side and connected it at input (I/P) side to set the input signal i.e. sine wave having the value of  $20\text{mV}_{\text{p-p}}$  & 1KHz.
- 3). Then switched ON the *function generator* and *CRO*; but don't switched ON the *RPS*.
- 4). Now Kept the *AC/GND/DC* switch is at *AC* position.
- 5). Now applied the input signal i.e. sine wave by pressing the sine wave function key in the *function generator*.
- 6). Initially kept the 1KHz. frequency by varying the frequency control in the *function generator*.
- 7). Now applied the peak to peak amplitude of a sine wave is of  $20\text{mV}_{\text{p-p}}$  by varying the amplitude control in the *function generator* through observing in the *CRO*.
- 8). Kept this value of input signal as constant up to the completion of the experiment Otherwise the wrong output would occurred.
- 9). Then removed the probe of *CRO* from the input side and connected it across the output side.
- 10). Now switched ON the *RPS* and set the 10V in it i.e.  $V_{\text{CC}} = 10\text{V}$ .
- 11). Varied the different frequency steps of 10Hz, 500Hz, 1KHz, 100KHz, 200KHz, 400KHz, 600KHz, 800KHz, 1MHz. by adjusted the frequency control in the *function generator* and noted down the corresponding values of output signal i.e. peak to peak amplitude (voltage) of sine wave by observing in the *CRO*.
- 12). Now switched OFF the *RPS*, *function generator* and *CRO*.
- 13). Then calculated the *voltage gain*  $A_V = V_O/V_i$  & *gain in dB*  $= 20\log_{10}(A_V)$  and noted down the values in the specified columns of the tabular column.
- 14). Plotted the graphs (frequency response curves) as per below,
  - a). frequency on X-axis & gain in dB on Y-axis.
  - b). frequency on X-axis & voltage gain on Y-axis.
- 15). Calculated the *band width* from the above two (frequency response curves) graphs by using the formula  $f_2 - f_1$  which is given under the heading of *parameters*.

**Notes:**

1. Amplifier means which amplifies the sinusoidal and non-sinusoidal wave forms with out change in frequency. In voltage series feedback amplifier, network is in parallel with the the output of the amplifier.
2. A fraction of the output voltage through the feedback network is applied in series with in the input voltage of the amplifier.
3. The series connections at the input, increase the input resistance. In this case the amplifier is a true voltage amplifier.
4. The common collector or emitter follower is an example of voltage series feedback amplifier. Since the voltage developed in the output is in series with the input voltage as for as the base – emitter junction is connected.

**TABULAR FORM :**

Sl.No.	Input Voltage( $V_i$ ) In milli Volts (peak to peak)	Frequency In Hz/KHz.	Output Voltage( $V_o$ ) In mVolts.	Voltage gain $A_v = V_o/V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20mV	10 Hz.			
2	20mV	500 Hz.			
3	20mV	1 KHz.			
4	20mV	100 KHz.			
5	20mV	200 KHz.			
6	20mV	400 KHz.			
7	20mV	600 KHz.			
8	20mV	800 KHz.			
9	20mV	1 MHz.			

**EXPECTED GRAPH :**

A). Frequency response curve for *frequency verses gain in dB.*

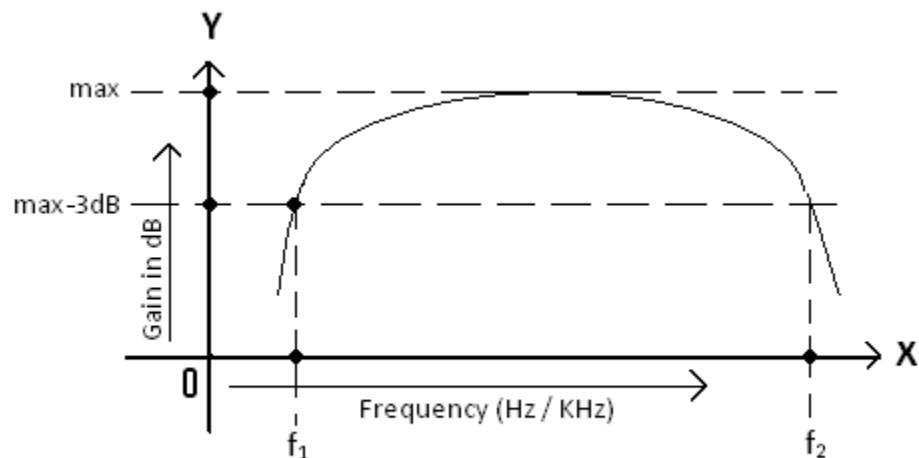


Figure: Frequency response curve of voltage series feed back amplifier  
For frequency verses gain in dB.

B). Frequency response curve for *frequency verses voltage gain.*

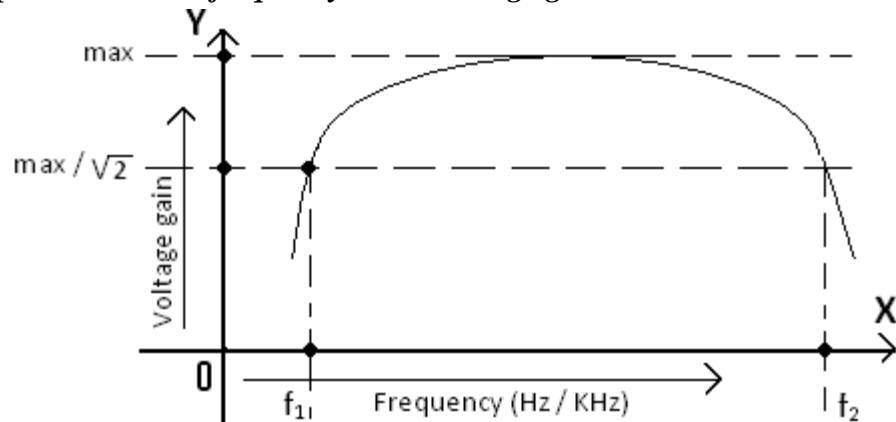


Figure: Frequency response curve of voltage series feed back amplifier  
For frequency verses voltage gain.

**PARAMETERS :**

- 1). Band width of frequency response curve for frequency verses gain in dB.  $= f_2 - f_1$   
=
- 2). Band width of frequency response curve for frequency verses voltage gain  $= f_2 - f_1$   
=

**RESULT :**

We have obtained the frequency response curves of *Voltage series feed back Amplifier* for frequency verses gain in dB & frequency verses voltage gain and calculated the band width of both of them. The band width values are given below,

- 1). Band width of frequency response curve for frequency verses gain in dB. =
- 2) Band width of frequency response curve for frequency verses voltage gain =

**VIVA VOICE Questions:**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.



**Experiment No. : 2****Date :****Name of the Experiment : BOOTSTRAPPED EMITTER FOLLOWER**

(By using Hardware)

**AIM :**To obtain the frequency response of *Bootstrapped Emitter Follower*.**APPARATUS :**

- |                              |       |            |
|------------------------------|-------|------------|
| 1). Function Generator       | ----- | 1 No.      |
| 2). Cathode Ray Oscilloscope | ----- | 1 No.      |
| 3). Regulated Power Supply   | ----- | 1No.       |
| 4). Bread Board              | ----- | 1 No.      |
| 5). Probes                   | ----- | 2 No.      |
| 6). Connecting wires         | ----- | A Few Nos. |

**COMPONENTS :**

- |                |                    |       |       |
|----------------|--------------------|-------|-------|
| 1). Transistor | a). BC547 NPN      | ----- | 1 No. |
| 2). Resistors  | a). 100 $\Omega$   | ----- | 1 No. |
|                | b). 4.7K $\Omega$  | ----- | 1 No. |
|                | b). 10 K $\Omega$  | ----- | 1 No. |
|                | c). 100 K $\Omega$ | ----- | 1 No. |
| 3). Capacitors | a). 10 $\mu$ F     | ----- | 2 No. |
|                | b). 22 $\mu$ F     | ----- | 1 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

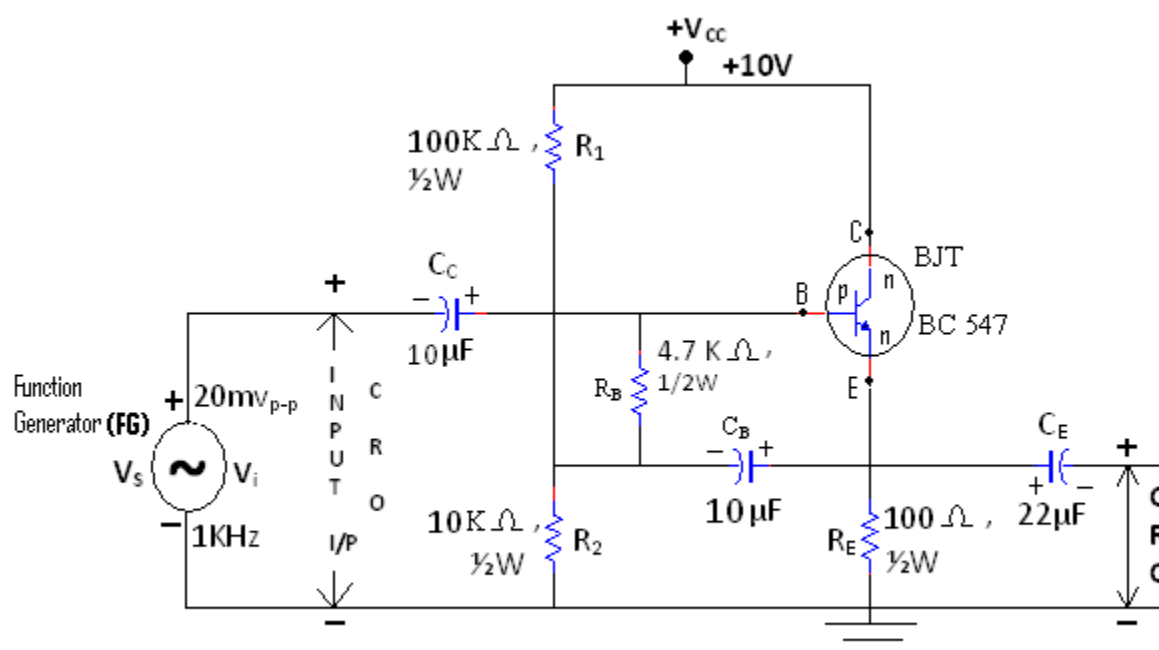
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Bootstrapped Emitter Follower

**PROCEDURE :**

- 1). Connected the circuit as per the circuit diagram.
- 2). Removed the probe of *CRO* from output (O/P) side and connected it at input (I/P) side to set the input signal i.e. sine wave having the value of  $20\text{mV}_{\text{p-p}}$  & 1 KHz.
- 3). Then switched ON the *function generator* and *CRO*; but don't switched ON the *RPS*.
- 4). Now Kept the *AC/GND/DC* switch is at *AC* position.
- 5). Now applied the input signal i.e. sine wave by pressing the sine wave function key in the *function generator*.
- 6). Initially kept the 1 KHz. frequency by varying the frequency control in the *function generator*.
- 7). Now applied the peak to peak amplitude of a sine wave is of  $20\text{mV}_{\text{p-p}}$  by varying the amplitude control in the *function generator* through observing in the *CRO*.
- 8). Kept this value of input signal as constant up to the completion of the experiment Otherwise the wrong output would occurred.
- 9). Then removed the probe of *CRO* from the input side and connected it across the output side.
- 10). Now switched ON the *RPS* and set the 10V in it i.e.  $V_{\text{CC}} = 10\text{V}$ .
- 11). Varied the different frequency steps of 10Hz, 500Hz, 1KHz, 100KHz, 200KHz, 400KHz, 600KHz, 800KHz, 1MHz. by adjusted the frequency control in the *function generator* and noted down the corresponding values of output signal i.e. peak to peak amplitude of sine wave by observing in the *CRO*.
- 12). Now switched OFF the *RPS*, *function generator* and *CRO*.
- 13). Then calculated the *voltage gain*  $A_V = V_o/V_i$  & *gain in dB*  $= 20\log_{10}(A_V)$  and noted down the values in the specified columns of the tabular column.
- 14). Plotted the graphs (frequency response curves) as per below,
  - a). frequency on X-axis & gain in dB on Y-axis.
  - b). frequency on X-axis & voltage gain on Y-axis.

*Note:* Bootstrap Emitter Follower uses to increase the input impedance and to work as correct *Buffer*. For example, The voltage gain of this *amplifier* is 1 it means the output voltage is equal to input voltage, then we can say that it is the correct *Buffer*. Now If you observed the output of *voltage series feedback amplifier* the max. output voltage is less as compared to input voltage, it means buffer is incorrect. To increase the output voltage which is equal to the input voltage here we have used the *Bootstrapped Emitter Follower*. It is not possible to find out the band width because there is no amplification.

**TABULAR FORM :**

Sl.No.	Input Voltage ( $V_{i\text{P-P}}$ ) In mVolts.	Frequency In Hz/KHz.	Output Voltage ( $V_{o\text{P-P}}$ ) In mVolts.	Voltage gain $A_V = V_o/V_i$	Gain in dB = $20\log_{10}(A_V)$
01	20mV	10 Hz.			
02	20mV	500 Hz.			
03	20mV	1 KHz.			
04	20mV	100 KHz.			
05	20mV	200 KHz.			
06	20mV	400 KHz.			
07	20mV	600 KHz.			
08	20mV	800 KHz.			
09	20mV	1 MHz.			

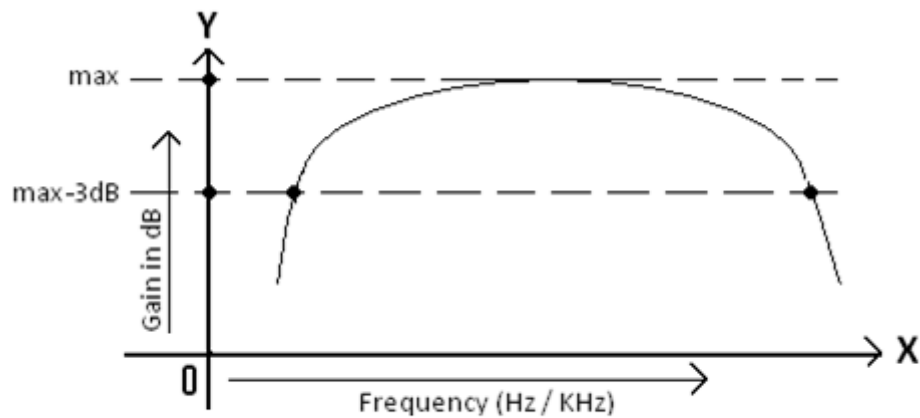
**EXPECTED GRAPH :**

Figure: Frequency response curve of Bootstrapped Emitter Follower.  
For Frequency verses gain in dB.

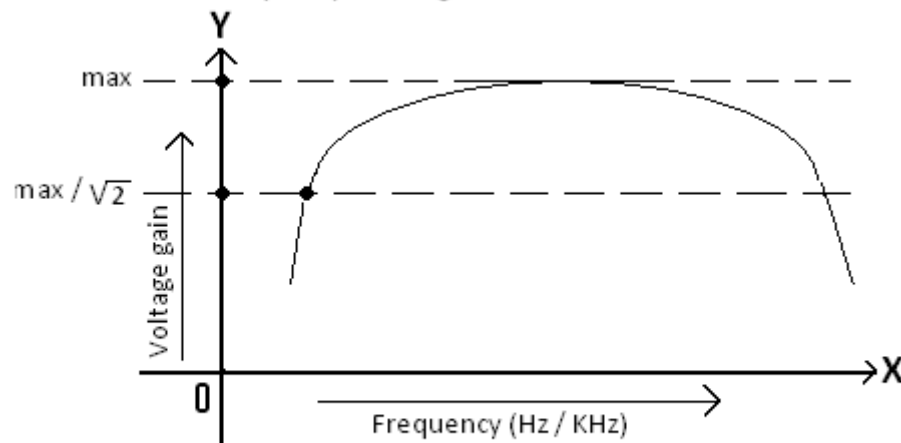


Figure: Frequency response curve of Bootstrapped Emitter Follower.  
For frequency verses voltage gain

**RESULT :**

We have obtained the gain for different frequencies of *Bootstrapped Emitter Follower*.

**VIVA VOICE Questions:**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.



**Experiment No. : 3****Date :**

**Name of the Experiment : DARLINGTON PAIR AMPLIFIER**  
(Using hardware)

**AIM :**

To obtain the frequency response curve for *Darlington pair amplifier* using hardware.

**APPARATUS :**

- |   |            |
|---|------------|
| 1. Regulated power supply ( RPS ) -----   | 1 No.      |
| 2. Cathode Ray Oscilloscope ( CRO ) ----- | 1 No.      |
| 3. Function generator -----               | 1 No.      |
| 4. Probes -----                           | 1 No.      |
| 5. Bread board -----                      | 1 No.      |
| 6. Connecting wires -----                 | A few Nos. |

**COMPONENTS :**

- |  |            |
|--|------------|
| 1. Transistor BC 547 -----   | 2 No.      |
| 2. Capacitors :  |            |
| ii). $10\ \mu\text{F}$ -----   | 2 No.      |
| i). $22\ \mu\text{F}$ -----  | 1 No.      |
| 3. Resistors :   |            |
| i). $100\ \text{K}\Omega$ , $10\ \text{K}\Omega$ , $100\ \Omega$ ----- | Each 2 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

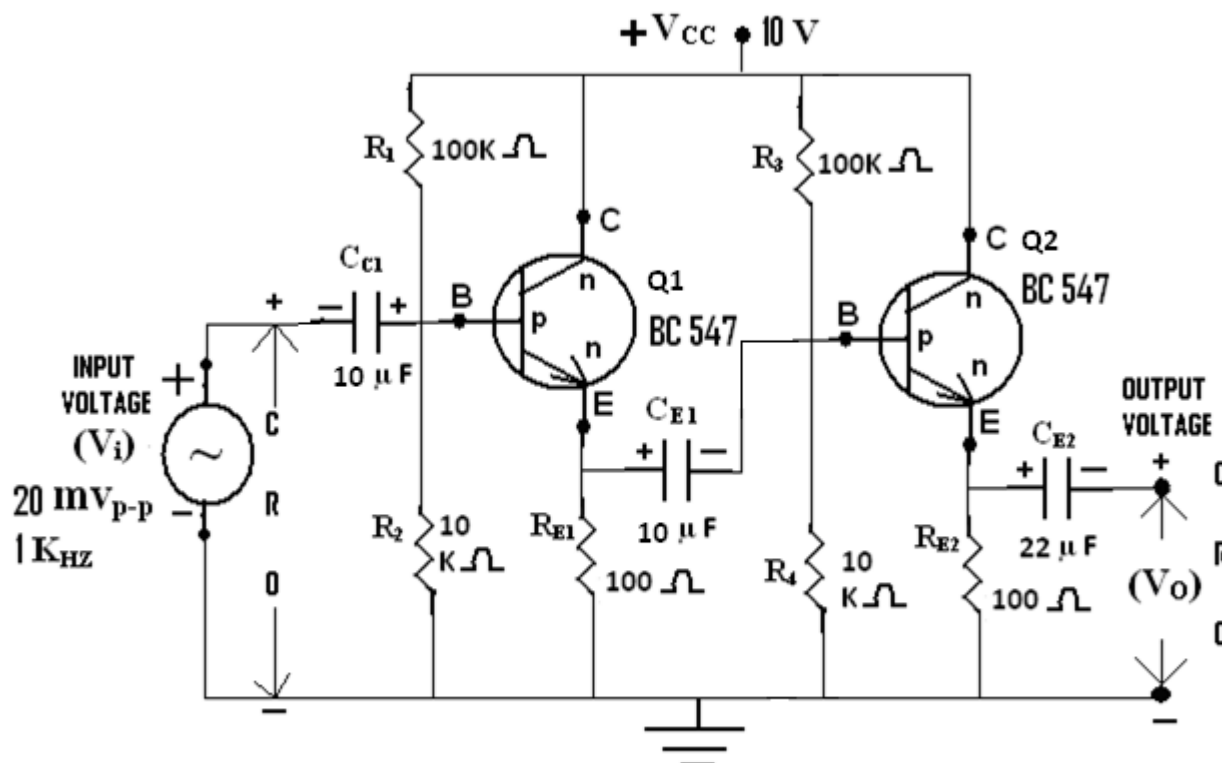
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Darlington pair amplifier.

**PROCEDURE :**

1. We have connected the circuit as per the circuit diagram which is shown above.
2. Initially connected the probe across the function generator as per shown in the circuit diagram to set the input signal.
3. Switched *ON* the *CRO* and *function generator*.
4. Applied the input signal as *sine wave form* having the values of  $20\text{mV}_{\text{p-p}}$ ,  $1\text{KHz}$ . from the function generator by observing in the *CRO*.
5. Later removed the probe from that place and connected it across the capacitor  $C_{C2}$  to observe the output.
6. Switched *ON* the *RPS* and kept the  $10\text{V}$  as  $V_{\text{CC}}$ .
7. Kept the amplitude of the input signal as constant as  $20\text{mV}_{\text{p-p}}$  for all frequency steps.
8. Noted down the values output voltage of output signal in terms of peak to peak voltages by varying the different frequency steps in the function generator which are given below,  $10\text{Hz}$ ,  $500\text{Hz}$ ,  $1\text{KHz}$ ,  $100\text{KHz}$ ,  $200\text{KHz}$ ,  $400\text{KHz}$ ,  $600\text{KHz}$ ,  $800\text{KHz}$ ,  $1\text{MHz}$ .
9. Repeat the same procedure for point 8 for corresponding frequency values.
10. Now calculated and noted down the values of *voltage gain* ( $A_v$ ) and *gain in dB* to the corresponding values of *output voltage* ( $V_o$ ) & *input voltage* ( $V_i$ ) by using the formulas given below,  


$$\text{Voltage gain } (A_v) = V_o / V_i \text{ and } \text{Gain in dB} = 20\log_{10}(A_v).$$
11. Plotted the graph between *frequency on X- axis* and *gain in dB on Y- axis*.

**TABULAR FORM:**

Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in mV	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			

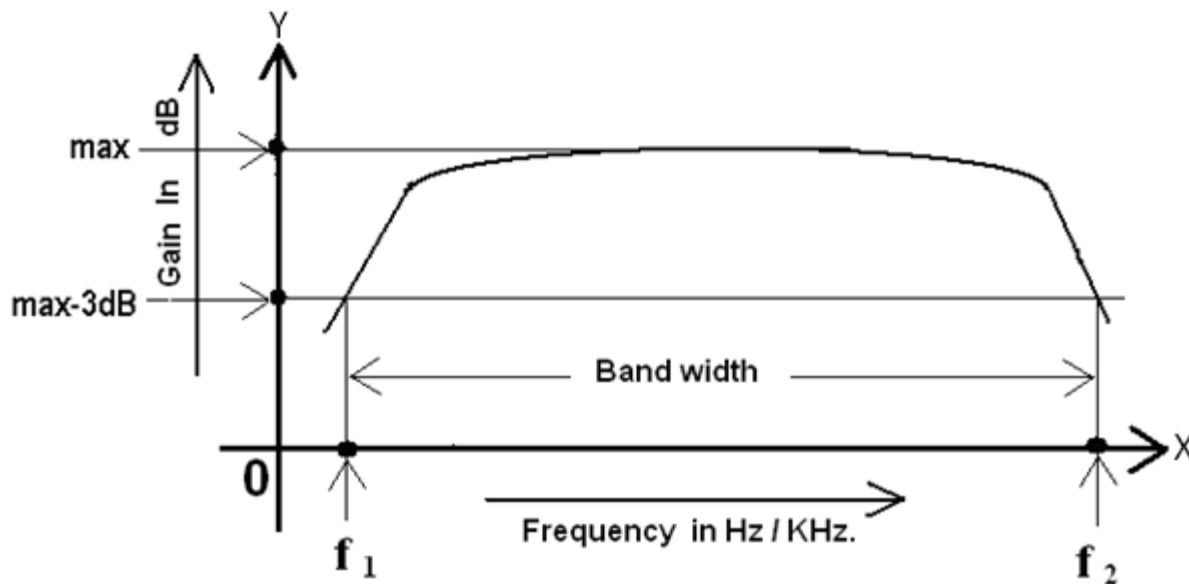**EXPECTED GRAPH :**

The following graph shows for frequency response curve of a *Darlington pair Amplifier*.



**Note :** . It is not possible to find out the band width because there is no amplification.

**CONCLUSSION :**

We have formed the circuit of Darlington pair amplifier by connected two common collector amplifiers in two stages. The input impedance of two stage common collector amplifier i.e. Darlington pair amplifier is very high as compared to single stage common collector amplifier. Due to this reason only the voltage gain of Darlington pair amplifier is less than as compared to single stage common collector amplifier.

**RESULT :**

I have drawn the frequency response curve and calculated the band width of a *Darlington pair amplifier*.

**VIVA VOICE Questions :**

**Note :** The questions which are avail in *Software section-A* under the same experiment are applicable here also.





**Experiment No. : 04****Date :****Name of the Experiment : TWO STAGE RC COUPLED AMPLIFIER  
(Using Hardware)****AIM :**

- i). To obtain the frequency response of *Two stage RC Coupled Amplifier*.
- ii). To calculate the bandwidth of this amplifier.

**APPARATUS :**

- |                              |       |            |
|------------------------------|-------|------------|
| 1). Function Generator       | ----- | 1 No.      |
| 2). Cathode Ray Oscilloscope | ----- | 1 No.      |
| 3). Regulated Power Supply   | ----- | 1 No.      |
| 4). Bread Board              | ----- | 1 No.      |
| 5). Probes                   | ----- | 2 No.      |
| 6). Connecting wires         | ----- | A Few Nos. |

**COMPONENTS :**

- |                |                    |       |       |
|----------------|--------------------|-------|-------|
| 1). Transistor | a). BC547 NPN      | ----- | 2No.  |
| 2). Resistors  | a). $1K\ \Omega$   | ----- | 2 No. |
|                | b). $2.2K\ \Omega$ | ----- | 2 No. |
|                | c). $10K\ \Omega$  | ----- | 2 No. |
|                | d). $47K\ \Omega$  | ----- | 2 No. |
|                | e). $100K\ \Omega$ | ----- | 1 No. |
| 3). Capacitors | a). $10\ \mu F$    | ----- | 3 No. |
|                | b). $22\ \mu F$    | ----- | 3 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

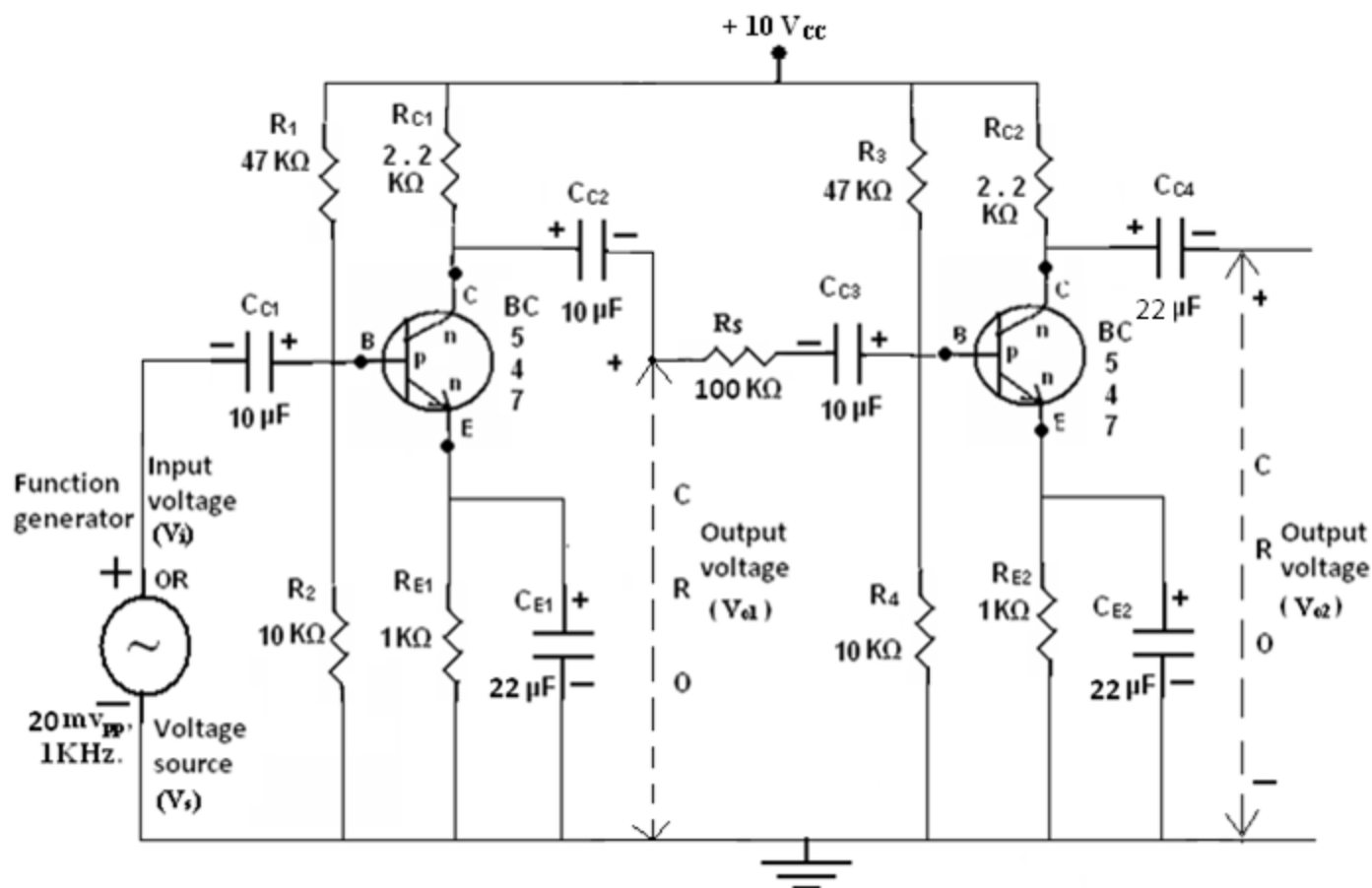
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Two stage RC coupled amplifier.

**PROCEDURE :**

1. We have connected the circuit as per the circuit diagram which is shown above.
2. Initially connected the probe across the function generator as per shown in the circuit diagram to set the input signal.
3. Switched *ON* the *CRO* and *function generator*.
4. Applied the input signal as *sine wave form* having the values of  $20\text{mV}_{\text{p-p}}$ ,  $1\text{KHz}$  from the function generator by observing in the *CRO*.
5. Removed the probe from that place and connected it across the  $C_{C2}$  to observe the output of single stage.
6. Switched *ON* the *RPS* and kept the  $10\text{V}$  as  $V_{\text{CC}}$ .
7. Kept the amplitude of the input signal as constant as  $20\text{mV}_{\text{p-p}}$  for all frequency steps.
8. Noted down the values of output voltage in terms of peak to peak voltages by varying the different frequency steps in the function generator which are given below,  
 $10\text{Hz}$ ,  $500\text{Hz}$ ,  $1\text{KHz}$ ,  $100\text{KHz}$ ,  $200\text{KHz}$ ,  $400\text{KHz}$ ,  $600\text{KHz}$ ,  $800\text{KHz}$ ,  $1\text{MHz}$ .
9. The above readings noted in the tabular form of *single stage RC coupled amplifier*.
10. Disconnect the probe from  $C_{C2}$  and reconnected it across  $C_{C4}$  to observe the output of second stage.
11. Repeat the same procedure as per point 8 for tabular form of *Two stage RC Coupled Amplifier*.

12. Now calculated and noted down the values in the tabular form of *single stage RC Coupled Amplifier* as per given below,

- Voltage gain  $(A_v) = V_o / V_i$  and Gain in dB  $= 20\log_{10}(A_v)$ .
- Plotted the graph between *frequency on X- axis* and *gain in dB on Y- axis*.
- Band width from the graph by using the formula-  $\text{Band width} = f_2 - f_1$

13. Now calculated and noted down the values in the tabular form of *Two stage RC Coupled Amplifier* as per given below,

- Voltage gain  $(A_v) = V_o / V_i$  and Gain in dB  $= 20\log_{10}(A_v)$ .
- Plotted the graph between *frequency on X- axis* and *gain in dB on Y- axis*.
- Band width from the graph by using the formula-  $\text{Band width} = f_4 - f_3$

#### TABULAR COLUMN :

##### A). Single stage RC coupled Amplifier :


Sl. No.	Input voltage $(V_i)$ in mV	Frequency in Hz / KHz.	Output Voltage $(V_o)$ in V	Voltage gain $(A_v) = V_o / V_i$	Gain in dB $= 20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			

##### B). Two stage RC coupled Amplifier :


Sl. No.	Input voltage $(V_i)$ in mV	Frequency in Hz / KHz.	Output Voltage $(V_o)$ in V	Voltage gain $(A_v) = V_o / V_i$	Gain in dB $= 20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			

**EXPECTED WAVEFORM :**

I have got the *Sine wave form* on the CRO as output signal for both *RC Coupled Amplifiers* which is shown below,

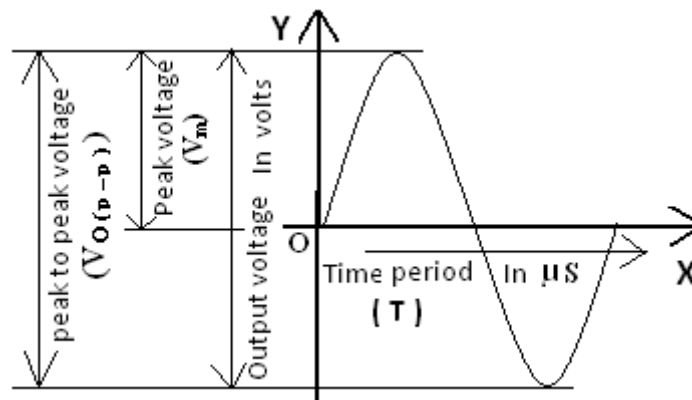**EXPECTED GRAPH :**

The following graph shows the frequency response curves of both *Single stage & Two stage RC coupled Amplifiers*.

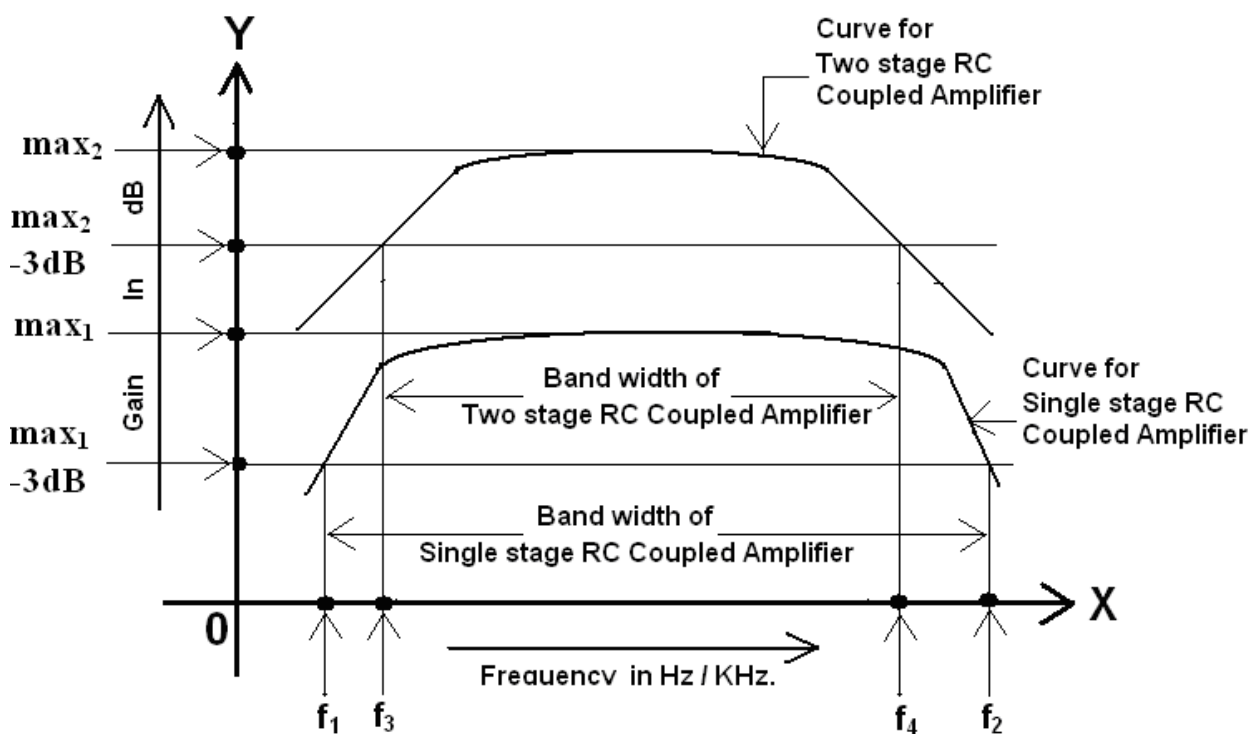**CALCULATIONS :**

- 1). Band width "*single stage RC coupled amplifier*" =  $f_2 - f_1$   
=
- 2). Band width "*two stage RC coupled amplifier*" =  $f_4 - f_3$   
=

**CONCLUSION :**

1. I have observed that

- a). The bandwidth of *Two stage RC coupled amplifier* is less as compared to *Single stage RC coupled amplifier* and
- b). The gain of *Two stage RC coupled amplifier* is more as compared to *Single stage RC coupled amplifier*

**RESULT :**

I verified / drawn the frequency response curve and found the bandwidth values of a *single stage & two stage RC coupled amplifiers*. The band width values are,

- 1). Band width of *single stage RC coupled amplifier* =
- 2). Band width of *two stage RC coupled amplifier* =

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.



**Experiment No. : 05****Date :****Name of the Experiment : CURRENT SHUNT FEED BACK AMPLIFIER**  
(By using Hardware)**AIM :**

1. To plot the frequency response curve of a *Current shunt feed back Amplifier* for both *with feed back & without feed back*.

**APPARATUS :**


- |                                    |       |            |
|------------------------------------|-------|------------|
| 1. Regulated power supply ( RPS )  | ----- | 1 No.      |
| 2. Cathode Ray Oscilloscope ( CRO) | ----- | 1 No.      |
| 3. Function generator              | ----- | 1 No.      |
| 4. Probes                          | ----- | 1 No.      |
| 3. Bread board                     | ----- | 1 No.      |
| 4. Connecting wires                | ----- | A few Nos. |

**COMPONENTS :**

- |                        |       |       |
|------------------------|-------|-------|
| 1. Transistor BC 547   | ----- | 2 No. |
| 2. Resistors :         |       |       |
| i). 100 $\Omega$       | ----- | 1 No. |
| ii). 1 K $\Omega$      | ----- | 2 No. |
| iii). 2 . 2 K $\Omega$ | ----- | 2 No. |
| iv). 10 K $\Omega$     | ----- | 2 No. |
| v). 47 K $\Omega$      | ----- | 2 No. |
| vi). 100 K $\Omega$    | ----- | 1 No. |
| 3. Capacitors :        |       |       |
| i). 10 $\mu$ F         | ----- | 4 No. |
| ii). 22 $\mu$ F        | ----- | 2 No. |

**THEORY :**

*Note : Theory had given in Software section-A of this same experiment. That same theory can apply here also.*

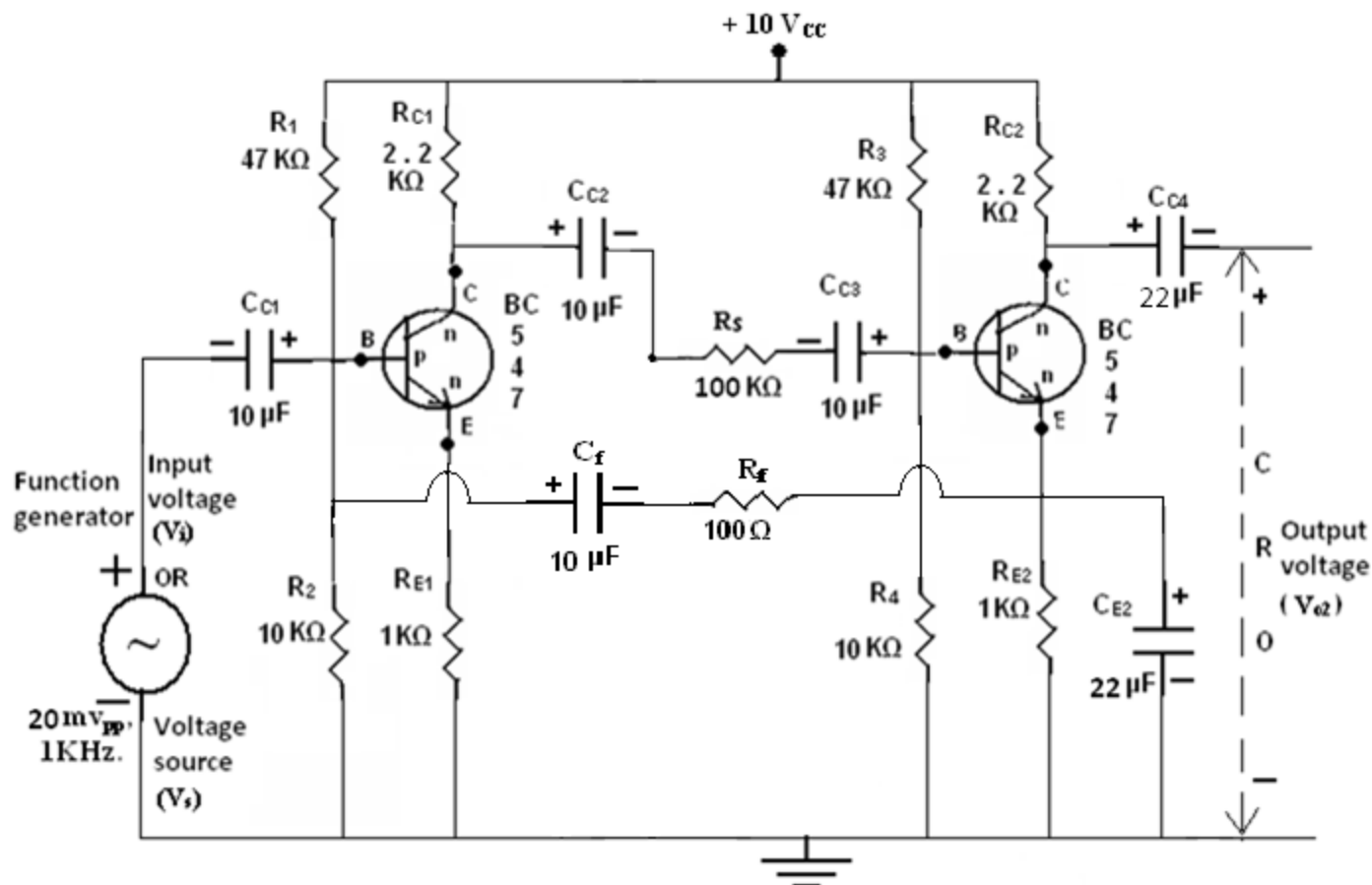**CIRCUIT DIAGRAM :****PROCEDURE :**

1. Connections are made as per the circuit diagram.
2. Initially connected the *CRO* across the *Function generator*.
3. Switched **ON** the Cathode ray oscilloscope (*CRO*) and *Function generator*.
4. Applied the  $20\text{ mV}_{pp}$ ,  $1\text{ KHz}$  sine wave signal to the circuit from *Function generator* by observing in the *CRO*.
5. We have kept this  $20\text{ mV}_{pp}$  input voltage (Which has been applied from function generator) as constant for all steps of frequency while taking the readings for *Current shunt feed back amplifier* for both with feed back & without feed back .
6. Disconnected the *CRO* from the function generator .
7. Now Connected the *CRO* at output side to measure the peak to peak output voltage.
8. Applied the  $+V_{CC}$  as  $10\text{ V}$  to the circuit from the *Regulated power supply (RPS)*.
9. Later we have noted down the readings for output voltage in the tabular form of *with feed back*. from the *CRO*, by varying the different steps of frequency (i.e.  $10\text{ Hz}$ ,  $500\text{ Hz}$ .,  $1\text{ KHz}$ ,  $100\text{ KHz}$ ,  $200\text{ KHz}$ ,  $400\text{ KHz}$ ,  $600\text{ KHz}$ ,  $800\text{ KHz}$ ,  $1\text{ MHz}$ .) in function generator.
10. After this we removed the feed back capacitor ( $C_f$ ) & resistor ( $R_f$ ) from the circuit completely.
11. Now the circuit is became as the *without feed back amplifier*.
12. Again we have noted down the readings for output voltage in the tabular form of *without feed back* .from the *CRO*, by varying the different steps of frequency (i.e.  $10\text{ Hz}$ ,  $500\text{ Hz}$ ,  $1\text{ KHz}$ ,  $100\text{ KHz}$ ,  $200\text{ KHz}$ ,  $400\text{ KHz}$ ,  $600\text{ KHz}$ ,  $800\text{ KHz}$ ,  $1\text{ MHz}$ .) in function generator.



13. We have observed that the readings of *without feed back amplifier's* output voltage is greater than the *with feed back amplifier*.
14. Finally we switched **OFF** the function generator, cathode ray oscilloscope and regulated power supply.
15. Calculated the Voltage gain by using the formula of  $V_o / V_i$  and Gain in dB by using the formula of  $20\log_{10}(A_v)$  in both tabular forms of *with feed back* and *without feed back amplifiers*.
16. Drawn the graphs of both amplifiers in single graph sheet.
17. While drawing the graph taken the *frequency* on X-axis and *Gain in dB* on Y-axis.
18. Finally calculated the *bandwidth* of both amplifiers from this graph sheet as per the following formulas,
  - i). For *Current shunt feed back amplifier (With feed back)*  $(BW) = f_2 - f_1$
  - ii). For *Current shunt feed back amplifier (Without feed back)*  $(BW) = f_4 - f_3$
19. We have noted down that the *band width* of *with feed back amplifier* is high as compared to the *without feed back amplifier*.

### TABULAR COLUMN :

#### A). With feed back :


Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in mV	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			

#### B). Without feed back :

Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in mV	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	100 KHz.			
5	20	200 KHz.			
6	20	400 KHz.			
7	20	600 KHz.			
8	20	800 KHz.			
9	20	1 MHz.			

**EXPECTED GRAPH :**

The following graph shows for *Current shunt feed back amplifier* for both *with feed back* and *without feed back*.

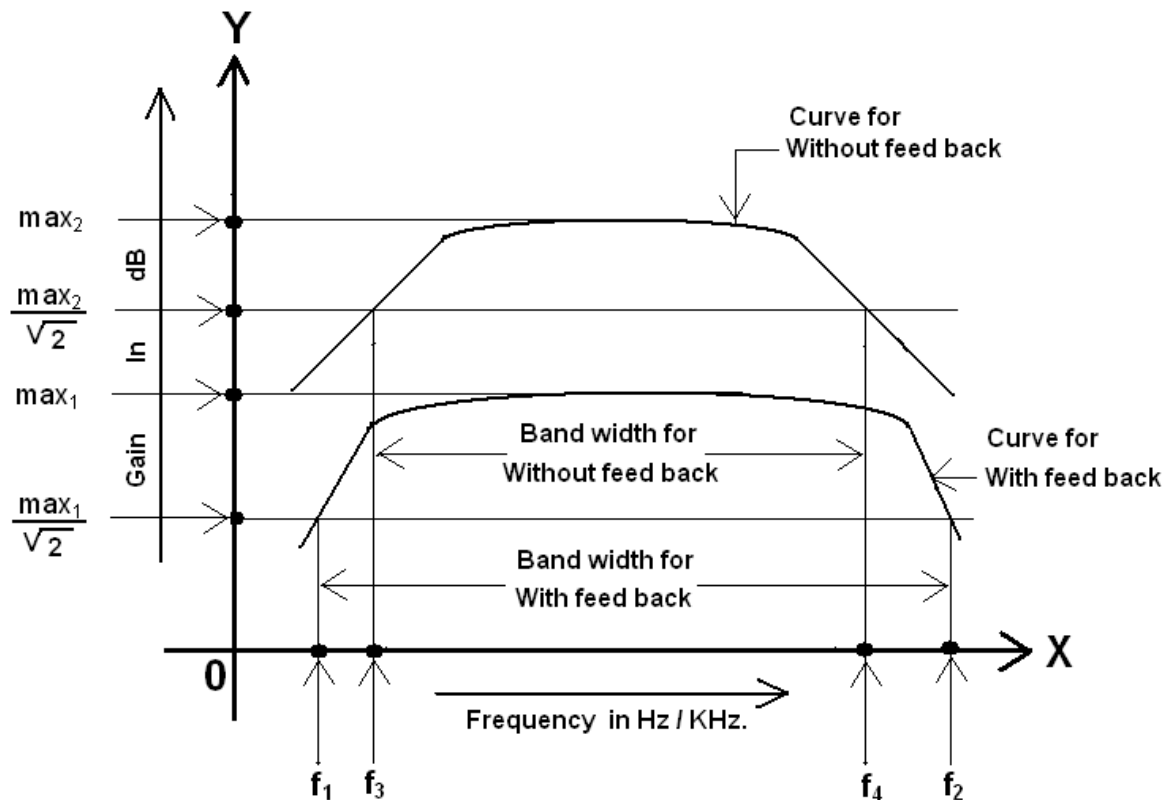**RESULT :**

We drawn the graph for frequency response of a *Current shunt feed back amplifier* for both *with feed back* and *without feed back*.

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.

**Experiment No. : 6****Date :****Name of the Experiment : SINGLE TUNED VOLTAGE AMPLIFIER  
(Using hardware)****AIM :**

To obtain the frequency response curve of *Single tuned voltage amplifier*.

**APPARATUS :**

- |   |            |
|---|------------|
| 1. Regulated power supply ( RPS ) -----   | 1 No.      |
| 2. Cathode Ray Oscilloscope ( CRO ) ----- | 1 No.      |
| 3. Function generator -----               | 1 No.      |
| 4. Decade Inductance box (DIB) -----      | 1 No.      |
| 5. Decade capacitance box (DCB) -----     | 1 No.      |
| 6. Probes -----                           | 1 No.      |
| 7. Bread board -----                      | 1 No.      |
| 8. Connecting wires -----                 | A few Nos. |

**COMPONENTS :**

- |                                |       |
|--------------------------------|-------|
| 1. Transistor BC 547 -----     | 1 No. |
| <b>2. Capacitors :</b>         |       |
| i). 10 $\mu\text{F}$ -----     | 1 No. |
| ii). 22 $\mu\text{F}$ -----    | 2 No. |
| <b>3. Resistors :</b>          |       |
| i). 100 $\text{K}\Omega$ ----- | 1 No. |
| ii). 10 $\text{K}\Omega$ ----- | 1 No. |
| iii). 100 $\Omega$ -----       | 1 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

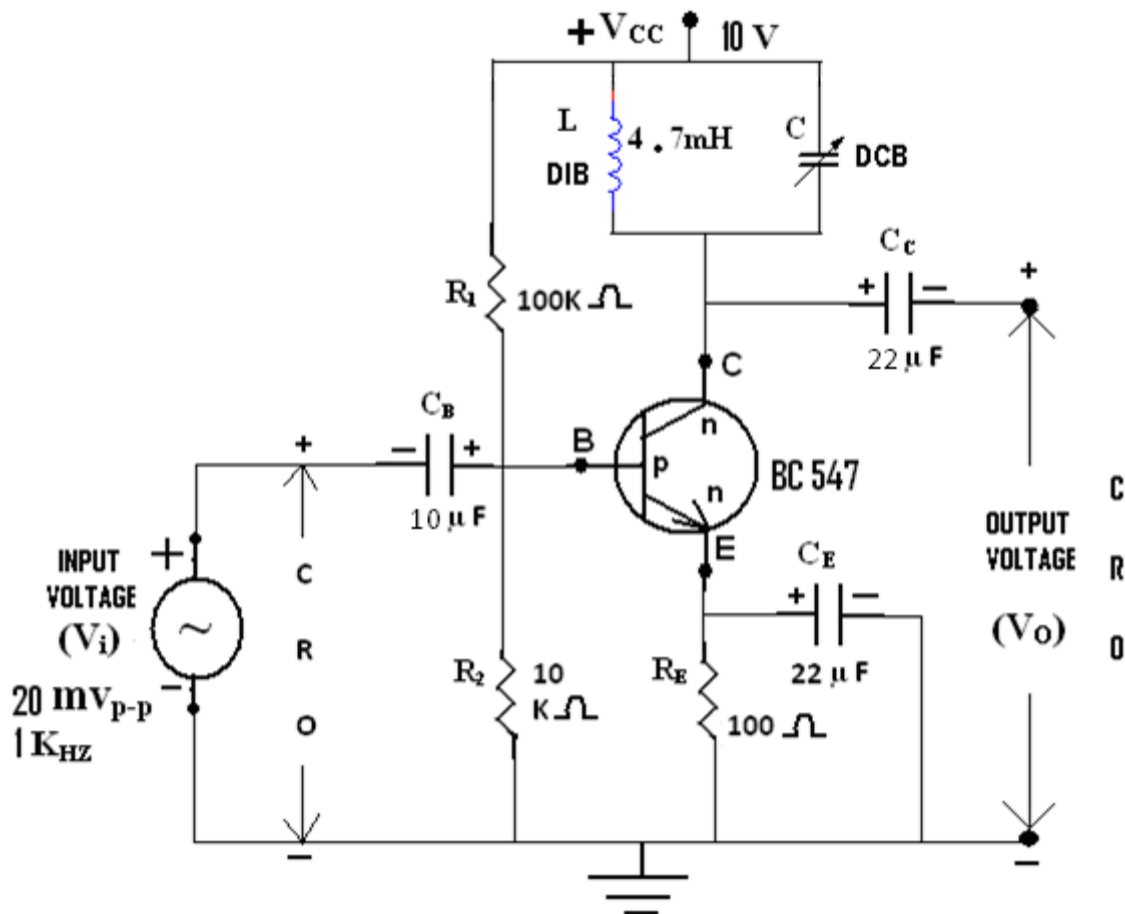
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of single tuned voltage amplifier.

**THEORETICAL CALCULATIONS :**1). When  $L=4.7\text{mH}$ ,  $f_r=10\text{KHz}$ , Then  $C=?$ 

$$\text{We have } f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{OR } C = \frac{1}{[2\pi f_r \sqrt{L}]^2}$$

$$\text{OR } C = \frac{1}{4\pi^2} \times \frac{1}{f_r^2 L} \quad \text{OR } C = \frac{0.0253}{f_r^2 L}$$

$$C = \frac{0.0253}{[10 \times 10^3]^2 \times 4.7 \times 10^{-3}}$$

$$= 54\text{Kpf OR } 54\text{ nF}$$

2). When  $L=4.7\text{mH}$ ,  $f_r=50\text{KHz}$ , Then  $C=?$ 

$$\text{We have } C = \frac{0.0253}{f_r^2 L}$$

$$= \frac{0.0253}{[50 \times 10^3]^2 \times 4.7 \times 10^{-3}}$$

$$= 2.16\text{Kpf OR } 2.16\text{ nF}$$

**PROCEDURE :**

1. We have connected the circuit as per the circuit diagram which is shown above. Initially connected the CRO across the function generator as per shown in the circuit diagram to set the input signal.
2. Switched *ON* the *CRO* and *function generator*.
3. Applied the input signal as *sine wave form* having the values of  $20\text{m}_{\text{p-p}}$ , 1KHz. from the function generator by observing in the CRO.
4. Kept the amplitude of the input signal as constant as  $20\text{mV}_{\text{p-p}}$  for all frequency steps until the experiment would completed.
5. Later removed the CRO and connected it across the capacitor  $C_C$  to observe the peak to peak output voltage.
6. Now set the  $C=54\text{Kpf}$  and  $L=4.7\text{mH}$  to take readings in tabular form-1
7. Switched *ON* the *RPS* and kept the 10V as  $V_{CC}$ .
8. Initially varied the frequency of input signal until the maximum output voltage could obtained, and noted this to the corresponding frequency value in the tabular form -1 .
9. Later calculated and noted the peak to peak output voltage to the remaining corresponding frequency values which are available in the tabular form-1.
10. Later set the  $C=2.16\text{Kpf}$  and  $L=4.7\text{mH}$  to take readings in tabular form-2
11. Repeat the same procedure from point 8 to 9.
12. Now calculated and noted down the values of *voltage gain* ( $A_V$ ) and *gain in dB* to the corresponding values of *output voltage* ( $V_o$ ) & *input voltage* ( $V_i$ ) by using the formulas given below,  

$$\text{Voltage gain } (A_V) = V_o / V_i \text{ and } \text{Gain in dB} = 20\log_{10}(A_V).$$
 These values has been noted in the both tabular forms.
13. Plotted the graphs for both tabular forms (frequency response curves) as per given below,
  - a). frequency on X-axis & gain in dB on Y-axis.
  - b). frequency on X-axis & voltage gain on Y-axis.
14. Calculated and noted the *band width* & *resonant frequency* from both frequency response curves by using the following formula,

$$\text{Band width} = f_2 - f_1.$$

**TABULAR FORM – 1:**

When  $f_r = 10\text{KHz}$ . ,  $C = 54\text{Kpf}$ ,  $L = 4.7\text{mH}$

Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in V	Voltage gain ( $A_V$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_V)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	5 KHz.			
5	20				
6	20	20KHz.			
7	20	50KHz.			
8	20	100 KHz.			
9	20	200 KHz.			
10	20	500 KHz.			
11	20	1 MHz.			

**TABULAR FORM – 2 :**


When  $f_r = 50 \text{ KHz.}$  ,  $C = 2.16 \text{ Kpf}$ ,  $L = 4.7\text{mH}$

Sl. No.	Input voltage ( $V_i$ ) in mV	Frequency in Hz / KHz.	Output Voltage ( $V_o$ ) in V	Voltage gain ( $A_v$ ) = $V_o / V_i$	Gain in dB = $20\log_{10}(A_v)$
1	20	10 Hz.			
2	20	500 Hz.			
3	20	1 KHz.			
4	20	20KHz.			
5	20				
6	20	60KHz.			
7	20	100 KHz.			
8	20	200 KHz.			
9	20	500 KHz.			
10	20	1 MHz.			

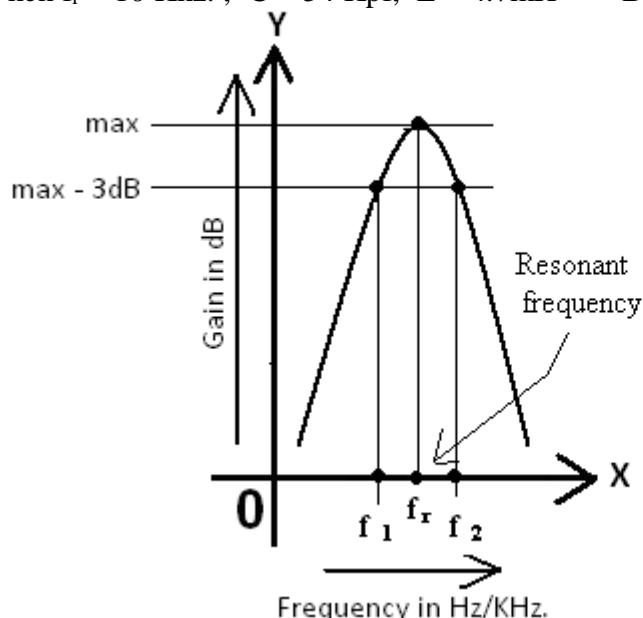
**EXPECTED GRAPH :**

The following graphs shows the frequency response curve for *single tuned voltage amplifie*

A). When  $f_r = 10 \text{ KHz.}$  ,  $C = 54 \text{ Kpf}$ ,  $L = 4.7\text{mH}$



B). When  $f_r = 50 \text{ KHz.}$  ,  $C = 2.16 \text{ Kpf}$ ,  $L = 4.7\text{mH}$

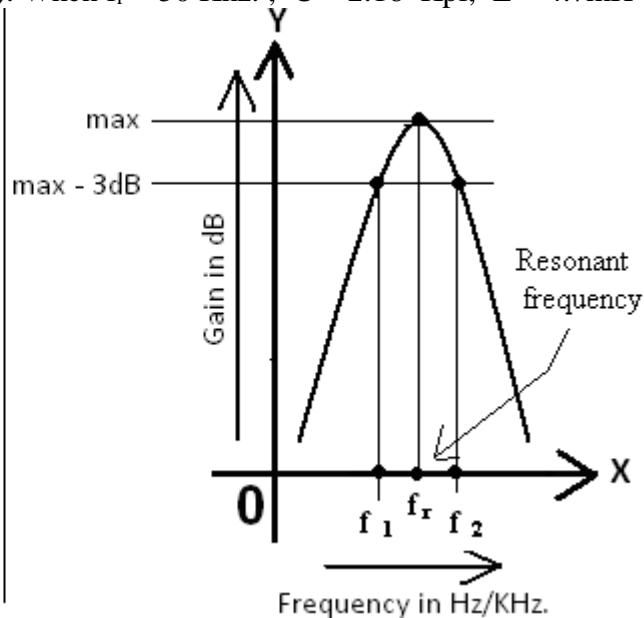**PRACTICAL CALCULATIONS :**

When $f_r = 10 \text{ KHz.}$ , $C = 54 \text{ Kpf}$ , $L = 4.7\text{mH}$	When $f_r = 50 \text{ KHz.}$ , $C = 2.16 \text{ Kpf}$ , $L = 4.7\text{mH}$
1). Band width = $f_2 - f_1$ =	1). Band width = $f_2 - f_1$ =
2). Resonant frequency ( $f_r$ ) =	2). Resonant frequency ( $f_r$ ) =

**TABULAR FORM -3 :**

The following tabular form shows the comparison between the theoretical and practical resonant frequency values.

Sl.No.	Inductor (L) (Note down from the theoretical calculations)	Capacitor (C) (Note down from the theoretical calculations)	Theoretical Resonant frequency ( $f_r$ ) (Note down from the theoretical calculations)	Practical Resonant frequency ( $f_r$ ) (Note down from the graph)	Max. voltage gain in dB at resonant frequency. (Note down from the graph)
1.	4.7mH	54Kpf	10KHz.		
2.	4.7mH	2.16Kpf	50KHz.		

**CONCLUSION :**

If I observed in the tabular form-3 the voltage gain of the output signal is maximum when the practical resonant frequency value is approximately equal to the theoretical resonant frequency value.

**APPLICATIONS :**

Mainly uses in the radio receivers to tuned the appropriate signal / station which is transmitted in relay station.

**RESULT :**

I have drawn the frequency response curve and calculated the values of band width, and resonant frequency of a *single tuned voltage amplifier*.

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.





**Experiment No. : 7****Date :**

**Name of the Experiment : CLASS A SERIES - FED POWER AMPLIFIER**  
**Using Hardware**

**AIM :**

1. To draw the output signal (sine wave form) on the graph of a given *Class-A series-fed power amplifier*.
2. To calculate the conversion efficiency of given *amplifier*.

**APPARATUS :**

1. Regulated power supply ( RPS ) ----- 1 No.
2. Cathode Ray Oscilloscope ( CRO ) ----- 1 No.
3. Function generator ----- 1 No.
4. Probes ----- 1 No.
5. **Ammeters :**
  - i). (0-10) mA Digital / Analog DC Type --- 1 No.
3. Bread board ----- 1 No.
4. Connecting wires ----- A few Nos.

**COMPONENTS :**

1. Transistor BC 547 ----- 1 No.
2. **Resistors :**
  - ii).  $1K\Omega$  ----- 1 No.
  - iii).  $10K\Omega$  ----- 1 No.
  - iv).  $47K\Omega$  ----- 1 No.
3. **Capacitors :**
  - i).  $10\mu F$  ----- 1 No.
  - i i).  $22\mu F$  ----- 2 No.

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

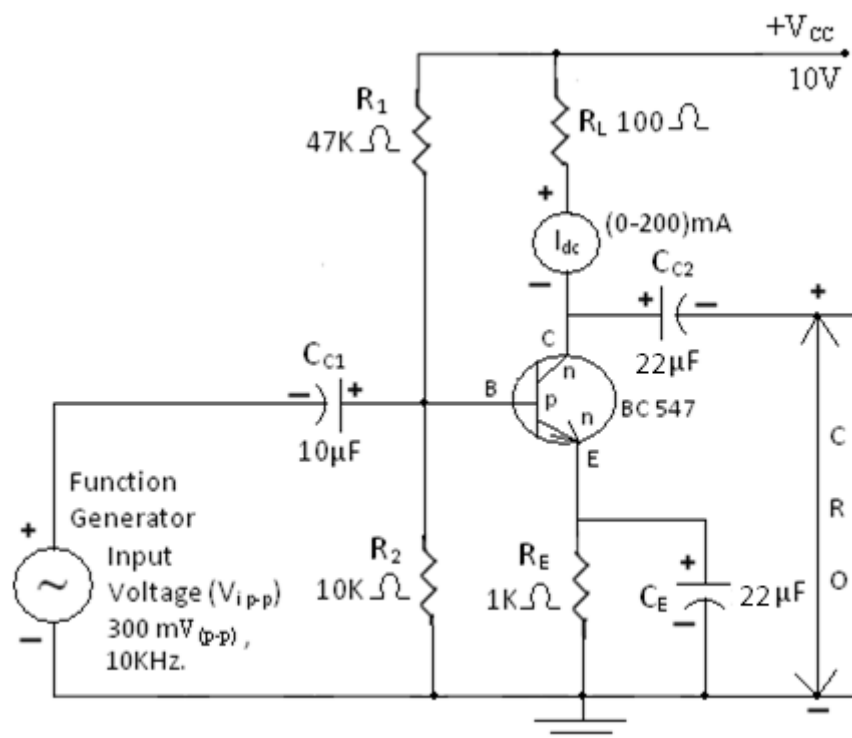
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Class A Series-fed Power Amplifier

**PRACTICAL CALCULATIONS :**

The practical calculations are shown in the following tabular form,


Sl.No.	Name of the parameter	Value
01.	Input Voltage ( $V_i$ ) <sub>p-p</sub> ( In mV).	300
02.	Input frequency (In Khz.).	10
03.	Supply DC Voltage ( $V_{CC}$ ) (in Volts.)	10
04.	Output voltage $V_{O(p-p)}$ (In volts.).	
05.	Time period (T) for output signal (In ms)	
06.	Frequency for output signal = $1/T$ (In Khz.)	
07.	Collector dc current ( $I_{dc}$ ) (At quiescent condition i.e. When no input signal is applied) (In mA.).	
08.	Collector DC current when sine wave (AC) signal is applied as input signal ( $I_{ac}$ )	
09.	Input DC power $P_i(dc) = I_{dc} \times V_{CC}$ (In Watts).	
10.	Output ac power $P_o(ac) = \frac{V_{O(p-p)}^2}{8R_L}$ (In Watts)	
11.	% of efficiency ( $\eta$ ) = $[ P_o(ac) / P_i(dc) ] \times 100 =$	
12.	Typical Max. efficiency ( $\eta$ ) =	25.40%

**PROCEDURE :**

1. Connections are made as per the circuit diagram.
2. Initially connected the *CRO* across the *Function generator*.
3. Switched **ON** the Cathode ray oscilloscope (CRO) and Function generator.
4. Applied the  $300\text{ mV}_{p-p}$ ,  $10\text{ KHz}$  sine wave signal to the circuit from the *Function generator* by observing on the *crt* of the *CRO*.
5. Later connected the *CRO* across  $R_L$  i.e at output side.
6. Now switched **ON** the Regulated Power Supply (RPS) and apply the *supply voltage*  $10\text{V}$  as  $V_{CC}$  to the circuit as per shown in the figure.
7. Observed the *sine wave* signal on the CRT of the CRO and draw this signal on the graph sheet.
8. Now noted down the *collector dc current*  $I_{(dc)}$  at *Quiescent* condition i.e. when no signal is applied and *supply voltage* ( $V_{CC}$ ) by disconnected the *function generator* from the circuit against the corresponding columns in the tabular form of *practical calculations*.
9. Switched **OFF** the *function generator*, *RPS*, *CRO*.
10. Noted down the *Input voltage* ( $V_i$ ), *Input frequency* against the corresponding columns in the tabular form.
11. Calculated the *output voltage* ( $V_{o_{p-p}}$ ), *time period* ( $T$ ), *frequency* ( $f$ ) from the graph, and noted down these values against the corresponding columns in the tabular form.
12. Later calculated the *Input dc power*  $P_i(dc)$ , *output ac power*  $P_o(ac)$  and *% of efficiency* ( $\eta$ ) by using the formulas which are mentioned in the corresponding columns in the tabular form.
13. Noted that The practical value should be less than the *Typical Max. efficiency value* i.e. **25.4%**.

**EXPECTED GRAPH :**

The following graph shows for *Class A power amplifier*.

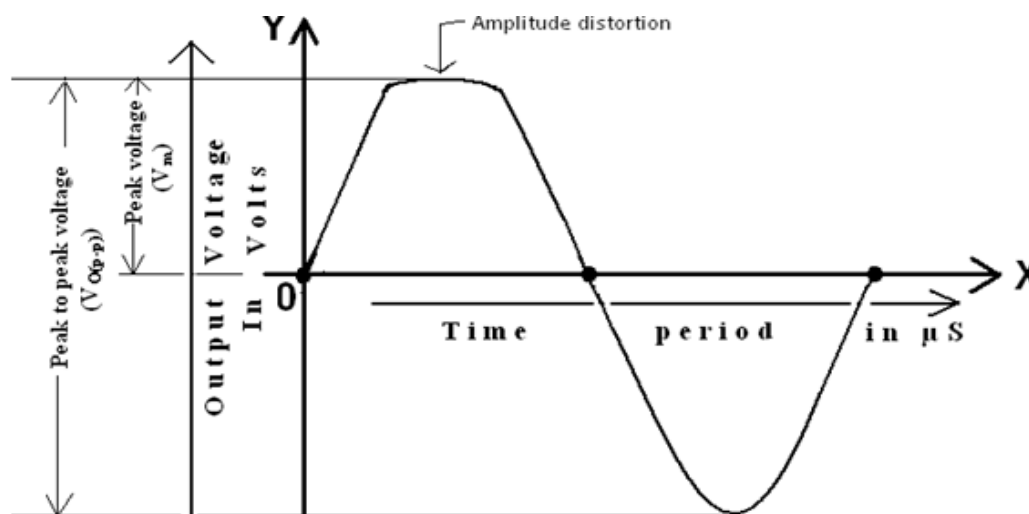**RESULT :**

I have drawn the graph for output signal and calculated the conversion efficiency of a given *Class-A series-fed power amplifier*.

**VIVA VOICE Questions :**

*Note* : The questions which are avail in *Software section-A* under the same experiment are applicable here also.



**Experiment No. : 8****Date :****Name of the Experiment : COMPLEMENTARY SYMMETRY CLASS B PUSH –  
PUSH POWER AMPLIFIER****(Using hardware)****AIM :**

1. To draw the output signal (sine wave form) on the graph of a given *complementary symmetry push-pull class-B push-pull power amplifier*.
2. To study the operation of this *amplifier*.
3. To calculate the conversion efficiency of a given *power amplifier*.

**APPARATUS :**

1. Regulated power supply ( RPS ) ----- 1 No.
2. Cathode Ray Oscilloscope ( CRO ) ----- 1 No.
3. Function generator ----- 1 No.
4. Probes ----- 1 No.
5. **Ammeters :**
  - i). (0-10) mA Digital / Analog DC Type ----- 1 No.
3. Bread board ----- 1 No.
4. Connecting wires ----- A few Nos.

**COMPONENTS :**

1. **Transistors**
  - i). BC 547 ----- 1 No.
  - ii). BC 557 ----- 1 No.
2. **Resistors :**
  - i). 220 K $\Omega$  ----- 2 No.
  - ii). 18 K $\Omega$  ----- 2 No.
  - iii). 1 K $\Omega$  ----- 1 No.
  - iv). 10 $\Omega$  ----- 3 No.
3. **Capacitors :**
  - i). 10  $\mu$ F ----- 2 No.

**THEORY :**

*Note : Theory had given in Software section-A of this same experiment. That same theory can apply here also.*

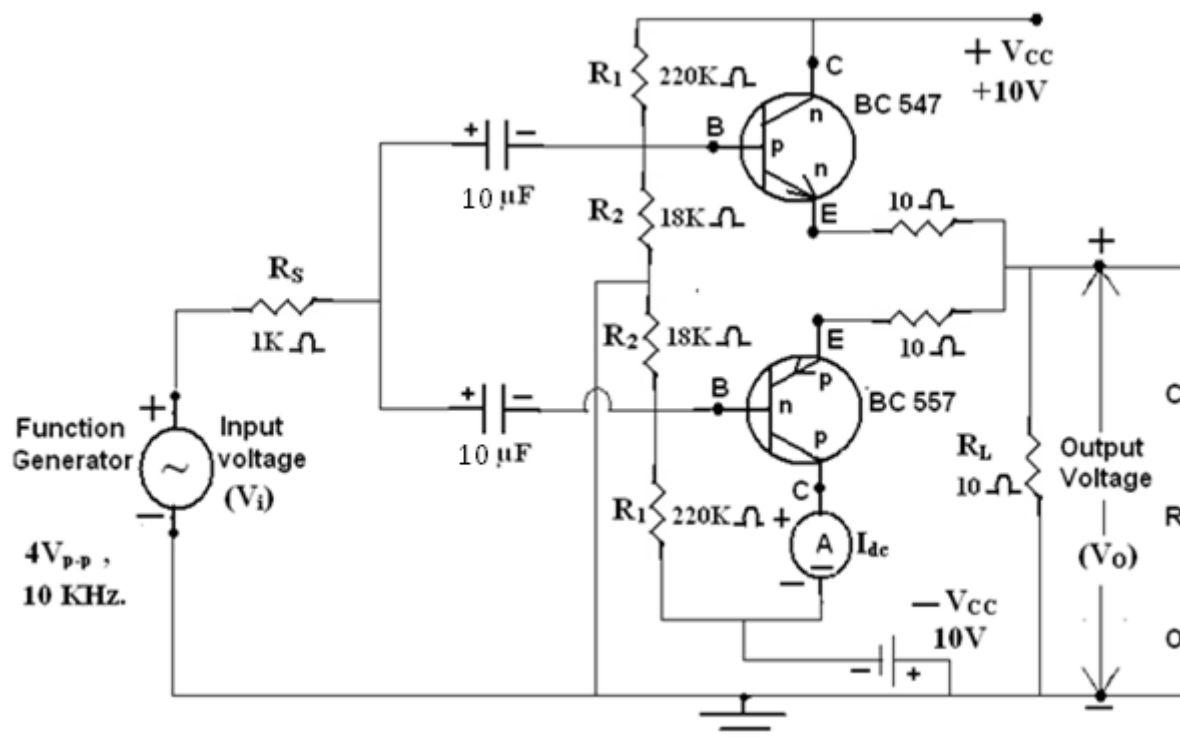
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Class-B complimentary symmetry power amplifier.

**PROCEDURE :**

1. Connections are made as per the circuit diagram.
2. Initially connected the *CRO* across the *Function generator*.
3. Switched **ON** the Cathode ray oscilloscope (*CRO*) and *Function generator*.
4. Applied the  $4V_{p-p}$ ,  $10\text{ KHz}$  sine wave signal to the circuit from the *Function generator* by observing on the *crt* of the *CRO*.
5. Later connected the *CRO* across  $R_L$  i.e. at output side.
6. Now switched **ON** the Regulated Power Supply (*RPS*) and apply the supply voltage  $+10V$  from one channel ( $+V_{CC}$ ) and  $-10V$  from another ( $-V_{CC}$ ) to the circuit as per shown in the figure.
7. Observed the sine wave signal on the *CRT* of the *CRO* and draw this signal on the graph sheet.
8. Now noted down the collector dc current  $I_{dc}$  at Quiescent condition i.e. when no signal is applied by disconnected the *function generator* from the circuit and supply voltage ( $V_{CC}$ ) against the corresponding columns of the tabular form of practical calculations.
9. Noted down the Input voltage ( $V_i$ ), Input frequency against the corresponding columns of the tabular form of practical calculations.
10. Switched **OFF** the *function generator*, *RPS*, *CRO*.
11. Calculated the peak to peak voltage ( $V_{o-p-p}$ ), peak voltage ( $V_m$ ), time period ( $T$ ), frequency ( $f$ ) from the graph, and noted down these values against the corresponding columns of the tabular form of practical calculations.
12. Later calculated the Input dc power  $P_i(dc)$ , output ac power  $P_o(ac)$  and % of efficiency ( $\eta$ ) by using the formulas which are mentioned in the corresponding columns of the tabular form of practical calculations.
13. Noted that The practical value should be less than the Typical Max. efficiency value i.e. 78.5%.


**PRACTICAL CALCULATIONS :**

The practical calculations for the parameters are shown in the following tabular form,

SlNo.	Name of the parameter	Value
01.	Input peak to peak voltage ( $V_i$ ) (In Volts).	4
02	Input frequency (In Khz.).	10
03	Positive supply DC Voltage ( $+V_{CC}$ ) (in Volts.)	10
	Negative supply DC Voltage ( $-V_{CC}$ ) (in Volts.)	10
04	Peak to peak voltage of output $V_{O(p-p)}$ (In volts.).	
05	Peak voltage of output ( $V_m$ ) = $V_{O(p-p)} / 2$ (In volts.).	
06	Time period (T) for output signal (In ms)	
07	Frequency for output signal = $1/T$ (In Khz.)	
08	Collector dc current ( $I_{dc}$ ) (At quiescent condition i.e. When no input signal is applied) (In mA.).	
09	Collector DC current when sine wave (AC) signal is applied as input signal ( $I_{ac}$ )	
10	Input DC power $P_i(dc) = I_{dc} \times V_{CC}$ (In mWatts).	
11	Output ac power $P_o(ac) = \frac{V_m^2}{2R_L}$ (In mWatts) =	
12	% of efficiency ( $\eta$ ) = $\frac{P_o(ac)}{P_i(dc)} \times 100$	
13	Typical Max. efficiency ( $\eta$ ) =	78.50 %

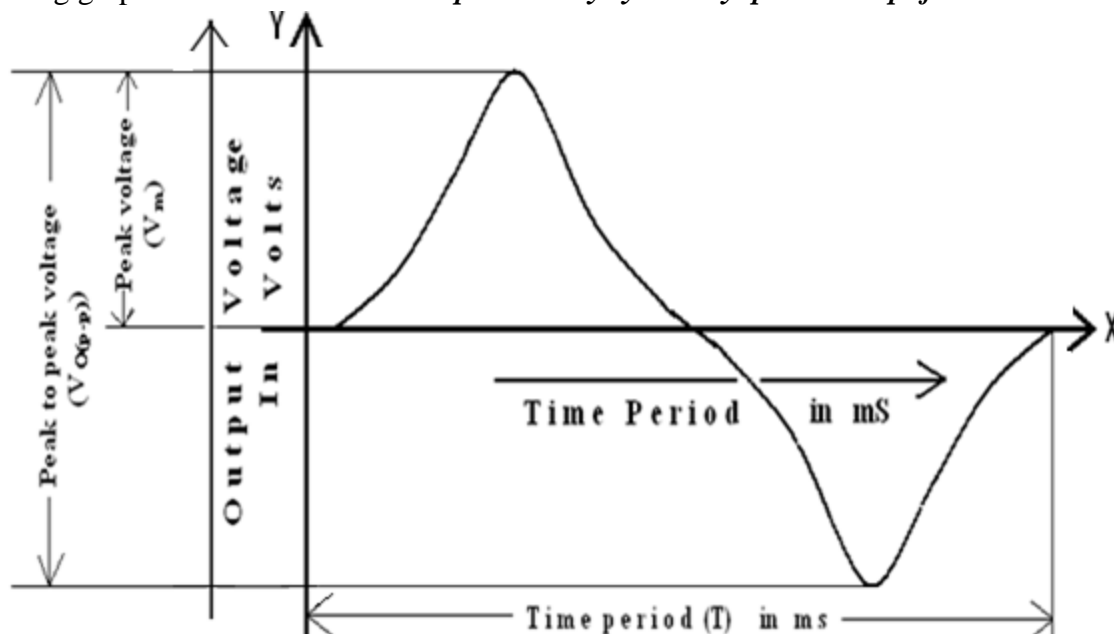**EXPECTED GRAPH :**

The following graph shows for *Class B complementary symmetry power amplifier*.



**RESULT :**

I have drawn the graph for output signal and calculated the conversion efficiency of given *complementary symmetry Class-B push-pull power amplifier*.

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.



**Experiment No. : 9****Date :****Name of the Experiment : RC PHASE SHIFT OSCILLATOR**

(By using hardware)

**AIM :**

To draw the *sine wave form* and to calculate its frequency values of a given *RC Phase shift Oscillator*.

**APPARATUS :**

- |   |       |
|---|-------|
| 1. Regulated power supply ( RPS ) ----- | 1 No. |
| 2. Cathode ray oscilloscope -----       | 1 No. |
| 3. Decade Resistance Box ( DRB ) -----  | 1 No. |
| 4. Decade Capacitance Box ( DCB ) ----- | 3 No. |
| 5. Bread board -----                    | 1 No. |
| 6. Probes -----                         | 1 No. |
| 7. Connecting wires -----               | 1 No. |

**COMPONENTS :**

- |                                     |       |
|-------------------------------------|-------|
| 1. Resistors : 1K $\Omega$ -----    | 1 No. |
| 4.7 K $\Omega$ -----                | 1 No. |
| 47 K $\Omega$ -----                 | 1 No. |
| 10 K $\Omega$ -----                 | 3 No. |
| 2. Capacitors : 0.047 $\mu$ F ----- | 1 No. |
| 1000 $\mu$ F -----                  | 1 No. |
| 3. Transistor : BC547 -----         | 1 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

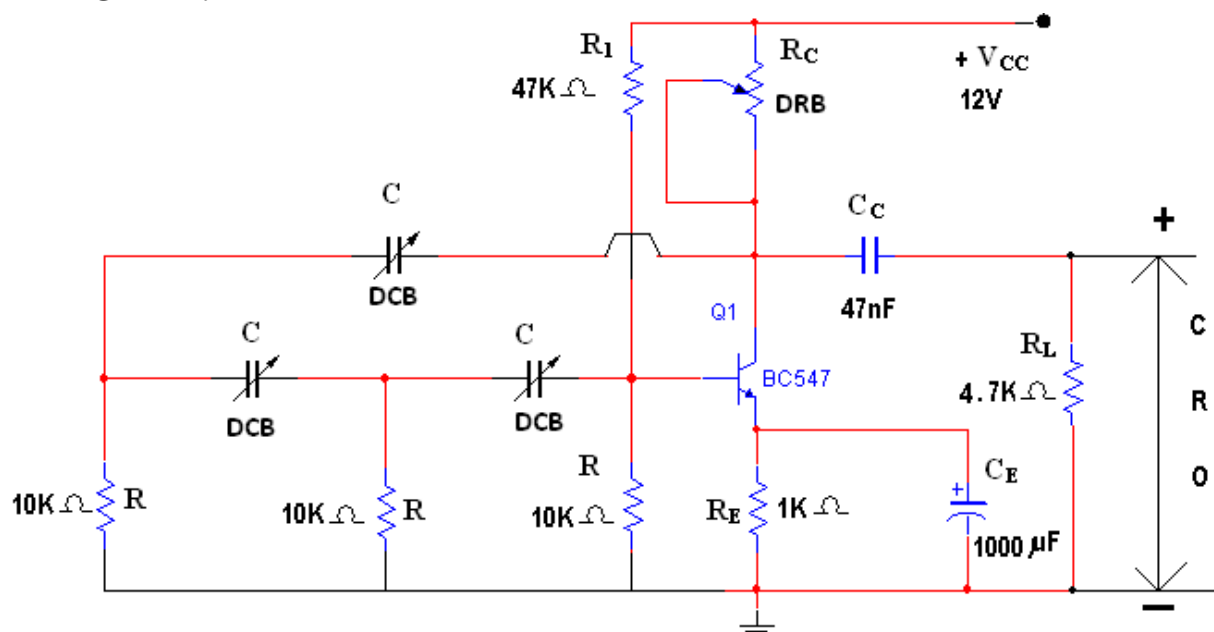
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of RC phase shift oscillator.

**PROCEDURE :**

1. Made the connections as per the circuit diagram.
2. Kept the  $V_{CC}$  value as 12V.
3. Kept the Capacitor  $C$  values as 1nF (0.001μF or 1Kpf) in DCB.
4. Varied the  $R_C$  (i.e. Appx. 4.3KΩ) until we get *sine wave form* which consist the  $V_{O(p-p)}$  is approximately 6V because this circuit is designed to get the output voltage as  $6V_{(p-p)}$  in the CRO.
5. Now noted the value of  $R_C$  to the corresponding  $C$  value in tabular form.
6. We observed the *Sine wave form* as a output signal in the CRO.
7. Now calculated and noted the *theoretical frequency value* ( $f_o$ ) to the corresponding  $C$  value in the tabular form by using the formula given below,

$$f_o = \frac{1}{2\pi RC \sqrt{6+4(R_C/R)}}$$

8. Drawn the *sine wave form* on the graph by taking the *time period* on X-axis and *amplitude* ( $V_{O(p-p)}$ ) on Y-axis.
9. Calculated the frequency and output voltage ( $V_{O(p-p)}$ ) values from the graph then noted in the Columns of *practical frequency* and *output voltage* in the tabular form respectively.
10. Repeat the same procedure from points 4 to 9 for corresponding  $C$  values which are given below,
  - a). 2.2 nF ( 0.0022 μF or 2.2Kpf ).
  - b). 3.3 nF ( 0.0033 μF or 3.3Kpf ).
  - c). 10.0 nF ( 0.01 μF or 10Kpf ).
11. Switch *OFF* the RPS and CRO.
12. We compared that *theoretical frequency value* ( $f_o$ ) and *practical frequency* values are approximately same.


**TABULAR FORM / CALCULATIONS :**

Sl. No.	Resistor (R) In KΩ	Capacitor (C) In Kpf	$R_C = R_{\text{selected}} - \left[ \frac{\text{Setting in \%} \times R_{\text{detected}}}{100} \right]$ In KΩ	Theoretical frequency ( $f_o$ ) $\frac{1}{2\pi RC \sqrt{6+4(R_C/R)}}$ In Hz/KHz.	Practical Time Period (In μS)	Practical Frequency In Hz/KHz.	Output Voltage ( $V_{O(p-p)}$ ) In Volts
1	10	1					
2	10	2.2					
3	10	3.3					
4	10	10					

*Note:* If I observed in the tabular form, for which the C value of 10nF the peak to peak output voltage ( $V_{O(p-p)}$ ) is 4V approximately, but this circuit is designed to get the ( $V_{O(p-p)}$ ) value as 6V approximately. So for this C value we can't consider. If we observed regarding to frequency value, when the C value is increases then the frequency value is decreases.

**EXPECTED WAVE FORM :**

The following waveform shows the output signal for *RC phase shift Oscillator*,

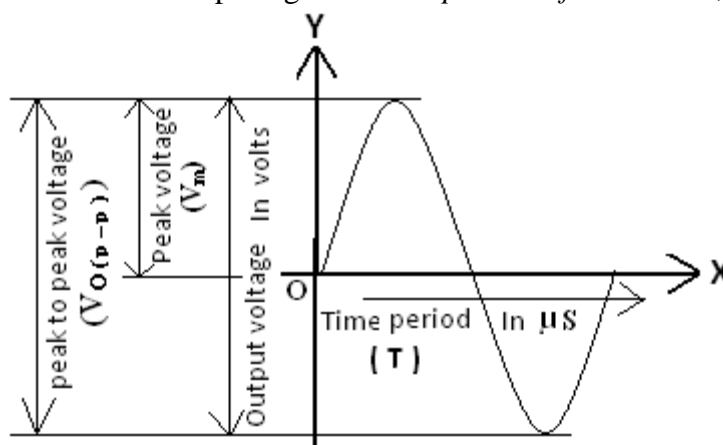**RESULT :**

I have drawn the output signal and calculated the frequency values of a given *RC phase shift oscillator*.

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.



**Experiment No. : 10****Date :****Name of the Experiment : COLPITTS OSCILLATOR**

(By using hardware)

**AIM :**

To draw the *sine wave form* and to calculate its frequency values of a given *Colpitts Oscillator*.

**APPARATUS :**

- |   |       |
|---|-------|
| 1. Regulated power supply ( RPS ) ----- | 1 No. |
| 2. Cathode ray oscilloscope -----       | 1 No. |
| 3. Decade Inductance Box ( DIB ) -----  | 1 No. |
| 4. Decade Capacitance Box ( DCB ) ----- | 1 No. |
| 5. Bread board -----                    | 1 No. |
| 6. Probes -----                         | 1 No. |
| 7. Connecting wires -----               | 1 No. |

**COMPONENTS :**

- |                                   |       |
|-----------------------------------|-------|
| 1. Resistors : 1K $\Omega$ -----  | 1 No. |
| 1.5 K $\Omega$ -----              | 1 No. |
| 10 K $\Omega$ -----               | 1 No. |
| 47 K $\Omega$ -----               | 1 No. |
| 2. Capacitors : 0.1 $\mu$ F ----- | 1 No. |
| 0.01 $\mu$ F -----                | 1 No. |
| 3. Transistor : BC547 -----       | 1 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

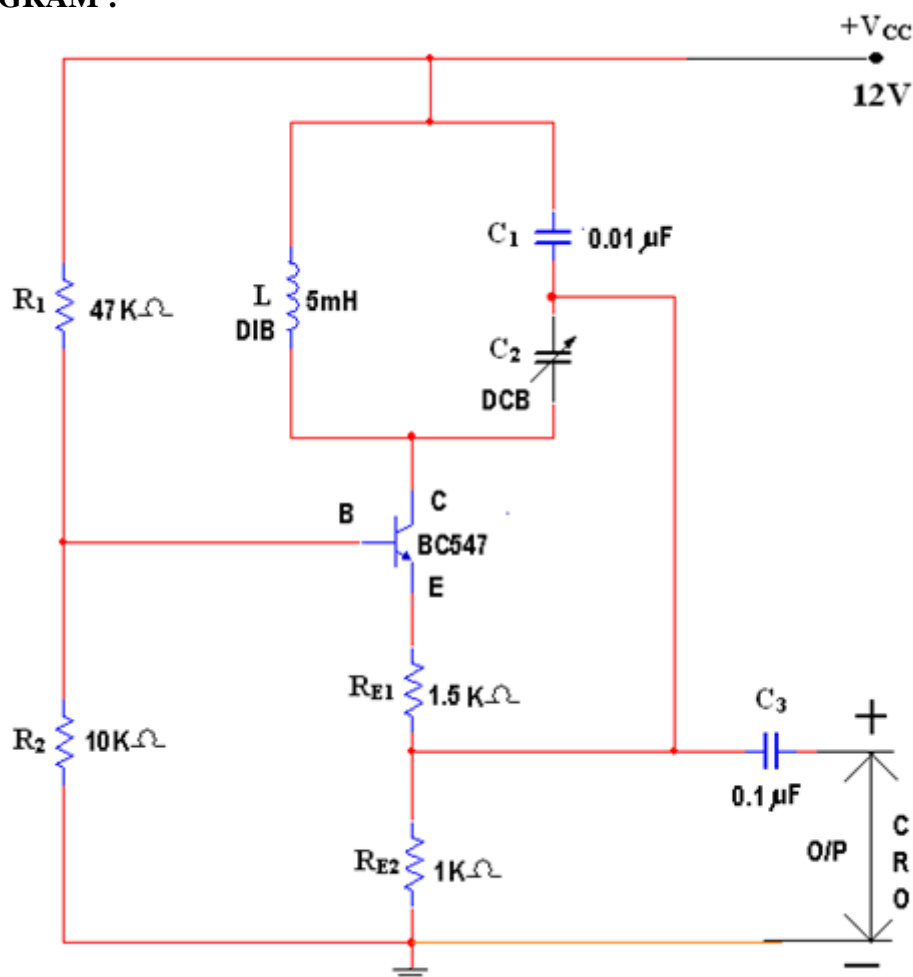
**CIRCUIT DIAGRAM :**

Figure: Circuit diagram of Colpitt's oscillator.

**PROCEDURE :**


1. Made the connections as per the circuit diagram.
2. Switched **ON** the RPS and CRO.
3. Set the  $V_{CC}$  value as 12V in RPS.
4. Set the inductance( $L$ ) value as 5mH in DIB .
5. Set the Capacitor  $C_2$  value as 1nF (0.001μF or 1Kpf) in DCB.
- 6.. We observed *Sine wave form* as a output signal in the CRO.
7. Drawn the *sine wave form* on the graph by taking the *time period* on X-axis and *amplitude( $V_{O(p-p)}$ )* on Y-axis.
8. Calculated the frequency and output voltage ( $V_{O(p-p)}$ ) values from the graph then noted in the columns of *practical frequency* and *output voltage* in the tabular form respectively.
9. Repeat the same procedure from points 5 to 7 for corresponding  $C_2$  values which are given below,
  - a). 2.2 nF ( 0.0022 μF or 2.2Kpf ).
  - b). 3.3 nF ( 0.0033 μF or 3.3Kpf ).
10. Switch **OFF** the RPS and CRO.
11. Finally calculated and noted down the *theoretical frequency value ( $F_o$ )* by using the formula,  $1 / (2\pi\sqrt{LC_T})$  in the tabular form.
12. I compared that *theoretical frequency value ( $F_o$ )* and *practical frequency* values are approximately same.

**TABULAR FORM / CALCULATIONS :**

Sl No.	Capa Citor (C <sub>1</sub> )	Capa Citor (C <sub>2</sub> )	Inductor (L) In mH	Total Capacitance (C <sub>T</sub> ) $C_1 C_2$ = $C_1 + C_2$ In nF	Theoretical Frequency (f <sub>0</sub> ) = $\frac{1}{2\pi\sqrt{LC_T}}$ In KHz	Practical – Time-Period. In μS	Practical frequency In KHz.	Output voltage (V <sub>O p-p</sub> ) In Volts.
1.	10Kpf	1Kpf	5					
2.	10Kpf	2.2Kpf	5					
3.	10Kpf	3.3Kpf	5					

**EXPECTED WAVEFORM :**

The following waveform shows the output signal for *Colpitts Oscillator*

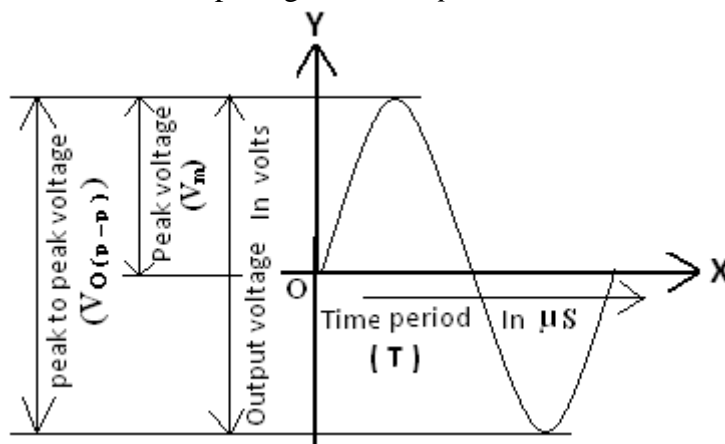**RESULT :**

I have drawn the output signal and calculated the frequency values of a given *Colpitts Oscillator*.

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.





# **PART – C**

**Beyond the Syllabus  
(Using Simulation software & Hardware)**



**Experiment No. : 11****Date :**

**Name of the Experiment : CE - CB CASCODE AMPLIFIER**  
**(Beyond the Syllabus-Using Software & Hardware)**

**AIM :**

- 1). To obtain the frequency response of *CE – CB cascade amplifier* using Software and Hardware
- 2). To calculate the band width of this amplifier.

**APPARATUS :****Software :**

1. System ..... 1 No.
2. Multisim software

**Hardware :**

- 1). Function generator(*FG*) ..... 1 No.
- 2). Cathode Ray Oscilloscope(*CRO*) ..... 1 No.
- 3). Regulated Power Supply (*RPS*) : (0-30)V, 1A Dual channel ..... 1 No.
- 4). Probes ..... 1 No.
- 5). Bread board ..... 1 No.
- 6). Connecting wires : ..... A few Nos.

**COMPONENTS :**


- 1). Transistor BC 547 ..... 1 No.
- 2) Carbon fixed resistors
 

a).	47K $\Omega$ , ½W	----- 1 No.
b).	40.2K $\Omega$	----- 1 No.
c).	10K $\Omega$ , ½W	----- 1 No.
d).	6.8 K $\Omega$ , ½W	----- 1 No.
e).	4.7 K $\Omega$ , ½W	----- 1 No.
f).	1 K $\Omega$ , ½W	----- 1 No.
- 3). Capacitors
 

g).	0.22 $\mu$ F	----- 3 No.
h).	33 $\mu$ F	----- 1 No.

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

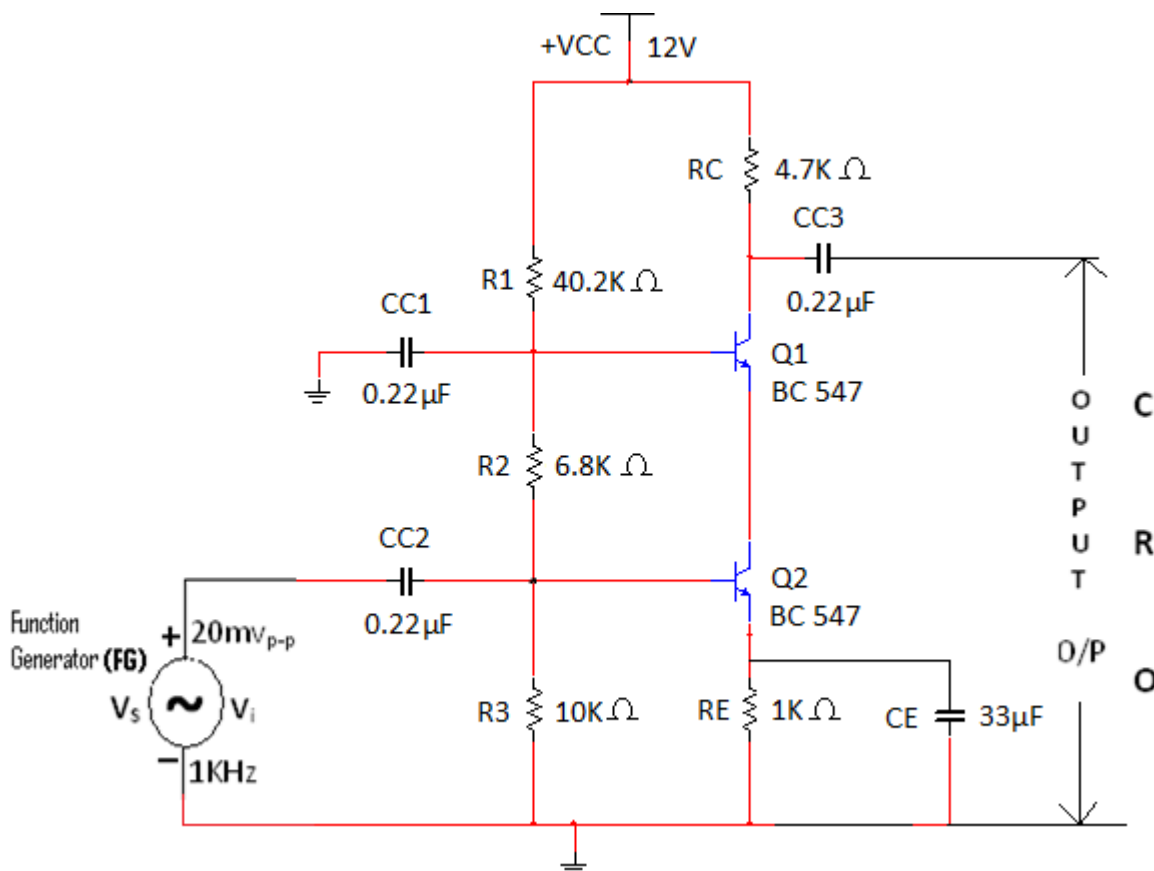**CIRCUIT DIAGRAM – SOFTWARE & HARDWARE :****PROCEDURE – SOFTWARE :**

1. We have picked up the components from the components bar as per above circuit.
2. Made the connections as per the above circuit diagram by using the components which we have picked up.
3. Set the input signal as *sine wave form* which is having the value  $20\text{mV}_{\text{P-P}}$  as constant in the function generator.
4. Initially set the input signal frequency value is  $1\text{KHz}$  in the function generator.
5. To simulate the circuit clicked on *run option* through *execute button* in *tool bar*.
6. We have seen the *sine wave* on the **CRO** screen as o/p signal.
7. Calculated the *peak to peak voltage* ( $V_{O(p-p)}$ ) and noted down in the tabular form Against the column of  $1\text{KHz}$ .
8. Stopped the simulation by clicked on *run option* through *execute button* in the *tool bar*.
9. Repeat the same procedure from points 7 to 9 for the corresponding frequency values by setting in the function generator for the following steps,  $20\text{Hz}$ ,  $100\text{Hz}$ ,  $200\text{Hz}$ ,  $1\text{KHz}$ ,  $200\text{KHz}$ ,  $400\text{KHz}$ ,  $600\text{KHz}$ ,  $920\text{KHz}$ ,  $1\text{MHz}$ ,  $100\text{MHz}$ ,  $500\text{MHz}$ . in the function generator.
10. Observed the graph for *frequency Vs amplitude* through the *AC Analysis*.
11. Finally shut down the system safely.
12. We have observed that, the graph which is drawn by manually is same to the graph which is obtained from the *AC Analysis*.
13. Now calculated and noted down the values of *voltage gain* ( $A_V$ ) and *gain in dB* to the corresponding values of *output voltage* ( $V_O$ ) & *input voltage* ( $V_i$ ) by using the formulas given below,

$$\text{Voltage gain } (A_V) = V_O / V_i \text{ and Gain in dB} = 20\log_{10}(A_V).$$

14). Plotted the graphs (frequency response curves) as per below

- frequency on X-axis & gain in dB on Y-axis.
- frequency on X-axis & voltage gain on Y-axis.

### PROCEDURE – HARDWARE :



- Connected the circuit as per the circuit diagram.
- Then switched ON the *function generator* and *CRO*; but don't switched ON the *RPS*.
- Now Kept the *AC/GND/DC* switch is at *AC* position.
- Initially kept the 1KHz. frequency by varying the frequency control in the *function generator*.
- Now applied the peak to peak amplitude of a sine wave is of  $20\text{mV}_{\text{p-p}}$  by varying the amplitude control in the *function generator* through observing in the *CRO*.
- Kept this input value as  $20\text{mV}_{\text{p-p}}$  constant up to the completion of the experiment  
Otherwise the wrong output would occurred.
- Now switched ON the *RPS* and set the 10V in it i.e.  $V_{\text{CC}} = 12\text{V}$ .
- Varied the different frequency steps of 20Hz, 100Hz, 200Hz, 1KHz, 200KHz, 400KHz, 600KHz, 920KHz, 1MHz. by adjusted the frequency control in the *function generator* and noted down the corresponding values of output signal i.e. peak to peak amplitude of sine wave by observing in the *CRO*.
- Now switched OFF the *RPS*, *function generator* and *CRO*.
- Then calculated the *voltage gain*  $A_V = V_O/V_i$  & *gain in dB*  $= 20\log_{10}(A_V)$  and noted down the values in the specified columns of the tabular column.
- Plotted the graphs (frequency response curves) as per below,
  - frequency on X-axis & gain in dB on Y-axis.
  - frequency on X-axis & voltage gain on Y-axis.
- Calculated the *band width* from the above two (frequency response curves) graphs by using the formula  $f_2 - f_1$  which is given under the heading of *parameters*.

### TABULAR COLUMNS :

Input Voltage ( $V_i$ ) = 20 mV <sub>p-p</sub> (0.02V) is constant for all readings.									
For Software :					For Hardware :				
Sl. No.	Frequency In Hz/KHz.	Output Voltage ( $V_O$ ) In mVolts.	Voltage gain $A_V = V_O/V_i$	Gain in dB = $20\log_{10}(A_V)$		Frequency In Hz/KHz.	Output Voltage ( $V_O$ ) In mVolts.	Voltage gain $A_V = V_O/V_i$	Gain in dB = $20\log_{10}(A_V)$
1	20 Hz.								
2	100 Hz.								
3	200 Hz.								
4	1 KHz.								
5	200KHz.								
6	400KHz.								
7	600KHz.								
Table form will continue in next page									

-----Table form Continued -----

Input Voltage ( $V_i$ ) = 20 mV <sub>P-P</sub> (0.02V) is constant for all readings.									
For Software :					For Hardware :				
Sl. No.	Frequ- ency In Hz/KHz.	Output Voltage ( $V_o$ ) In mVolts.	Voltage gain $A_v = V_o/V_i$	Gain in dB = $20\log_{10}(A_v)$		Frequ- ency In Hz/KHz.	Output Voltage ( $V_o$ )In mVolts.	Voltage gain $A_v = V_o/V_i$	Gain in dB = $20\log_{10}(A_v)$
8	920KHz.								
9	1 MHz.								
10	100 MHz					-----	-----	-----	-----
11	500MHz.					-----	-----	-----	-----

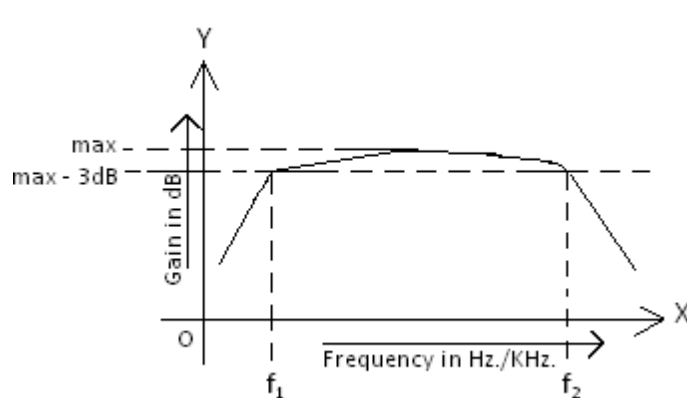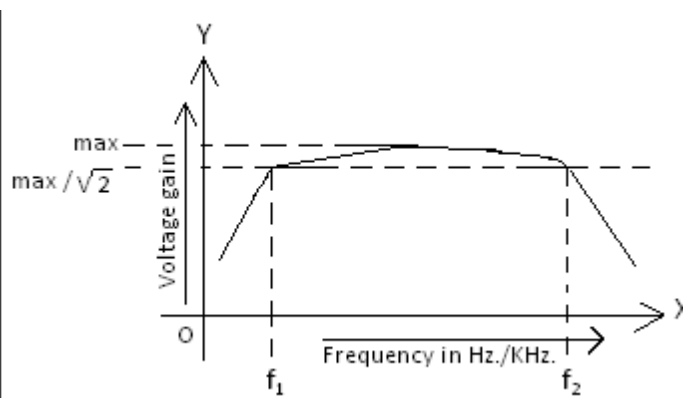**EXPECTED GRAPHS – SOFTWARE & HARDWARE :****A). Frequency response curve****For frequency verses gain in dB.****B). Frequency response curve****For frequency verses voltage gain.****PARAMETERS – SOFTWARE & HARDWARE :**

- 1). Band width of frequency response curve for frequency verses gain in dB. =  $f_2 - f_1$
- 2) Band width of frequency response curve for frequency verses voltage gain =  $f_2 - f_1$

**RESULT –SOFTWARE & HARDWARE :**

We have obtained the frequency response curves of *CE-CB cascode Amplifie* for frequency verses gain in dB & frequency verses voltage gain and calculated the band width of both of them. The band width values are given below,

- 1). Band width of frequency response curve for frequency verses gain in dB. =
- 2) Band width of frequency response curve for frequency verses voltage gain =

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.

**Experiment No. : 12****Date :****Name of the Experiment :****ASTABLE MULTIVIBRATOR**  
**(Beyond the Syllabus-Using Software & Hardware)****AIM :**

To conduct and verify the Astable multi vibrator and to draw the waveforms using software and hardware

**APPARATUS :**

- |                                   |       |       |
|-----------------------------------|-------|-------|
| 1. System with Multisim software  | ----- | 1 No. |
| 2. Regulated power supply ( RPS ) | ----- | 1 No. |
| 3. Cathode ray oscilloscope       | ----- | 1 No. |
| 4. Function Generator             | ----- | 1 No. |
| 5. Bread board                    | ----- | 1 No. |
| 6. Probes                         | ----- | 1 No. |
| 7. Connecting wires               | ----- | 1 No. |

**COMPONENTS :**

- |                                     |       |       |
|-------------------------------------|-------|-------|
| 1. Resistors : 1K $\Omega$          | ----- | 2 No. |
| 10 K $\Omega$                       | ----- | 2 No. |
| 100 K $\Omega$                      | ----- | 2 No. |
| 2. Capacitors : 0.1 $\mu$ F / 100nF | ----- | 2 No. |
| 3. Transistor : BC547               | ----- | 2 No. |

**THEORY :**

*Note :* Theory had given in *Software section-A* of this same experiment. That same theory can apply here also.

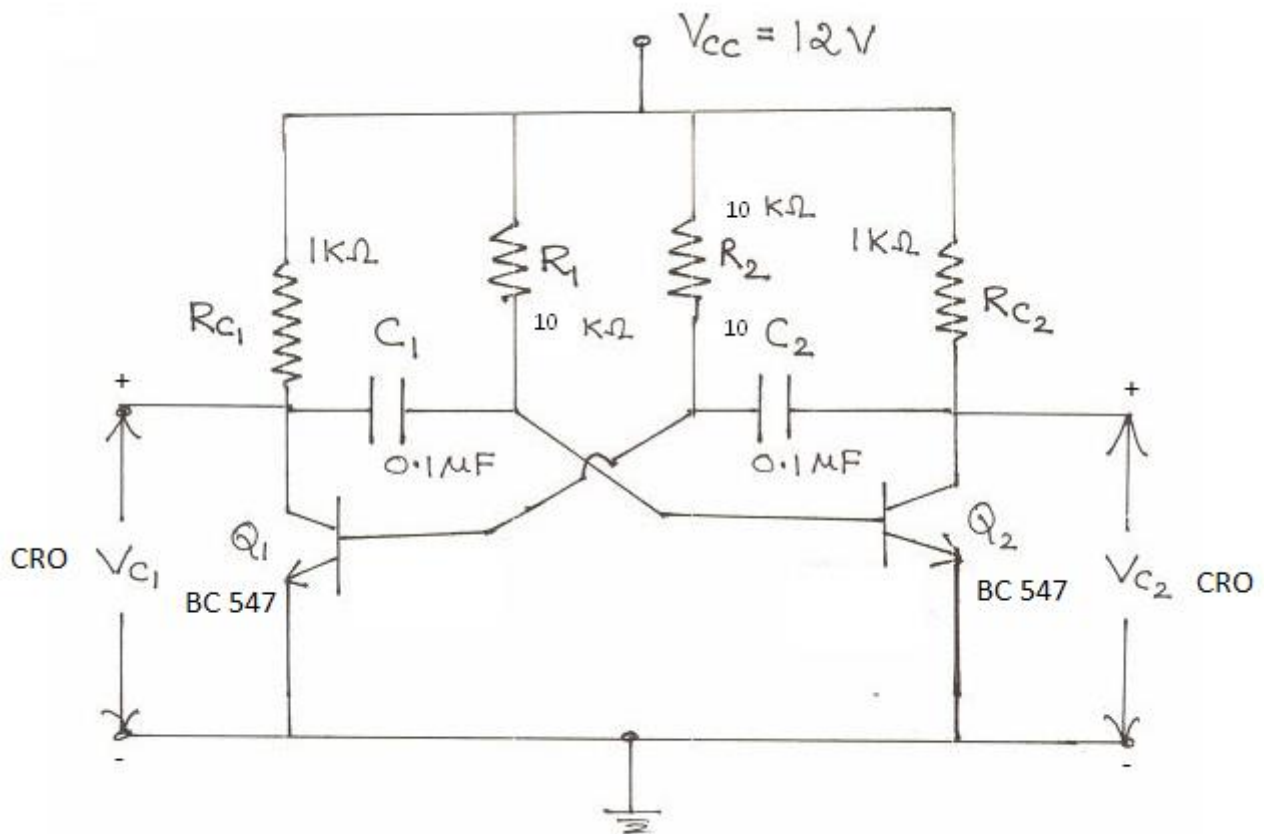
**CIRCUIT DIAGRAMS – SOFTWARE & HARDWARE:**

Fig : Circuit diagram of Astable Multivibrator

**Design Procedure :**

The period T is given by

$$T = T_1 + T_2 = 0.69 (R_1 C_1 + R_2 C_2)$$

For symmetrical circuit,

$$\text{with } R_1 = R_2 = R \text{ \& } C_1 = C_2 = C$$

$$T = 1.38 RC$$

Let  $V_{CC} = 12V$ ;  $h_{fe} = 51$  (for BC107),  $V_{BESat} = 0.7V$ ;  $V_{CESat} = 0.3V$  Let  $C = 0.1\mu F$  &  $T = 1mSec$ .  
 $10^{-3} = 1.38 \times R \times 0.1 \times 10^{-6}$

$R = 7.24K\Omega$  (Practically choose  $10K\Omega$ ) i.e.,  $R_1$  and  $R_2$  resistors =  $10K\Omega$

Let  $I_{Cmax} = 10mA$

$$R_C = \frac{V_{CC} - V_{cesat}}{I_{cmax}} = \frac{12 - 0.3}{0.01} = 1.17K\Omega \text{ (Practically choose } 1K\Omega \text{ ) i.e., } R_{c1} \text{ and } R_{c2} \text{ resistors} = 1K\Omega$$

**Theoretical calculations :**

$$F = 1/T = (1/1.38RC)$$

$$R = 10K\Omega \quad C = 0.1\mu F$$



**PROCEDURE - SOFTWARE :**


1. I have picked up the components from the components bar as per above circuit.
2. Made the connections as per the above circuit diagram by using the components which we have picked up.
3. Connected the CRO across VC1 and VC2 .
6. To simulate the circuit clicked on *run option* through *execute button* in *tool bar*.
7. I have observed the wave forms as shown under the heading of Expected graphs .
8. Observed the Base Voltage and Collector Voltages of Q1 & Q2 on CRO in DC mode and measured the frequency ( $f = 1/T$ ).
9. Traced the waveforms at collector and base as each transistor with the help of dual trace CRO and plot the waveforms.
10. Verified the practical output frequency with theoretical values  $f = 1/T$ , where  $T = 1.38RC$
11. Shut down the system safely.
12. Plotted the graphs for VB1 & VC1 and VB2 and VC2 by taking the Time period on X-axis and Voltage on Y-axis for all graphs as per shown in the Expected graphs heading.
13. Noted the practical Time period T values at VB1 & VC1 and VB2 and VC2 and noted down in the corresponding columns of the Tabular form.
14. Calculated the practical frequency values by using formula  $1/T$  and noted down in the corresponding columns of the Tabular form.
15. I Compared the Theoretical and practical values are approximately same.

**PROCEDURE - HARDWARE :**

1. I have made the connections as per the circuit diagram.
2. Observed the Base Voltage and Collector Voltages of Q1 & Q2 on CRO in DC mode and measured the frequency ( $f = 1/T$ ).
3. Traced the waveforms at collector and base as each transistor with the help of dual trace CRO and plot the waveforms.
4. Verified the practical output frequency with theoretical values  $f = 1/T$ , where  $T = 1.38RC$
5. Switched off the RPS and CRO.
6. Plotted the graphs for VB1 & VC1 and VB2 and VC2 by taking the Time period on X-axis and Voltage on Y-axis for all graphs as per shown in the Expected graphs heading.
7. Noted the practical Time period T values at VB1 & VC1 and VB2 and VC2 and noted down in the corresponding columns of the Tabular form.
8. Calculated the practical frequency values by using formula  $1/T$  and noted down in the corresponding columns of the Tabular form.
9. I Compared the Theoretical and practical values are approximately same.

**TABULAR FORMS – SOFTWARE & HARDWARE :**

	Software					Hardware			
	At VB1	At VC1	At VB2	At VC2		At VB1	At VC1	At VB2	At VC2
Theoretical Time period (T)									
Theoretical Frequency (f) = 1/T									
Practical Time period (T)									
Practical Frequency (f) = 1/T									

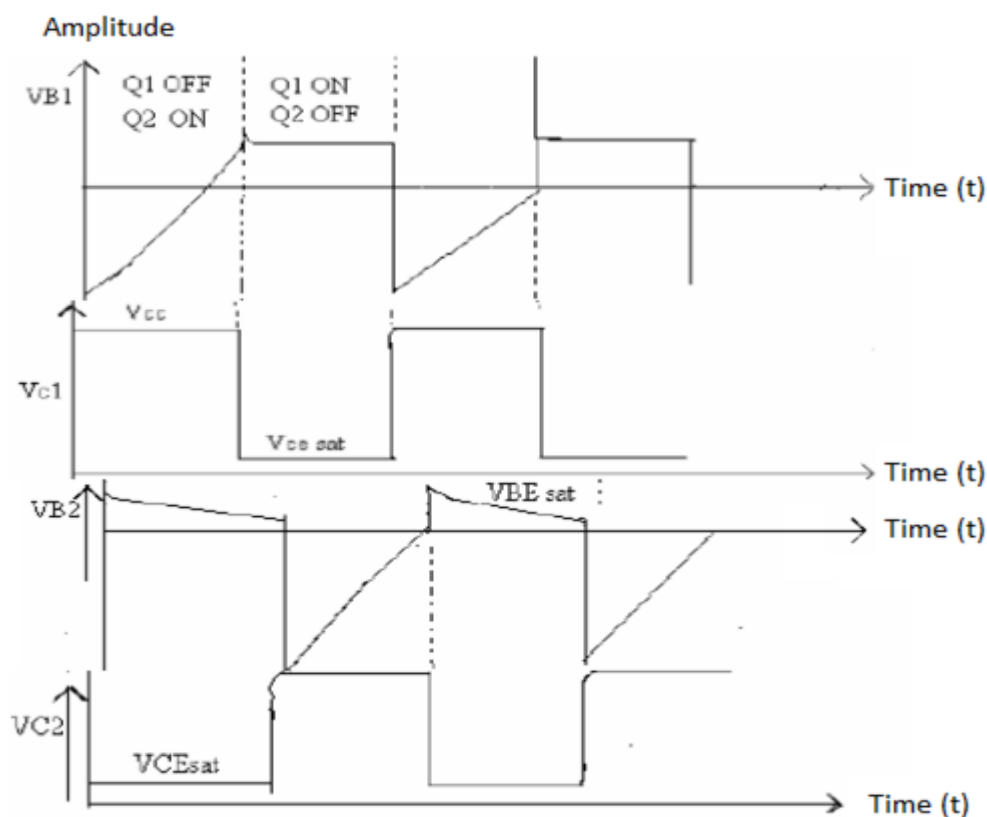**EXPECTED WAVEFORM - SOFTWARE & HARDWARE :****Fig : Waveforms of Astable Multivibrator**

**RESULT :** I have conducted and verified the Astable Multivibrator.

**VIVA VOICE Questions :**

*Note :* The questions which are avail in *Software section-A* under the same experiment are applicable here also.

# **PART – D**

**Data sheets, Rules & Syllabus Copy**



## A. DATA SHEETS

### PN JUNCTION DIODE :


**1N4001 - 1N4007    1.0A**

#### Features

- Diffused Junction
- High Current Capability and Low Forward Voltage Drop
- Surge Overload Rating to 30A Peak
- Low Reverse Leakage Current
- Lead Free Finish, RoHS Compliant (Note 3)
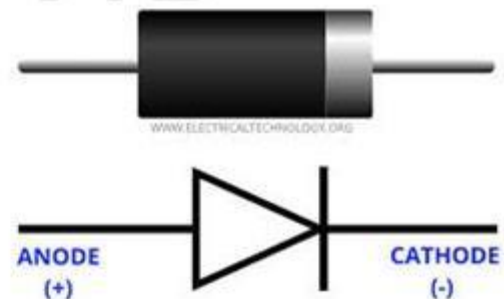
#### Mechanical Data

- Case: DO-41
- Case Material: Molded Plastic. UL Flammability Classification Rating 94V-0
- Moisture Sensitivity: Level 1 per J-STD-020D
- Terminals: Finish - Bright Tin. Plated Leads
- Solderable per MIL-STD-202, Method 208
- Polarity: Cathode Band
- Ordering Information: See Page 2
- Marking: Type Number
- Weight: 0.30 grams (Approximate)



**Maximum Ratings and Electrical Characteristics** (@ $T_A = +25^\circ\text{C}$  unless otherwise specified.) Single phase, half wave,

For capacitive load, derate current by 20%.

Characteristic	Symbol	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	Unit
Peak Repetitive Reverse Voltage Working Peak Reverse Voltage DC Blocking Voltage	$V_{RRM}$ $V_{RW}$ $M V_R$	50	100	200	400	800	800	1000	V
RMS Reverse Voltage	$V_{R(RMS)}$	35	70	140	280	420	580	700	V
Average Rectified Output Current (Note 1) @ $T_A = +75^{\circ}C$	$I_O$	1.0							A
Non-Repetitive Peak Forward Surge Current 8.3ms Single Half Sine-Wave Superimposed on Rated Load	$I_{FSM}$	30							A
Forward Voltage @ $I_F = 1.0A$	$V_{FM}$	1.0							V
Peak Reverse Current @ $T_A = +25^{\circ}C$ at Rated DC Blocking Voltage @ $T_A = +100^{\circ}C$	$I_{RM}$	5.0 50							$\mu A$
Typical Junction Capacitance (Note 2)	$C_j$	15				8			pF
Typical Thermal Resistance Junction to Ambient	$R_{\theta JA}$	100							K/W
Maximum DC Blocking Voltage Temperature	$T_A$	+150							$^{\circ}C$
Operating and Storage Temperature Range	$T_J, T_{STG}$	-65 to +150							$^{\circ}C$

**ZENER DIODE :****TOSHIBA**

1Z6.2~1Z390, 1Z6.8A~1Z30A

TOSHIBA ZENER DIODE SILICON DIFFUSED JUNCTION TYPE

**1Z6.2~1Z390, 1Z6.8A~1Z30A**


CONSTANT VOLTAGE REGULATION

TRANSIENT SUPPRESSORS

- Average Power Dissipation :  $P = 1W$
- Peak Reverse Power Dissipation :  $PRSM = 200W$  at  $t_w = 200\mu s$
- Zener Voltage :  $V_Z = 6.2 \sim 390V$
- Tolerance of Zener Voltage
  - 1Z6.2 Series :  $\pm 10\%$
  - 1Z6.8A Series :  $\pm 5\%$
- Plastic Mold Package

**MAXIMUM RATINGS ( $T_a = 25^\circ C$ )**

CHARACTERISTIC	SYMBOL	RATING	UNIT
Power Dissipation	P	1	W
Junction Temperature	$T_j$	-40~150	$^\circ C$
Storage Temperature Range	$T_{stg}$	-40~150	$^\circ C$

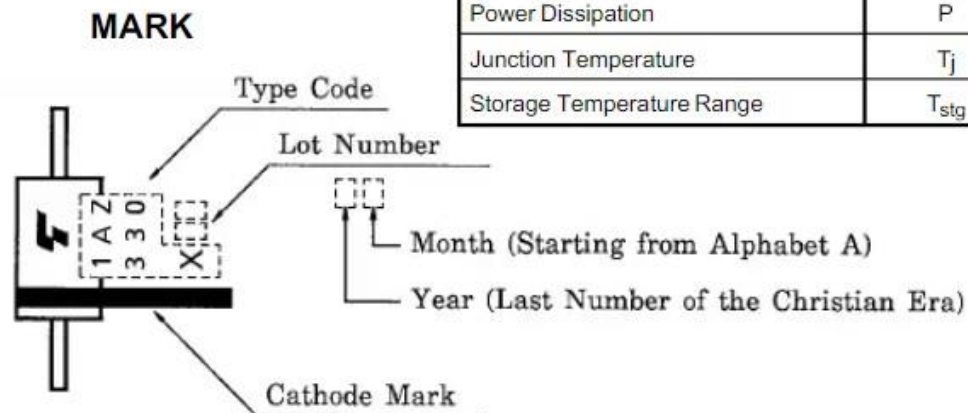

Color : Silver


**BIPOLAR JUNCTION TRANSISTORS (BJT) :**

## BC546 / BC547 / BC548 / BC549 / BC550

### NPN Epitaxial Silicon Transistor

**Features**

- Switching and Amplifier
- High-Voltage: BC546,  $V_{CEO} = 65\text{ V}$
- Low-Noise: BC549, BC550
- Complement to BC556, BC557, BC558, BC559, and BC560

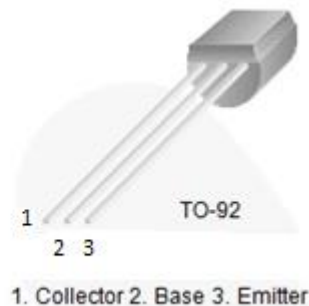**Absolute Maximum Ratings**

Stresses exceeding the absolute maximum ratings may damage the device. The device may not function or be operable above the recommended operating conditions and stressing the parts to these levels is not recommended. In addition, extended exposure to stresses above the recommended operating conditions may affect device reliability. The absolute maximum ratings are stress ratings only. Values are at  $T_A = 25^\circ\text{C}$  unless otherwise noted.



Symbol	Parameter	Value	Unit
$V_{CBO}$	Collector-Base Voltage	BC546	80
		BC547 / BC550	50
		BC548 / BC549	30
$V_{CEO}$	Collector-Emitter Voltage	BC546	65
		BC547 / BC550	45
		BC548 / BC549	30
$V_{EBO}$	Emitter-Base Voltage	BC546 / BC547	6
		BC548 / BC549 / BC550	5
$I_C$	Collector Current (DC)	100	mA
$P_C$	Collector Power Dissipation	500	mW
$T_J$	Junction Temperature	150	$^\circ\text{C}$
$T_{STG}$	Storage Temperature Range	-65 to +150	$^\circ\text{C}$

## Electrical Characteristics

Values are at  $T_A = 25^\circ\text{C}$  unless otherwise noted.

Symbol	Parameter	Conditions	Min.	Typ.	Max.	Unit
$I_{CBO}$	Collector Cut-Off Current	$V_{CB} = 30\text{ V}, I_E = 0$			15	nA
$h_{FE}$	DC Current Gain	$V_{CE} = 5\text{ V}, I_C = 2\text{ mA}$	110		800	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = 10\text{ mA}, I_B = 0.5\text{ mA}$		90	250	mV
		$I_C = 100\text{ mA}, I_B = 5\text{ mA}$		250	600	
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	$I_C = 10\text{ mA}, I_B = 0.5\text{ mA}$		700		mV
		$I_C = 100\text{ mA}, I_B = 5\text{ mA}$		900		
$V_{BE(on)}$	Base-Emitter On Voltage	$V_{CE} = 5\text{ V}, I_C = 2\text{ mA}$	580	660	700	mV
		$V_{CE} = 5\text{ V}, I_C = 10\text{ mA}$			720	
$f_T$	Current Gain Bandwidth Product	$V_{CE} = 5\text{ V}, I_C = 10\text{ mA}, f = 100\text{ MHz}$		300		MHz
$C_{ob}$	Output Capacitance	$V_{CB} = 10\text{ V}, I_E = 0, f = 1\text{ MHz}$		3.5	6.0	pF
$C_{ib}$	Input Capacitance	$V_{EB} = 0.5\text{ V}, I_C = 0, f = 1\text{ MHz}$		9		pF
NF	Noise Figure	BC546 / BC547 / BC548	$V_{CE} = 5\text{ V}, I_C = 200\text{ }\mu\text{A}, f = 1\text{ kHz}, R_G = 2\text{ k}\Omega$	2.0	10.0	dB
		BC549 / BC550		1.2	4.0	
		BC549	$V_{CE} = 5\text{ V}, I_C = 200\text{ }\mu\text{A}, R_G = 2\text{ k}\Omega, f = 30\text{ to }15000\text{ MHz}$	1.4	4.0	
		BC550		1.4	3.0	

## $h_{FE}$ Classification


Classification	A	B	C
$h_{FE}$	110 ~ 220	200 ~ 450	420 ~ 800



**UNIJUNCTION TRANSISTOR (UJT) :**

**2N2646  
2N2647**


**SILICON  
PN UNIJUNCTION TRANSISTORS**




[www.centrasemi.com](http://www.centrasemi.com)

**DESCRIPTION:**  
The CENTRAL SEMICONDUCTOR 2N2646 and 2N2647 devices are silicon PN Unijunction Transistors designed for general purpose industrial applications.

**UJT Symbol & Terminal Identification**

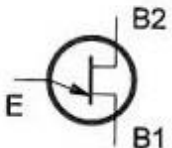

**(a). Symbol**

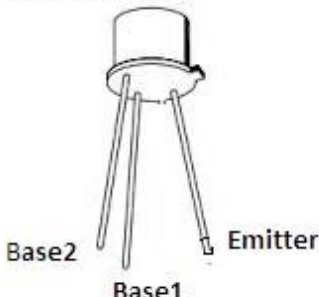

**(b). Terminal Identification**

MAXIMUM RATINGS: ( $T_A=25^\circ\text{C}$ )	SYMBOL		UNITS
Emitter Reverse Voltage	$V_{B2E}$	30	V
Interbase Voltage	$V_{B2B1}$	35	V
RMS Emitter Current	$I_e$	50	mA
Peak Emitter Current (Duty Cycle $\leq 1\%$ , $PRR \leq 10\text{pps}$ )	$I_{ep}$	2.0	A
RMS Power Dissipation	$P_D$	300	mW
Operating and Storage Junction Temperature	$T_J, T_{stg}$	-65 to +150	$^\circ\text{C}$

**ELECTRICAL CHARACTERISTICS: ( $T_A=25^\circ\text{C}$  unless otherwise noted)**


SYMBOL	TEST CONDITIONS	2N2646		2N2647		UNITS
		MIN	MAX	MIN	MAX	
$\eta$	$V_{B2B1}=10\text{V}$	0.56	0.75	0.68	0.82	
$R_{BB}$	$V_{B2B1}=3.0\text{V}$	4.7	9.1	4.7	9.1	k $\Omega$
$I_{EB2O}$	$V_{B2E}=30\text{V}$	-	12	-	0.2	$\mu\text{A}$
$I_V$	$V_{B2B1}=20\text{V}, R_{B2}=100\Omega$	4.0	-	8.0	18	mA
$I_P$	$V_{B2B1}=25\text{V}$	-	5.0	-	2.0	$\mu\text{A}$
$V_{OB1}$	$V_1=20\text{V}$	3.0	-	6.0	-	V

**FIELD EFFECT TRANSISTOR (FET) :**

MOTOROLA SC-{XSTRS/R F}

**MAXIMUM RATINGS**

Rating	Symbol	Value	Unit
Drain-Source Voltage	$V_{DS}$	30	Vdc
Drain-Gate Voltage	$V_{DG}$	30	Vdc
Reverse Gate-Source Voltage	$V_{GSR}$	-30	Vdc
Forward Gate Current	$I_{GF}$	10	mAdc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	PD	300 1.71	mW mW/ $^\circ\text{C}$
Operating and Storage Junction Temperature Range	$T_J, T_{stg}$	-65 to +150	$^\circ\text{C}$

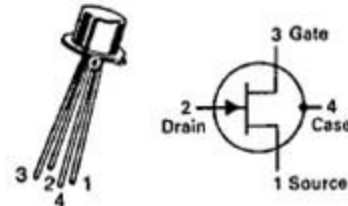**BFW10  
BFW11****CASE 20-03, STYLE 1  
TO-72 (TO-206A)****JFET  
VHF/UHF AMPLIFIER  
N-CHANNEL - DEPLETION****ELECTRICAL CHARACTERISTICS ( $T_A = 25^\circ\text{C}$  unless otherwise noted.)**

Characteristic	Symbol	Min	Typ	Max	Unit
<b>OFF CHARACTERISTICS</b>					
Gate-Source Breakdown Voltage ( $I_G = 10 \mu\text{Adc}$ , $V_{DS} = 0$ )	$V_{(BR)GSS}$	30	—	—	Vdc
Gate-Source Cutoff Voltage ( $V_{DS} = 15 \text{ Vdc}$ , $I_D = 0.5 \text{ nAdc}$ )	$V_{GS(off)}$	—	—	8 6	Vdc
Gate Reverse Current ( $V_{GS} = 20 \text{ Vdc}$ , $V_{DS} = 0$ )	$I_{GSS}$	—	—	0.1	nAdc
Gate-Source Voltage ( $V_{DS} = 15 \text{ Vdc}$ , $I_D = 400 \mu\text{Adc}$ )	$V_{GS}$	2	—	7.5	Vdc
Gate-Source Voltage ( $V_{DS} = 15 \text{ Vdc}$ , $I_D = 50 \mu\text{Adc}$ )	$V_{GS}$	1.25	—	4	Vdc
<b>ON CHARACTERISTICS</b>					
Zero-Gate Voltage Drain Current ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ )	$I_{DSS}$	8 4	—	20 10	mAdc
<b>SMALL-SIGNAL CHARACTERISTICS</b>					
Forward Transadmittance ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 1 \text{ kHz}$ )	$Y_{fs}$	3.5 3.0	—	6.5 6.5	mmhos
Output Admittance ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 1.0 \text{ kHz}$ )	$Y_{os}$	—	—	85 50	$\mu\text{mhos}$
Input Capacitance ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0 \text{ Vdc}$ , $f = 1.0 \text{ MHz}$ )	$C_{iss}$	—	—	5.0	pF
Reverse Transfer Capacitance ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0 \text{ Vdc}$ , $f = 1.0 \text{ MHz}$ )	$C_{rss}$	—	—	0.8	pF
Forward Transadmittance ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 200 \text{ MHz}$ )	$Y_{fs}$	3.2	—	—	mmhos
Equivalent Noise Voltage ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0$ , $f = 25 \text{ Hz}$ )	$e_n$	—	—	75	nV/ $\sqrt{\text{Hz}}$
Noise Figure ( $V_{DS} = 15 \text{ Vdc}$ , $V_{GS} = 0 \text{ V}$ , see Figures 1, 2, 3)	NF	—	—	2.5	dB

## N-channel silicon field-effect transistors

BF245A; BF245B;  
BF245C

## FEATURES

- Interchangeability of drain and source connections
- Frequencies up to 700 MHz

## APPLICATIONS

- LF, HF and DC amplifiers.

## DESCRIPTION

General purpose N-channel symmetrical junction field-effect transistors in a plastic TO-92 variant package.

## CAUTION

The device is supplied in an antistatic package. The gate-source input must be protected against static discharge during transport or handling.

## PINNING

PIN	SYMBOL	DESCRIPTION
1	d	drain
2	s	source
3	g	gate

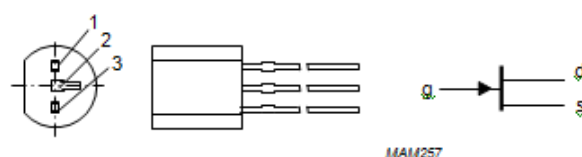


Fig.1 Simplified outline (TO-92 variant) and symbol.

## QUICK REFERENCE DATA

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
$V_{DS}$	drain-source voltage		–	–	$\pm 30$	V
$V_{GSoff}$	gate-source cut-off voltage	$I_D = 10 \text{ nA}$ ; $V_{DS} = 15 \text{ V}$	–0.25	–	–8	V
$V_{GS0}$	gate-source voltage	open drain	–	–	–30	V
$I_{DSS}$	drain current	$V_{DS} = 15 \text{ V}$ ; $V_{GS} = 0$				
	BF245A		2	–	6.5	mA
	BF245B		6	–	15	mA
	BF245C		12	–	25	mA
$P_{tot}$	total power dissipation	$T_{amb} = 75 \text{ }^\circ\text{C}$	–	–	300	mW
$ y_{fs} $	forward transfer admittance	$V_{DS} = 15 \text{ V}$ ; $V_{GS} = 0$ ; $f = 1 \text{ kHz}$ ; $T_{amb} = 25 \text{ }^\circ\text{C}$	3	–	6.5	mS
$C_{ts}$	reverse transfer capacitance	$V_{DS} = 20 \text{ V}$ ; $V_{GS} = -1 \text{ V}$ ; $f = 1 \text{ MHz}$ ; $T_{amb} = 25 \text{ }^\circ\text{C}$	–	1.1	–	pF

**LIMITING VALUES**

In accordance with the Absolute Maximum Rating System (IEC 134).

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
$V_{DS}$	drain-source voltage		–	$\pm 30$	V
$V_{GDO}$	gate-drain voltage	open source	–	–30	V
$V_{GSO}$	gate-source voltage	open drain	–	–30	V
$I_D$	drain current		–	25	mA
$I_G$	gate current		–	10	mA
$P_{tot}$	total power dissipation	up to $T_{amb} = 75\text{ }^{\circ}\text{C}$ ;	–	300	mW
		up to $T_{amb} = 90\text{ }^{\circ}\text{C}$ ; note 1	–	300	mW
$T_{stg}$	storage temperature		–65	+150	$^{\circ}\text{C}$
$T_j$	operating junction temperature		–	150	$^{\circ}\text{C}$

**Note**

- Device mounted on a printed-circuit board, minimum lead length 3 mm, mounting pad for drain lead minimum 10 mm  $\times$  10 mm.

**THERMAL CHARACTERISTICS**

SYMBOL	PARAMETER	CONDITIONS	VALUE	UNIT
$R_{th\ j-a}$	thermal resistance from junction to ambient	in free air	250	K/W
	thermal resistance from junction to ambient		200	K/W

**STATIC CHARACTERISTICS**

$T_j = 25\text{ }^{\circ}\text{C}$ ; unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
$V_{(BR)GSS}$	gate-source breakdown voltage	$I_G = -1\text{ }\mu\text{A}$ ; $V_{DS} = 0$	–30	–	V
$V_{GSoff}$	gate-source cut-off voltage	$I_D = 10\text{ nA}$ ; $V_{DS} = 15\text{ V}$	–0.25	–8.0	V
$V_{GS}$	gate-source voltage	$I_D = 200\text{ }\mu\text{A}$ ; $V_{DS} = 15\text{ V}$			
	BF245A		–0.4	–2.2	V
	BF245B		–1.6	–3.8	V
	BF245C		–3.2	–7.5	V
$I_{DSS}$	drain current	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; note 1			
	BF245A		2	6.5	mA
	BF245B		6	15	mA
	BF245C		12	25	mA
$I_{GSS}$	gate cut-off current	$V_{GS} = -20\text{ V}$ ; $V_{DS} = 0$	–	–5	nA
		$V_{GS} = -20\text{ V}$ ; $V_{DS} = 0$ ; $T_j = 125\text{ }^{\circ}\text{C}$	–	–0.5	$\mu\text{A}$

**Note**


- Measured under pulse conditions:  $t_p = 300\text{ }\mu\text{s}$ ;  $\delta \leq 0.02$ .

**DYNAMIC CHARACTERISTICS**Common source;  $T_{amb} = 25\text{ }^{\circ}\text{C}$ ; unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
$C_{is}$	input capacitance	$V_{DS} = 20\text{ V}$ ; $V_{GS} = -1\text{ V}$ ; $f = 1\text{ MHz}$	–	4	–	pF
$C_{rs}$	reverse transfer capacitance	$V_{DS} = 20\text{ V}$ ; $V_{GS} = -1\text{ V}$ ; $f = 1\text{ MHz}$	–	1.1	–	pF
$C_{os}$	output capacitance	$V_{DS} = 20\text{ V}$ ; $V_{GS} = -1\text{ V}$ ; $f = 1\text{ MHz}$	–	1.6	–	pF
$g_{is}$	input conductance	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $f = 200\text{ MHz}$	–	250	–	$\mu\text{S}$
$g_{os}$	output conductance	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $f = 200\text{ MHz}$	–	40	–	$\mu\text{S}$
$ y_{fs} $	forward transfer admittance	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $f = 1\text{ kHz}$	3	–	6.5	mS
		$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $f = 200\text{ MHz}$	–	6	–	mS
$ y_{rs} $	reverse transfer admittance	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $f = 200\text{ MHz}$	–	1.4	–	mS
$ y_{os} $	output admittance	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $f = 1\text{ kHz}$	–	25	–	$\mu\text{S}$
$f_{gfs}$	cut-off frequency	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $g_{fs} = 0.7$ of its value at 1 kHz	–	700	–	MHz
F	noise figure	$V_{DS} = 15\text{ V}$ ; $V_{GS} = 0$ ; $f = 100\text{ MHz}$ ; $R_G = 1\text{ k}\Omega$ (common source); input tuned to minimum noise	–	1.5	–	dB

**MOSFET IRFZ 44N :****IRFZ44NPbF**


HEXFET® Power MOSFET

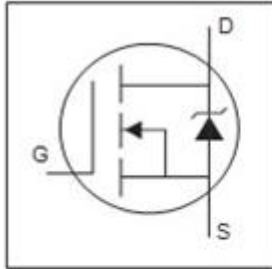

$$V_{DSS} = 55V$$

$$R_{DS(on)} = 17.5m\Omega$$

$$I_D = 49A$$

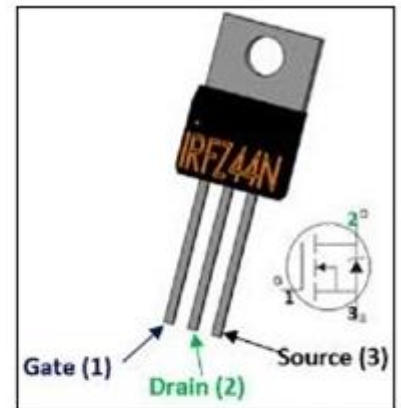**Absolute Maximum Ratings**

	Parameter	Max.	Units
$I_D @ T_C = 25^\circ C$	Continuous Drain Current, $V_{GS} @ 10V$	49	A
$I_D @ T_C = 100^\circ C$	Continuous Drain Current, $V_{GS} @ 10V$	35	
$I_{DM}$	Pulsed Drain Current ①	160	
$P_D @ T_C = 25^\circ C$	Power Dissipation	94	W
	Linear Derating Factor	0.63	W/°C
$V_{GS}$	Gate-to-Source Voltage	$\pm 20$	V
$I_{AR}$	Avalanche Current①	25	A
$E_{AR}$	Repetitive Avalanche Energy①	9.4	mJ
$dv/dt$	Peak Diode Recovery $dv/dt$ ③	5.0	V/ns
$T_J$	Operating Junction and	-55 to + 175	°C
$T_{STG}$	Storage Temperature Range		
	Soldering Temperature, for 10 seconds	300 (1.6mm from case )	
	Mounting torque, 6-32 or M3 screw	10 lbf•in (1.1N•m)	


**Thermal Resistance**

	Parameter	Typ.	Max.	Units
$R_{\theta JC}$	Junction-to-Case	—	1.5	°C/W
$R_{\theta CS}$	Case-to-Sink, Flat, Greased Surface	0.50	—	
$R_{\theta JA}$	Junction-to-Ambient	—	62	



**Electrical Characteristics @  $T_J = 25^\circ\text{C}$  (unless otherwise specified)**

	Parameter	Min.	Typ.	Max.	Units	Conditions
$V_{(BR)DSS}$	Drain-to-Source Breakdown Voltage	55	—	—	V	$V_{GS} = 0V, I_D = 250\mu A$
$\Delta V_{(BR)DSS}/\Delta T_J$	Breakdown Voltage Temp. Coefficient	—	0.058	—	V/ $^\circ\text{C}$	Reference to $25^\circ\text{C}$ , $I_D = 1\text{mA}$
$R_{DS(on)}$	Static Drain-to-Source On-Resistance	—	—	17.5	m $\Omega$	$V_{GS} = 10V, I_D = 25A$ ④
$V_{GS(th)}$	Gate Threshold Voltage	2.0	—	4.0	V	$V_{DS} = V_{GS}, I_D = 250\mu A$
$g_{fs}$	Forward Transconductance	19	—	—	S	$V_{DS} = 25V, I_D = 25A$ ④
$I_{DSS}$	Drain-to-Source Leakage Current	—	—	25	$\mu A$	$V_{DS} = 55V, V_{GS} = 0V$
		—	—	250		$V_{DS} = 44V, V_{GS} = 0V, T_J = 150^\circ\text{C}$
$I_{GSS}$	Gate-to-Source Forward Leakage	—	—	100	nA	$V_{GS} = 20V$
	Gate-to-Source Reverse Leakage	—	—	-100		$V_{GS} = -20V$
$Q_g$	Total Gate Charge	—	—	63	nC	$I_D = 25A$
$Q_{gs}$	Gate-to-Source Charge	—	—	14		$V_{DS} = 44V$
$Q_{gd}$	Gate-to-Drain ("Miller") Charge	—	—	23		$V_{GS} = 10V$ , See Fig. 6 and 13
$t_{d(on)}$	Turn-On Delay Time	—	12	—	ns	$V_{DD} = 28V$
$t_r$	Rise Time	—	60	—		$I_D = 25A$
$t_{d(off)}$	Turn-Off Delay Time	—	44	—		$R_G = 12\Omega$
$t_f$	Fall Time	—	45	—		$V_{GS} = 10V$ , See Fig. 10 ④
$L_D$	Internal Drain Inductance	—	4.5	—	nH	Between lead, 6mm (0.25in.) from package and center of die contact
$L_S$	Internal Source Inductance	—	7.5	—		
$C_{iss}$	Input Capacitance	—	1470	—	pF	$V_{GS} = 0V$
$C_{oss}$	Output Capacitance	—	360	—		$V_{DS} = 25V$
$C_{rss}$	Reverse Transfer Capacitance	—	88	—		$f = 1.0\text{MHz}$ , See Fig. 5
$E_{AS}$	Single Pulse Avalanche Energy ②	—	530③	150⑥	mJ	$I_{AS} = 25A, L = 0.47\text{mH}$

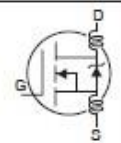**Source-Drain Ratings and Characteristics**

	Parameter	Min.	Typ.	Max.	Units	Conditions
$I_S$	Continuous Source Current (Body Diode)	—	—	49	A	MOSFET symbol showing the integral reverse p-n junction diode.
$I_{SM}$	Pulsed Source Current (Body Diode) ①	—	—	160		
$V_{SD}$	Diode Forward Voltage	—	—	1.3	V	$T_J = 25^\circ\text{C}, I_S = 25A, V_{GS} = 0V$ ④
$t_{rr}$	Reverse Recovery Time	—	63	95	ns	$T_J = 25^\circ\text{C}, I_F = 25A$
$Q_{rr}$	Reverse Recovery Charge	—	170	260	nC	$di/dt = 100A/\mu s$ ④
$t_{on}$	Forward Turn-On Time	Intrinsic turn-on time is negligible (turn-on is dominated by $L_S + L_D$ )				

**Notes:**

- ① Repetitive rating; pulse width limited by max. junction temperature. (See fig. 11)
- ② Starting  $T_J = 25^\circ\text{C}$ ,  $L = 0.48\text{mH}$   
 $R_G = 25\Omega$ ,  $I_{AS} = 25A$ . (See Figure 12)

- ③  $I_{SD} \leq 25A$ ,  $di/dt \leq 230A/\mu s$ ,  $V_{DD} \leq V_{(BR)DSS}$ ,  
 $T_J \leq 175^\circ\text{C}$

- ④ Pulse width  $\leq 400\mu s$ ; duty cycle  $\leq 2\%$ .

- ⑤ This is a typical value at device destruction and represents operation outside rated limits.

- ⑥ This is a calculated value limited to  $T_J = 175^\circ\text{C}$ .





## **RULES TO BE FOLLOWED WHILE OPERATING THE REGULATED POWERSUPPLY(RPS)**

The following rules should be followed before switch ON the Regulated Power Supply,

1. Initially Keep the *voltage Course & Voltage fine controls* of RPS at minimum position. Later (After switch ON the RPS) can vary these controls slowly to get the required voltage.
2. Always keep the Current Limit control at maximum position, Otherwise the display can shows the constant voltage instead of varying.



### **Trouble shooting while operating the rps :**

The following trouble shooting can done while operating the RPS,

During connecting the RPS to the circuit and varying the Voltage Course & Voltage Fine Controls, If it displays the voltage as constant or above 30V then it can said that either the circuit is shorted OR the Current Limit control is not kept at maximum position. This problem can solve to prevent the circuit from shorted and by keeping the Current Limit control at maximum.

### **RULES TO OPERATE THE CRO:**

The following rules should be follows before operate the CRO.

1. Keep the following controls at middle position or vary until the electron beam is generated.
  - a) INTENSITY
  - b) FOCUS
  - c)  (Horizontal position)  
(Horizontal position common for both channels)
  - d)  Vertical Position (Vertical position individual per each channel)
  - e) LEVEL (Trigger Level)
1. Keep the following controls at maximum position.
  - (a). **VARIABLE** controls of VOLTS/DIV switch in both channels.
  - (b). **SWP.VAR** (Sweep Variation)
2. Keep the following switches at releasing mode.
  - a)  $\times 10$  MAG
  - b) TRIG.ALT
  - c) SLOPE
  - d) ALT/CHOP
  - e) CH2 INV
3. Initially should keep the **TIME/DIV** control at 1mS position, later can change this switch depending upon our requirement , i.e. if we can't get the signal clearly on the CRT, then we can vary this switch until to get the signal.
4. Set the channel selector control **MODE** at the appropriate position i.e. if we want to see the signal in channel1, set this control at CH1, in channel2 set at CH2, in both channels set at DUAL. To add the signals (algebraically sum or difference) available in both channels set at ADD.
5. **AC/GND/DC**: Before setting the signals on CRT, first we should keep the electron beam on reference line. To set this beam on reference line, keep this control at GND position and then vary vertical position control until to get the beam on the reference line. After that to see the applied signals, keep this control at AC or DC positions.
6. Always keep the **TRIGGER MODE** control at AUTO position.
7. Keep the **SOURCE** control at approximate channel. It means if MODE control is selected to CH1, then the SOURCE control should select to CH1. If MODE control at CH2, set the SOURCE control at CH2. If MODE control at DUAL or ADD, set the SOURCE control either at CH1 or CH2.

**Rules for how to write the observation and records:**

1. Make the top & right margins in each page of right side.
2. In top margin make the headings as Experiment No., date and name of the experiment.
3. Circuit diagrams, tabular columns, expected graphs and parameters/calculations should write on leftside page (even No. page) .
4. Aim, apparatus, components, theory, procedure, applications, conclusion and result should write on right side page (Odd No. Page) .
5. Headings should underline with any other ink except red, orange and green.
6. The every new experiment should start with right side page.
7. leave the half of the page under the heading of *theory*.

---

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY ANANTAPUR****B.Tech –II-II Sem 15A04404, ANALOG CIRCUIT ANALYSIS LABORATORY****LIST OF EXPERIMENTS****Branch : For ECE only****R15**

---

**Syllabus – List of experiments :****(Minimum 10 experiments to be done using simulation software and hardware)**

1. Determination of  $f_T$  of a given transistor.
2. Voltage-Series Feedback Amplifier.
3. Current-Shunt Feedback Amplifier.
4. RC Phase Shift/Wein Bridge Oscillator.
5. Hartley/Colpitt's Oscillator.
6. Two Stage RC Coupled Amplifier.
7. Darlington Pair Amplifier.
8. Bootstrapped Emitter follower.
9. Class A Series-fed Power Amplifier.
10. Transformer-coupled Class A Power Amplifier.
11. Class B Push-Pull Power Amplifier.
12. Complementary Symmetry Class B Push-Pull Power Amplifier.
13. Single Tuned Voltage Amplifier.
14. Double Tuned Voltage Amplifier.

